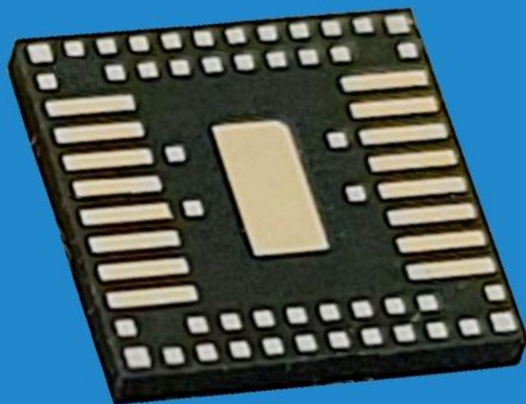




Xilinx Versal AI Core (Low Voltage, Minimum Rails) Power Solution


Power Mapping

Versal AI Core Power Mapping Highlights

- Power tree mappings completed per data received from Xilinx Power Management team
- Both Typical and Upper use-cases are served by the same design
- Data gathered and bench tested by applications team at AnDAPT
 - Data meets or exceeds Xilinx power and timing specifications
- Total 10 power rails covered by 2x AmP ICs including memory and termination rails
- VCCINT (core rail) draws current from 127 A to 152 A and thus will be served using an external IC enabled/disabled by AmP IC
- Total solution area (excluding external core rail) is 1237.61 mm²
- Presentation contains thermal views of both ICs

Xilinx Versal AI Core Power Tree

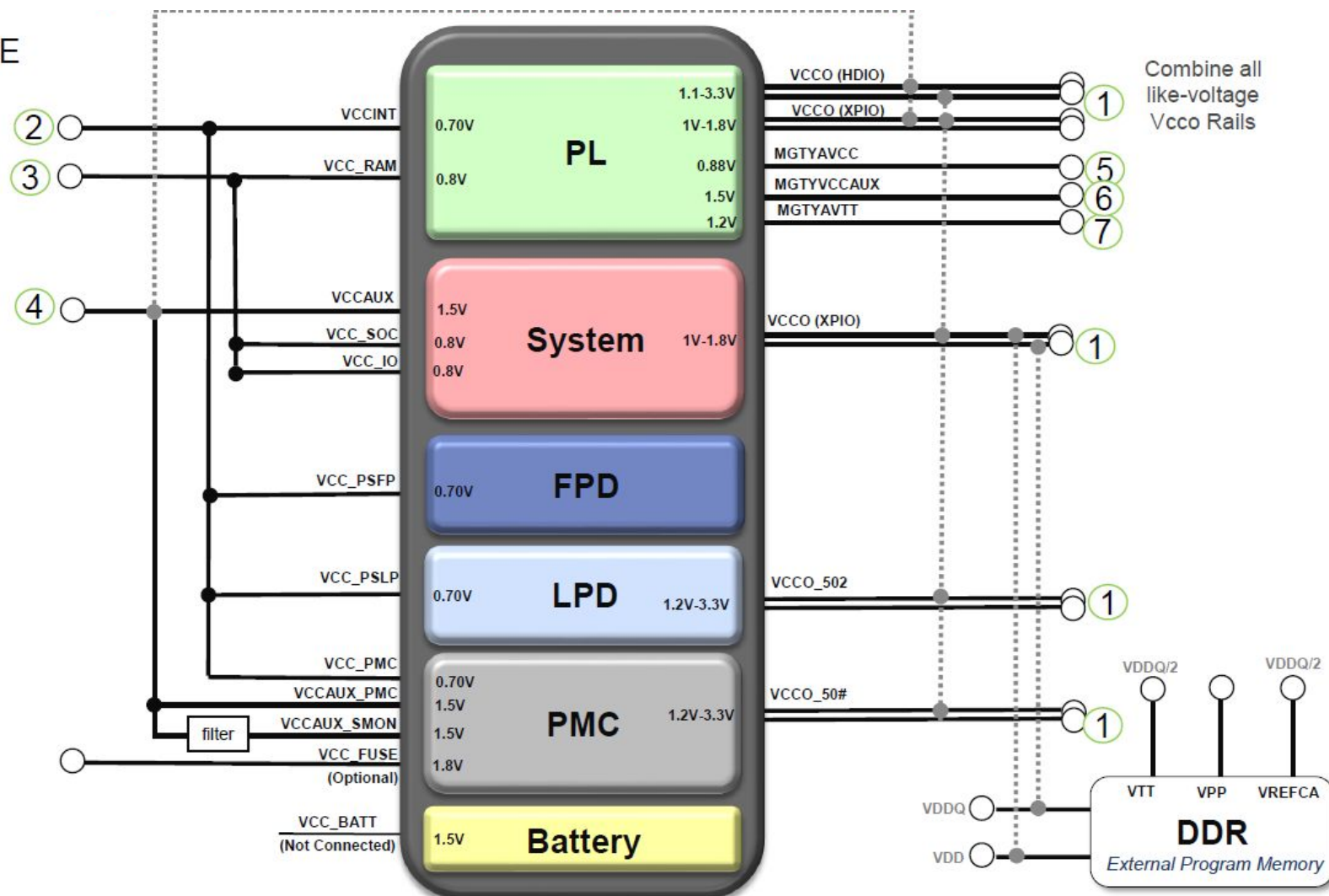Check the latest XPE on Xilinx.com for supported rail groupings and sequences



Versal AI Core Power Rails: Low Voltage (Typical & Upper)

Sequence	Rail Name	Voltage (V)	AI Core	
			Typical (A)	Upper (A)
Rail 1	VCCINT, VCC_PSLP, VCC_PSFP, VCC_PMC	0.7V	127.13	152.556
Rail 2	VCC_IO, VCCRAM, VCC_SOC	0.8V	4.88	5.856
Rail 3	VCCAUX, VCCAUX_SMON, VCCAUX_PMC	1.5V	3.12	3.744
Rail 4	MGTAVCC	.88V	2.47	3.08
Rail 5	MGTAVAUX	1.5V	0.23	0.29
Rail 6	MGTAVTT	1.2V	3.85	4.81
Rail 7	VCCO[0....] (HDIO)	1.1V-3.3V, 1V-1.8V, 1.2V-3.3V	3.39	4.068
Current Total (A)			138.52	166.22


Power Tree Mapping: Versal AI Core

#	Rail	Seq	Power Component	Type	Upstream Rail	Vinput (V)	Vout (V)	Iout (A)	AnDAPT PMIC
1	VCCO_XPIO (VCCO_XPIO, VCCO_HDIO)	1	Sync Buck	C200	PVIN	12	1.5	6	ARD_X_VRACRA_IC1
2	VCCO_503 (VCCO_502, VCCO_50X)	1	Sync Buck	C200	PVIN	12	1.5	4	
3	VCCINT (VCCINT, VCC_PMC, VCC_PSF, VCC_PSLP)	2	Ext IC	-	PVIN	12	0.7	152	
4	VCC_RAM (VCC_RAM, VCC_SOC, VCC_IO)	3	Sync Buck	C200	PVIN	12	0.8	5.8	
5	VCCAUX (VCCAUX, VCCAUX_PMC, VCCAUX_SMON)	4	Sync Buck	C200	PVIN	12	1.5	3.8 + 0.29	
6	MGTAVCC	5	Sync Buck	C200	PVIN	12	0.88	3.1	ARD_X_VRACRA_IC2
7	MGTAVCCAUX	6	Load Switch	C750	VCCAUX	1.5	1.5	0.29	
8	MGTAVTT	7	Async Buck	C150	PVIN	12	1.2	4.81	
9	VDDQ	8	Sync Buck	C200	PVIN	12	1.2	3 + 2	
10	VTT	9	VTT Terminator	C210	VDDQ	1.2	0.6	2	


PVIN = 12V

Total estimated solution area = 1237.61 mm²


Power Tree Mapping- Versal AI Core

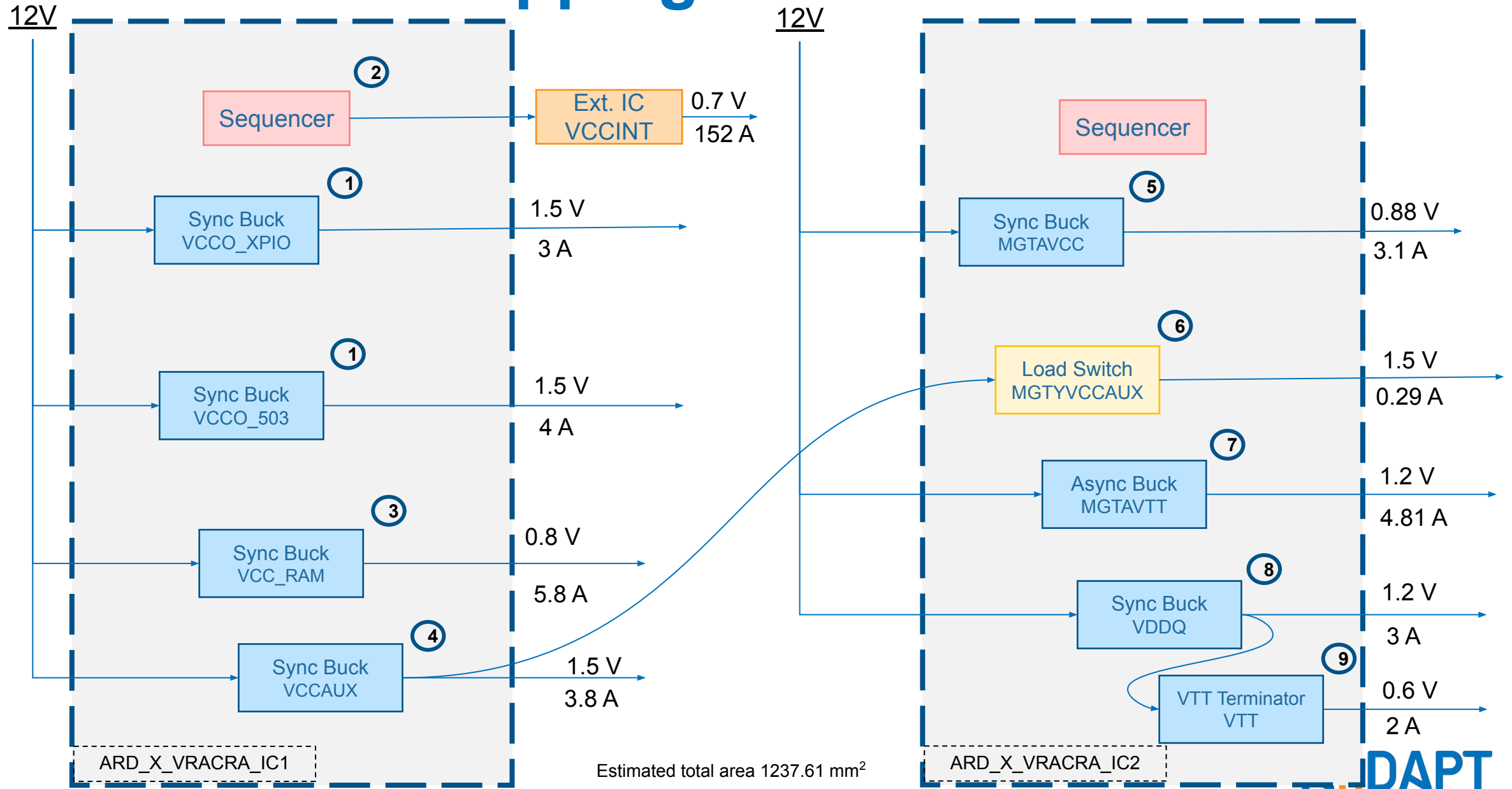


Mapping (WebAmP View) Design –IC1

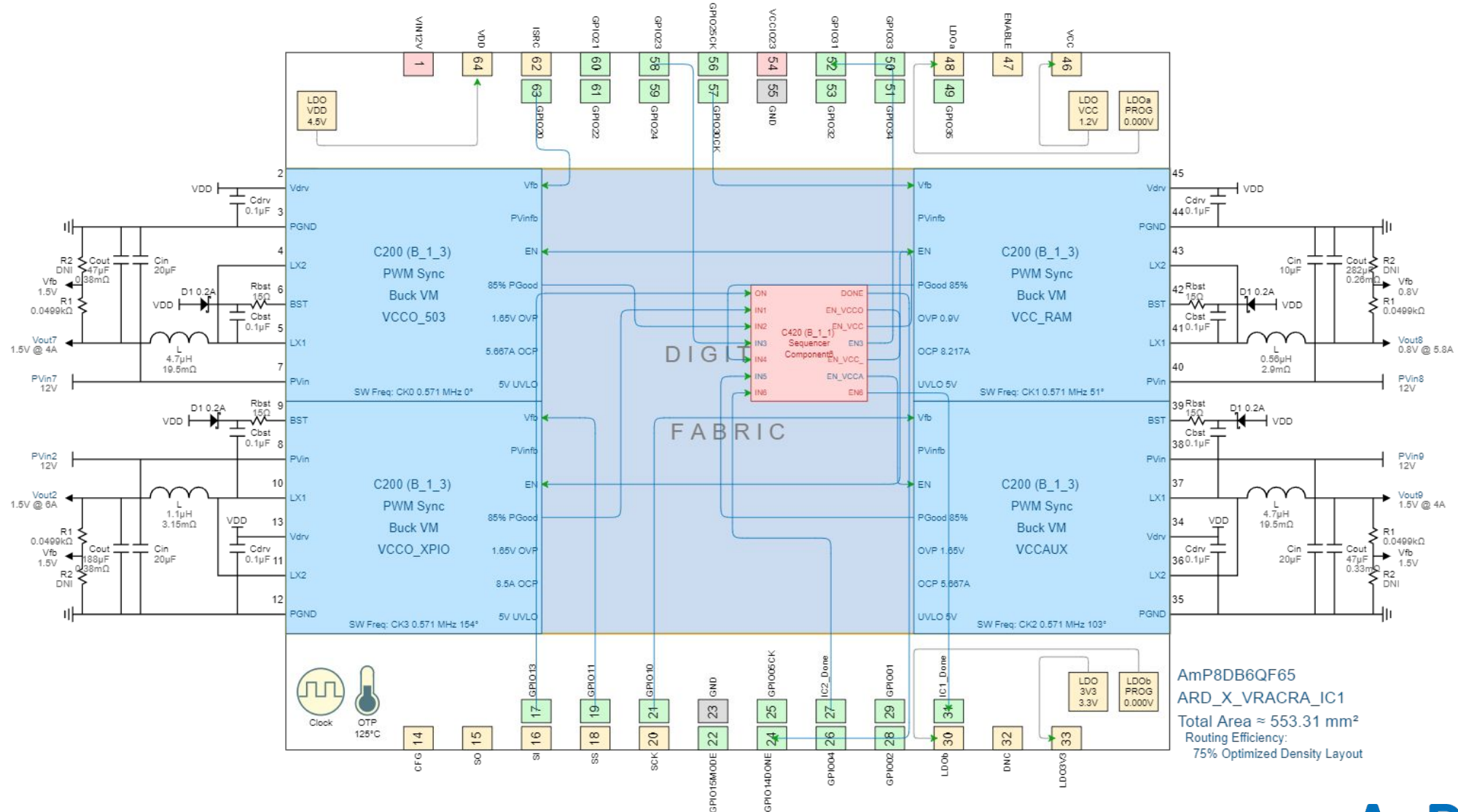


Mapping (Thermal View) –IC1

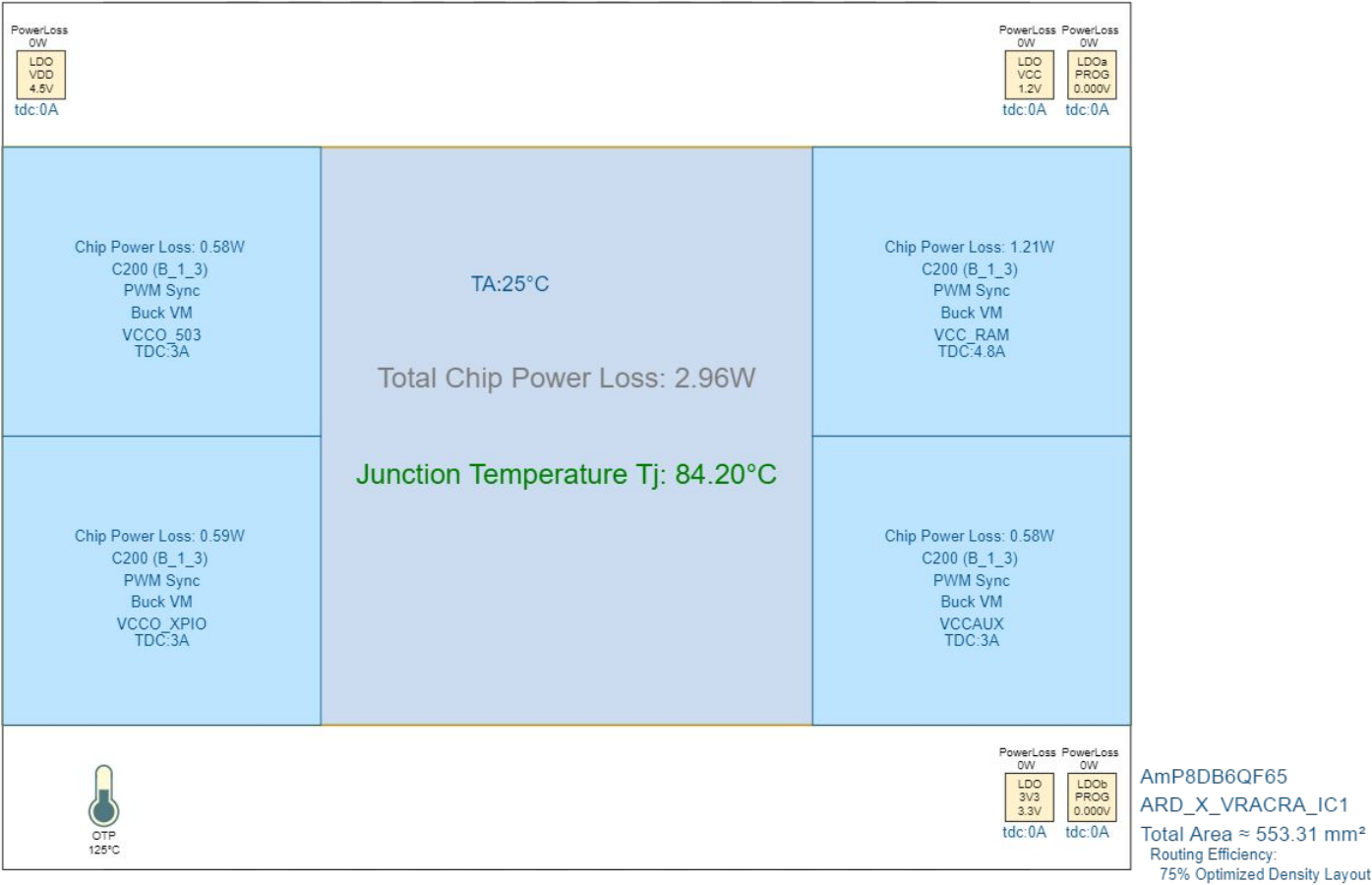


Mapping (WebAmP View) Design –IC2

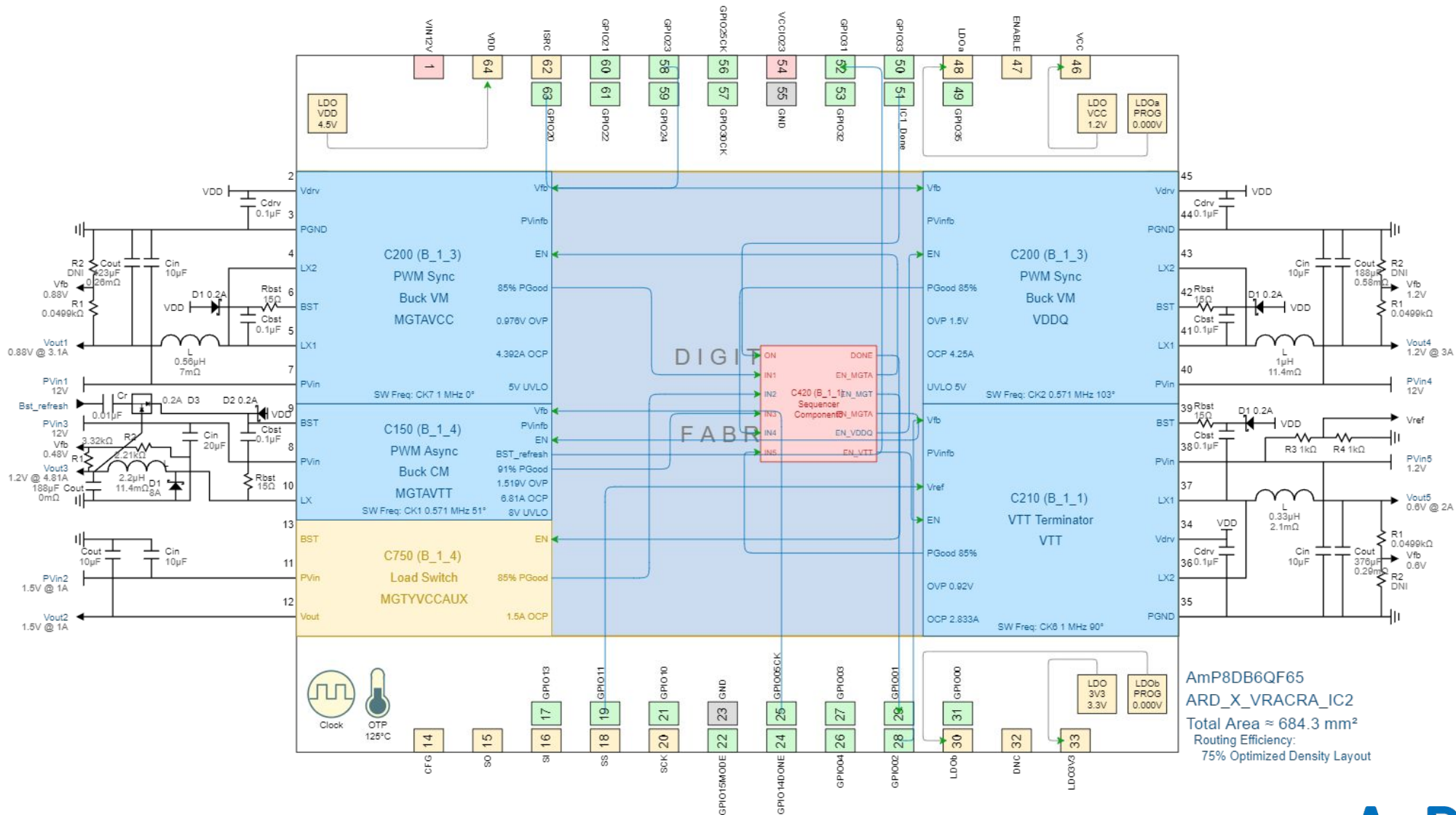

Mapping (Thermal View) –IC2

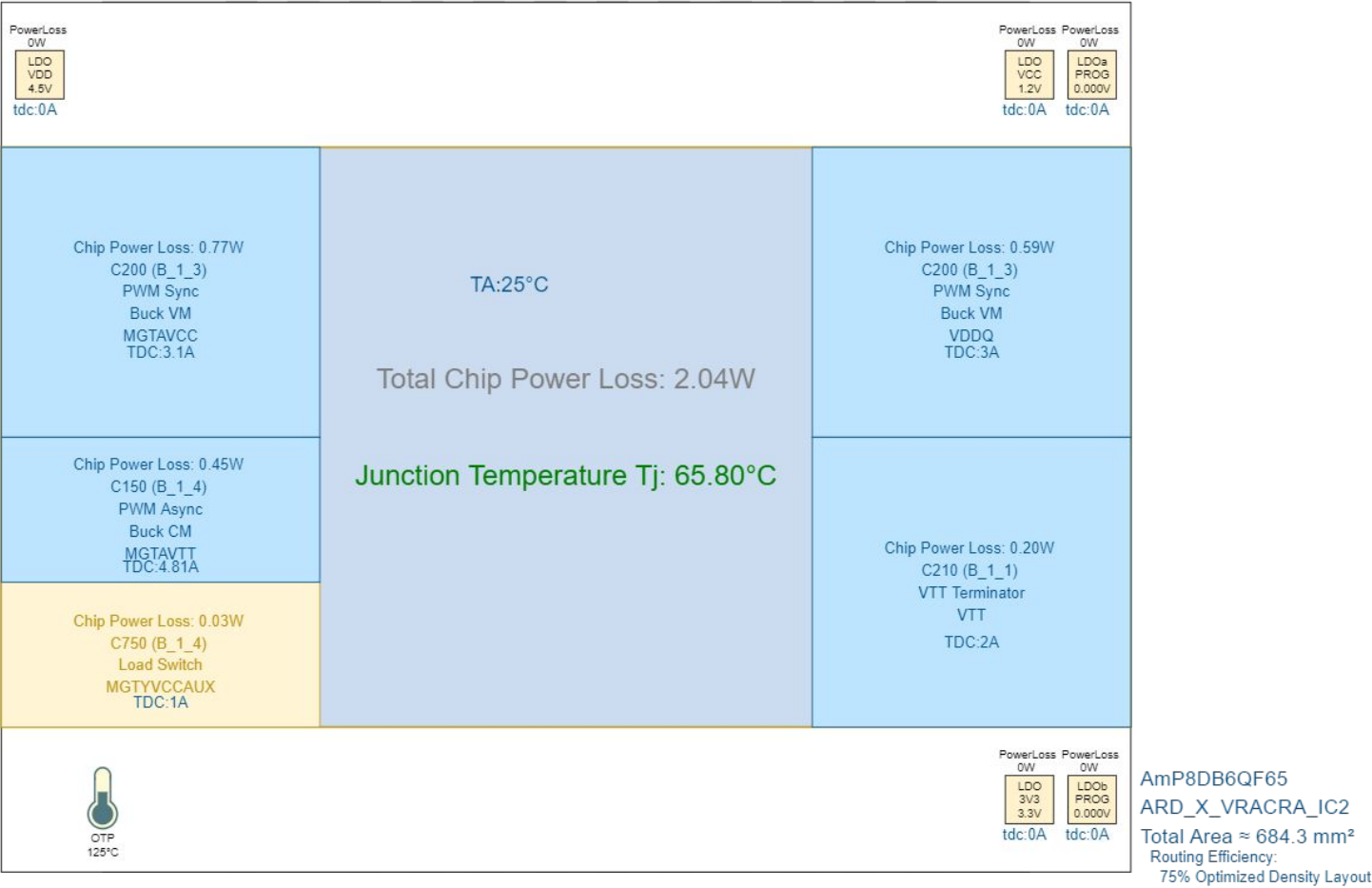

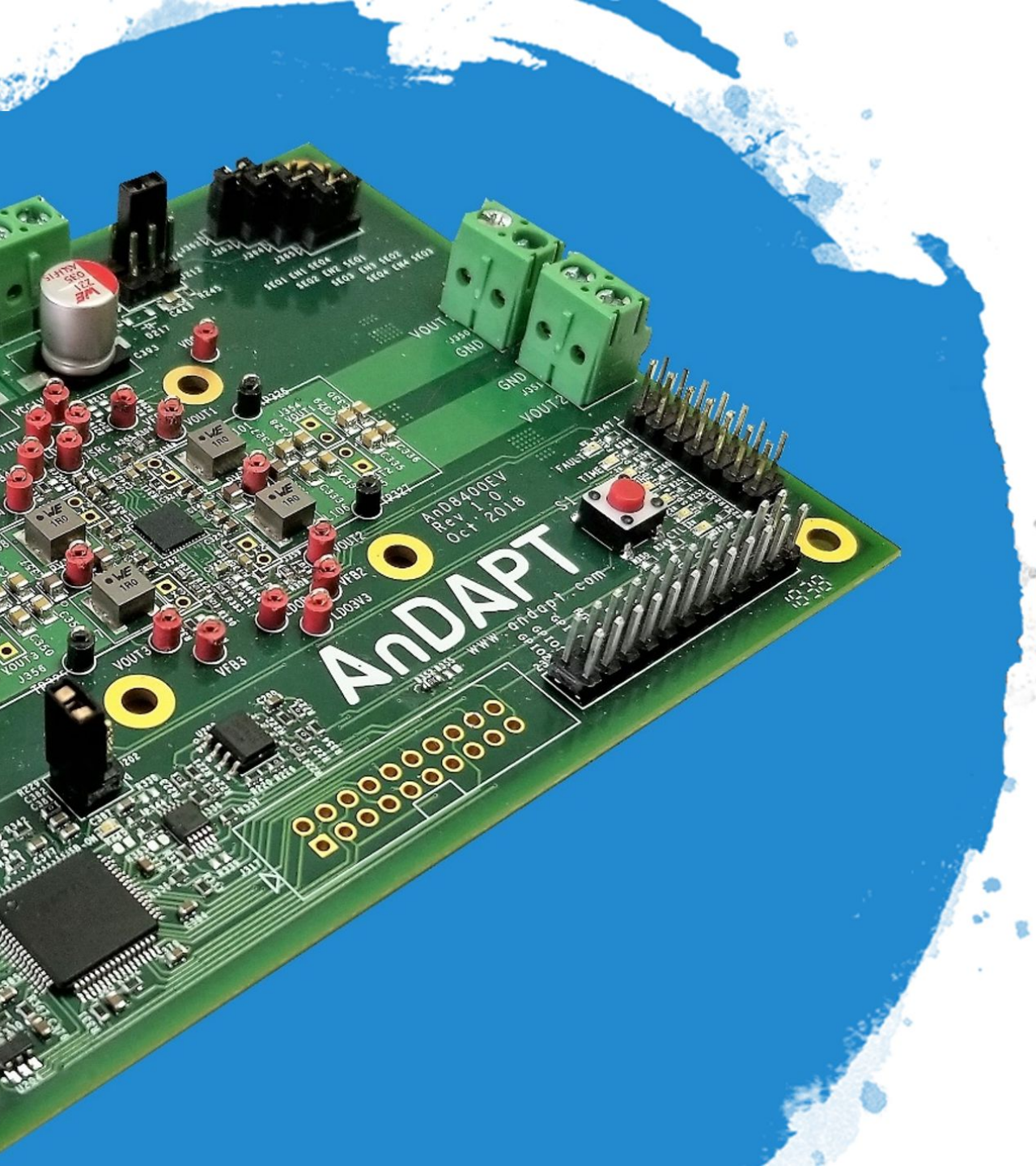

Test Data



Versal AI Core

VCCO_XPIO

1.5 V / 6 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1.1 \text{ } \mu\text{H}$, P/N Wurth 744314110
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

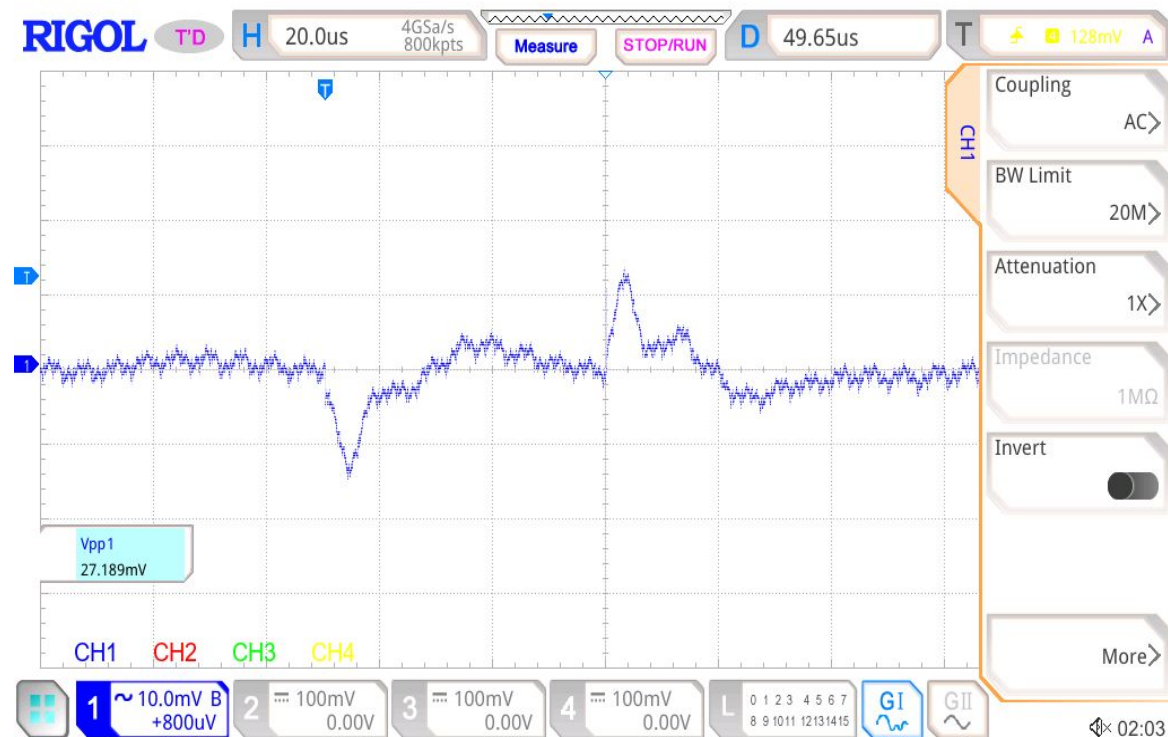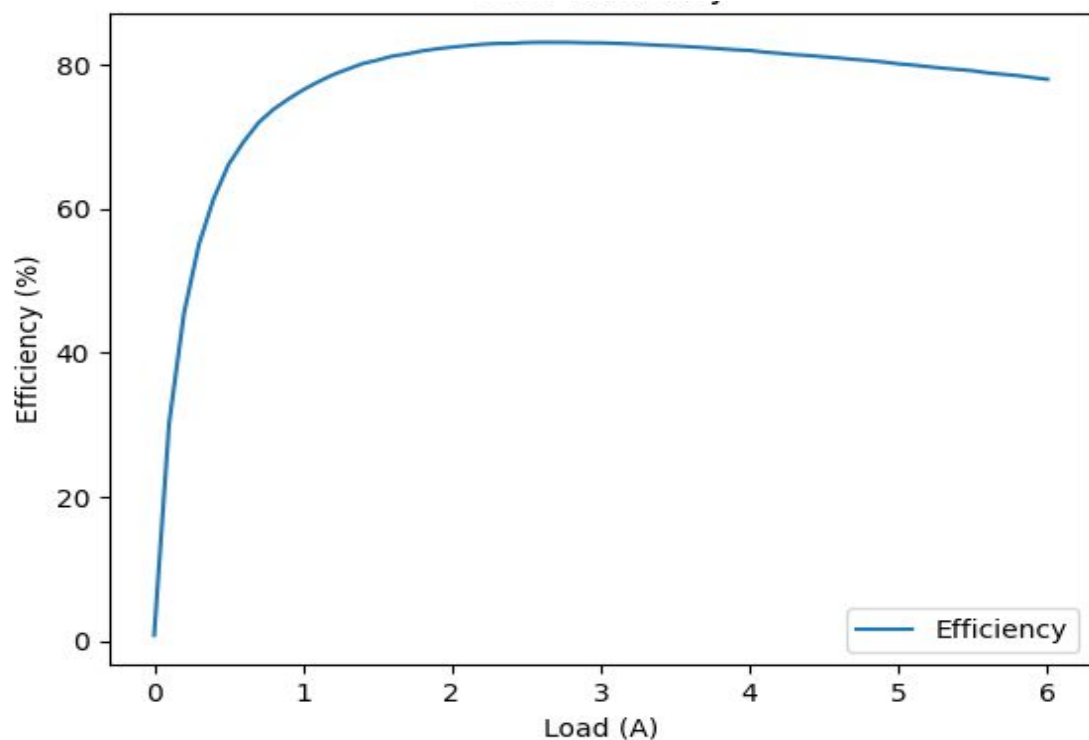


V_{out} = 1.5V
Transient 4.5 – 6 A@10 A/μs
V_{PP} = 27.18 mV
F_{sw} = 0.571 MHz
L = 1.1 μH, C = 4x47 μF

Ripple

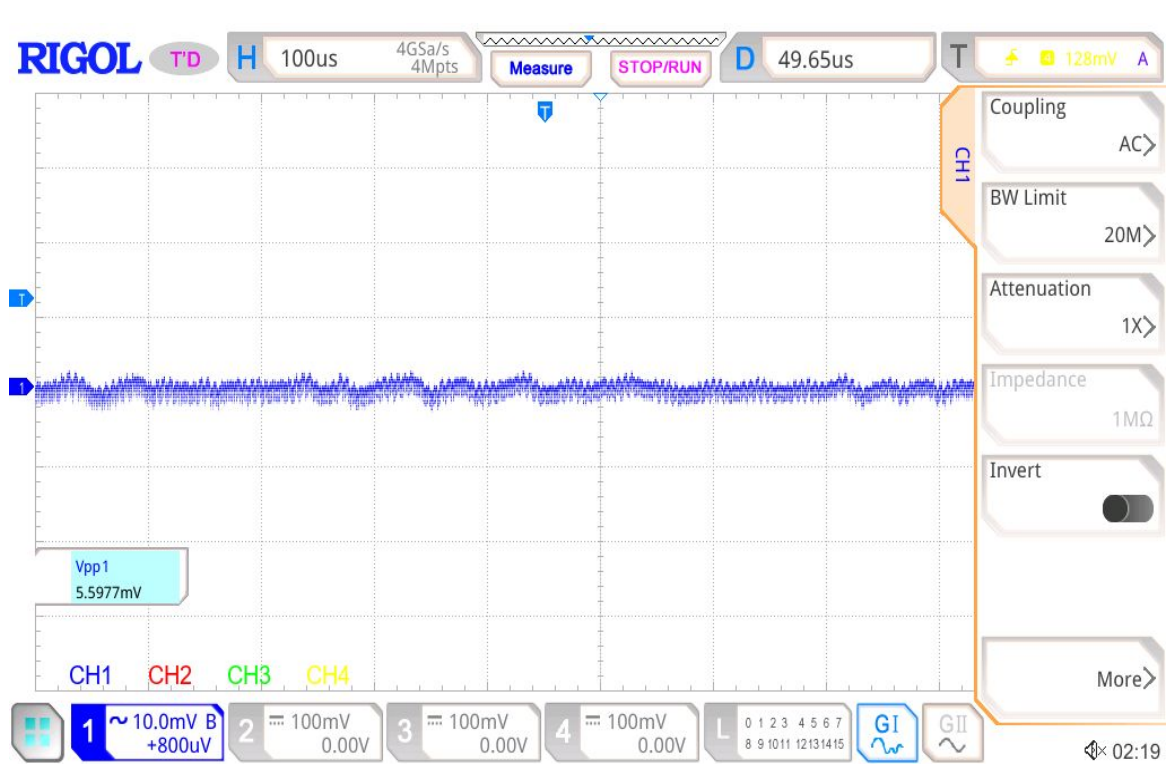

No Load
 $V_{PP} = 5.59 \text{ mV}$

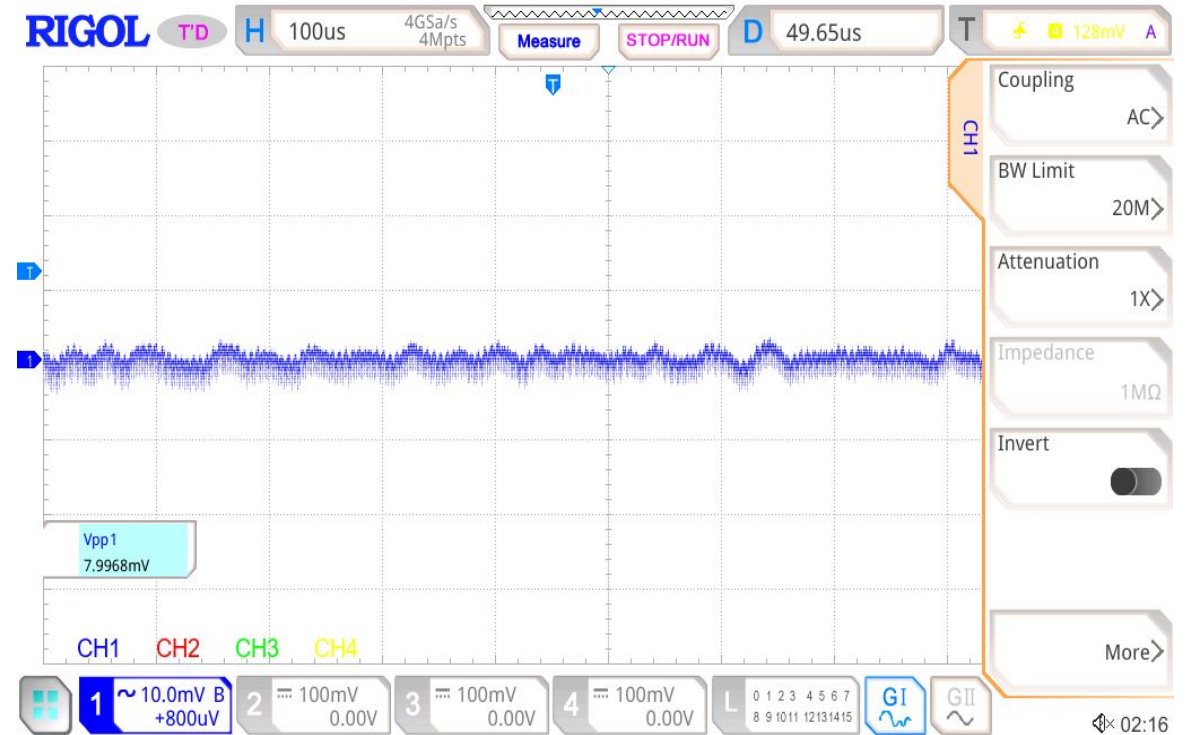

6 A Load
 $V_{PP} = 7.99 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

VCCO_503

1.5 V / 4 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \text{ } \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

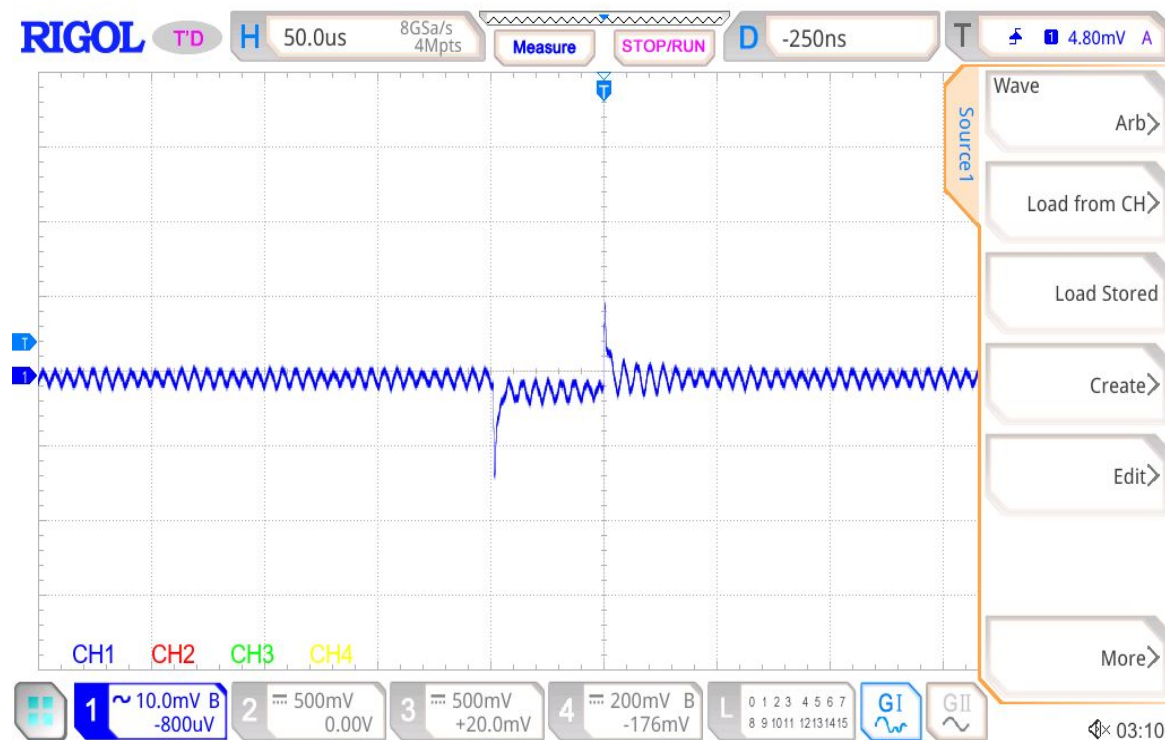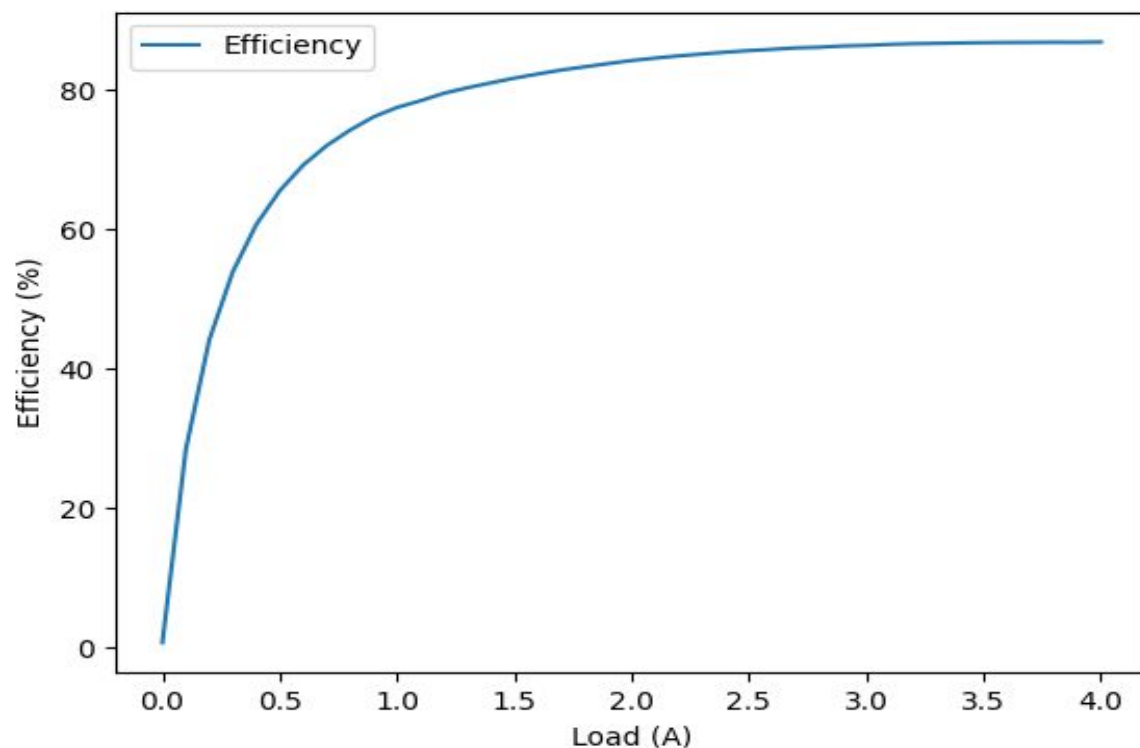


Vout = 1.5V
Transient 2.68A – 4A @ 10 A/μs
 $V_{PP} = 25 \text{ mV}$
 $F_{sw} = 0.571 \text{ MHz}$
 $L = 4.7 \text{ } \mu\text{H}$, $C = 1 \times 47 \text{ } \mu\text{F}$

Ripple

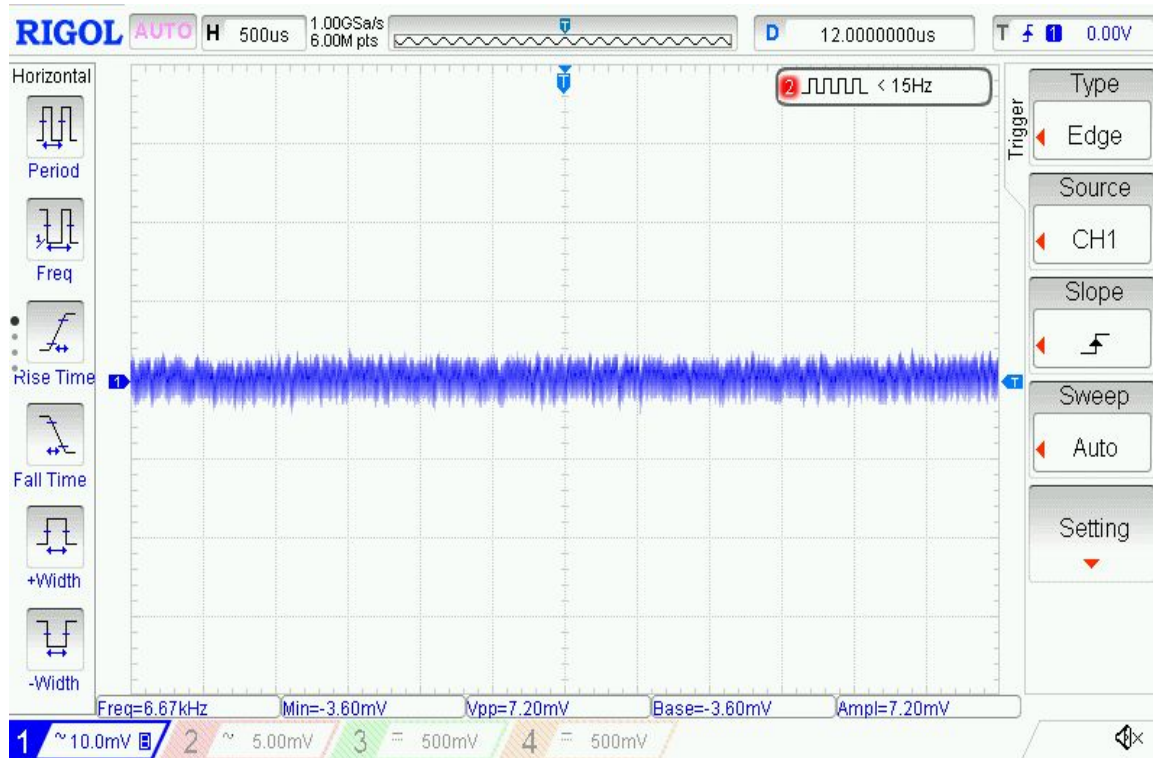

No Load
 $V_{PP} = 7.20 \text{ mV}$

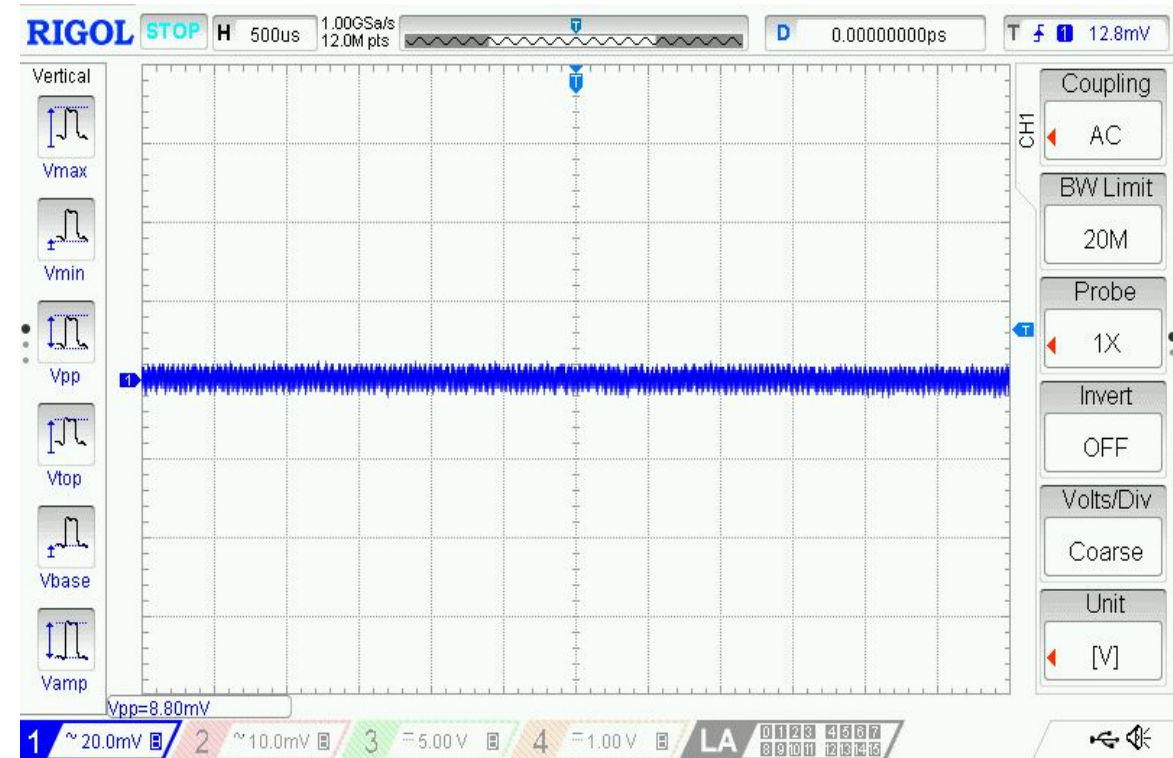

4 A Load
 $V_{PP} = 8.80 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

VCC_RAM

0.8 V / 5.8 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744383560056
- $C = 6 \times 47 \mu\text{F}$

Efficiency & Transient

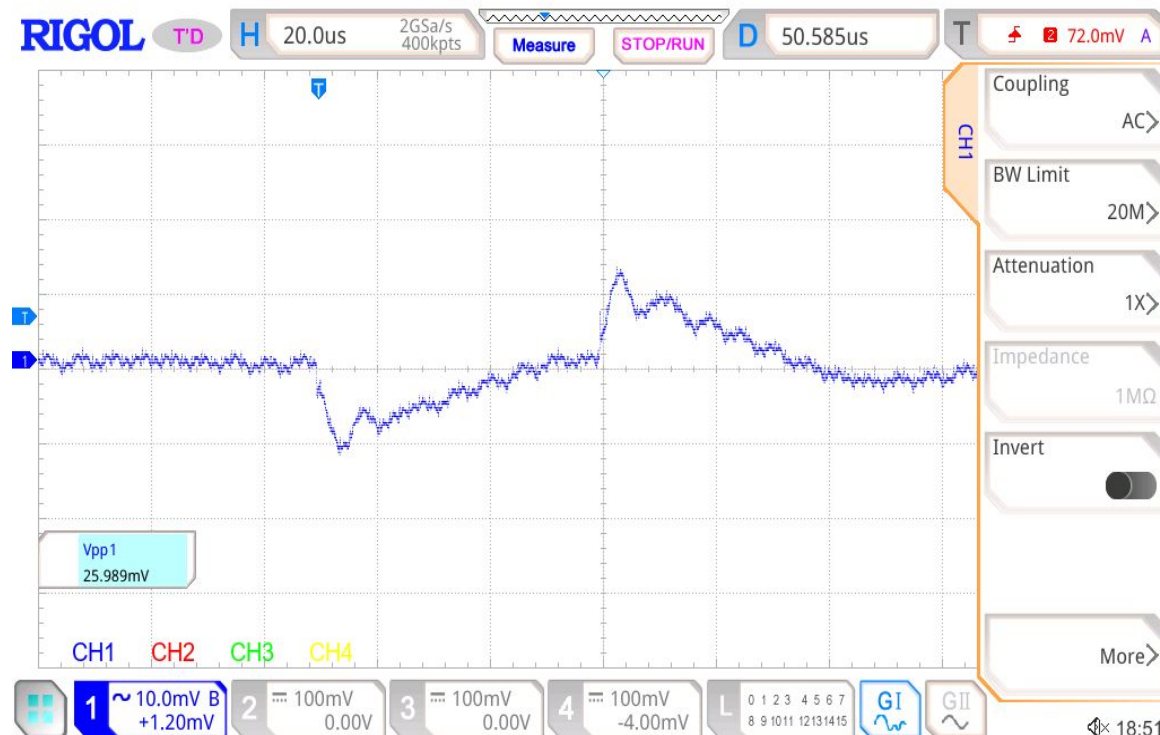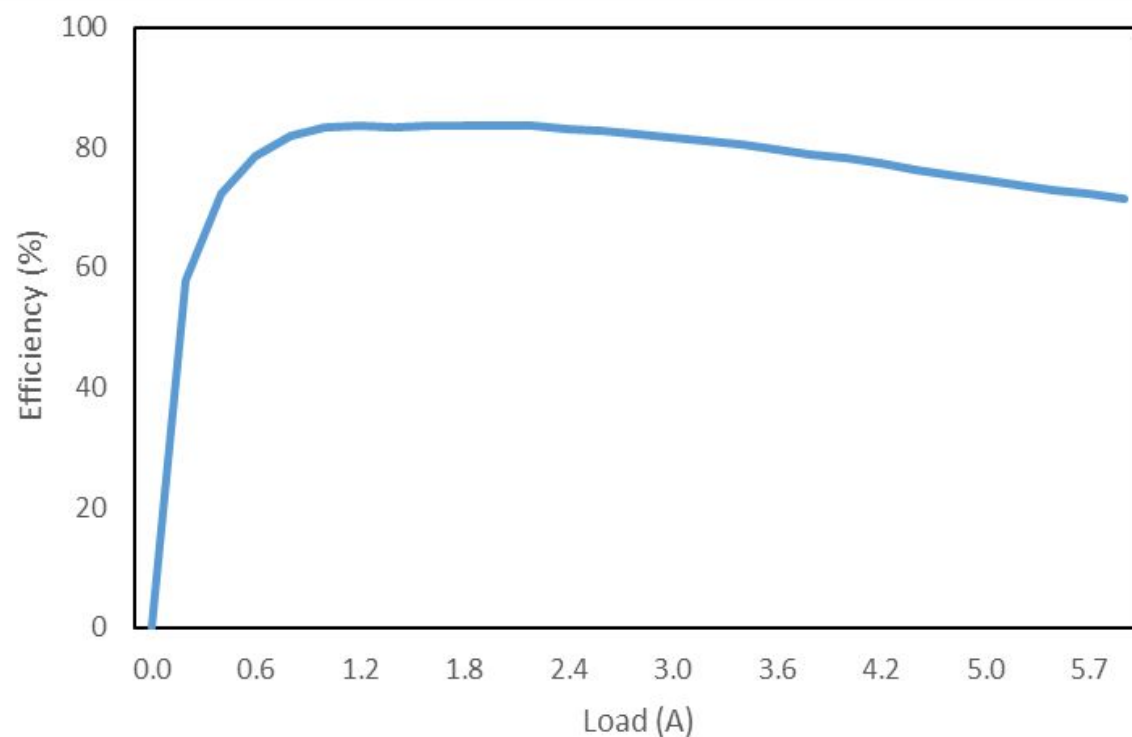


Vout = 0.8V
Transient 3.48A – 5.8A @ 10 A/μs
 $V_{PP} = 25.98 \text{ mV}$
Fsw = 0.571 MHz
L = 0.56 μH, C = 6x47 uF

Ripple

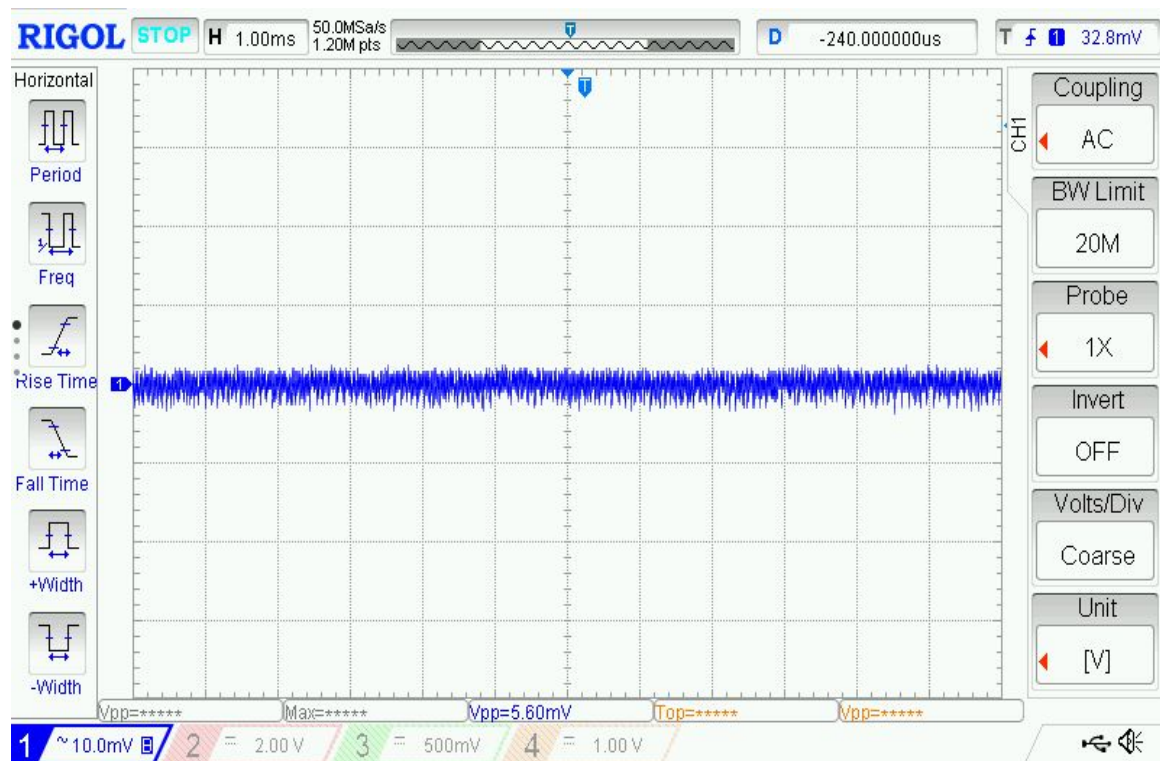

No Load
 $V_{PP} = 5.60 \text{ mV}$

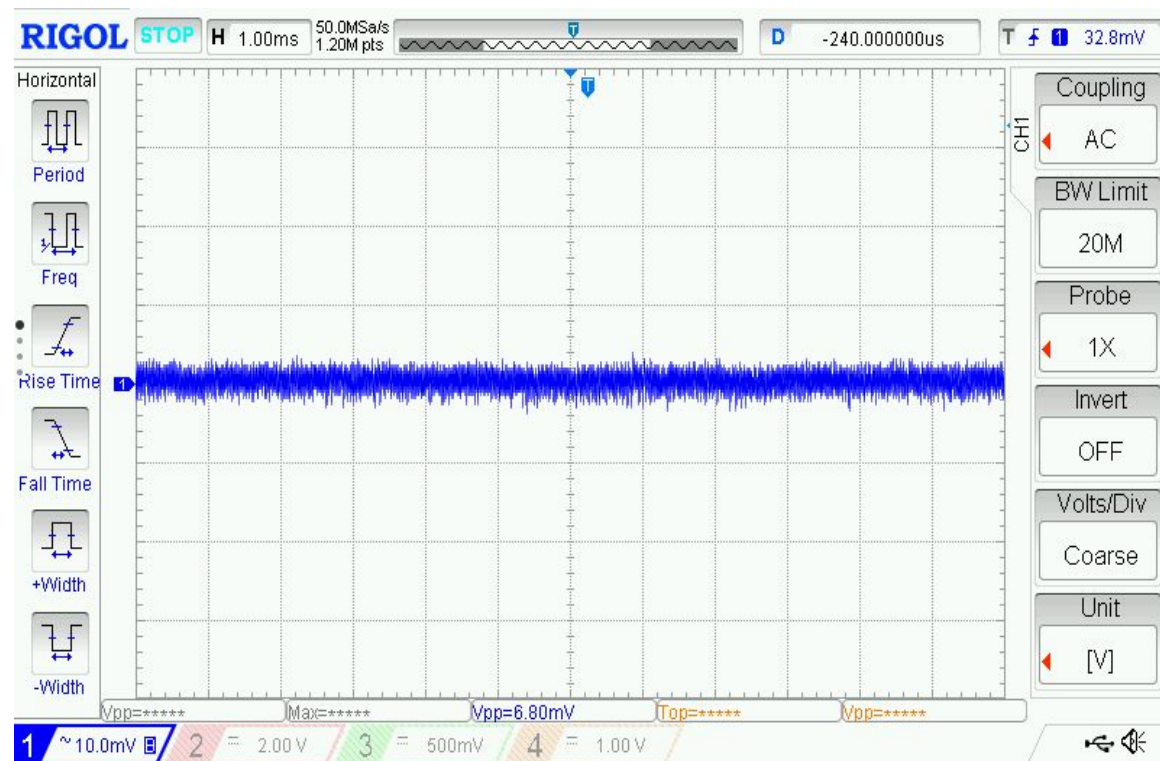

5.8 A Load
 $V_{PP} = 6.80 \text{ mV}$



$V_{out} = 0.8 \text{ V}$

VCCAUX

1.5 V / 4 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \text{ } \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

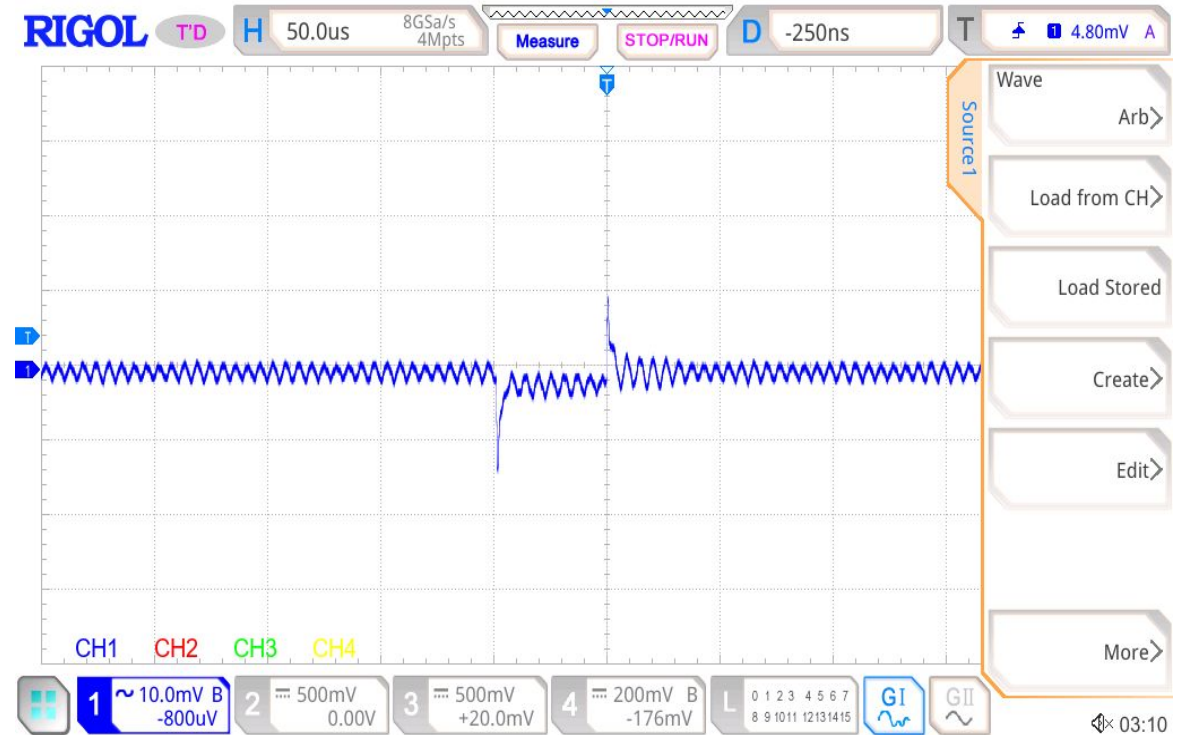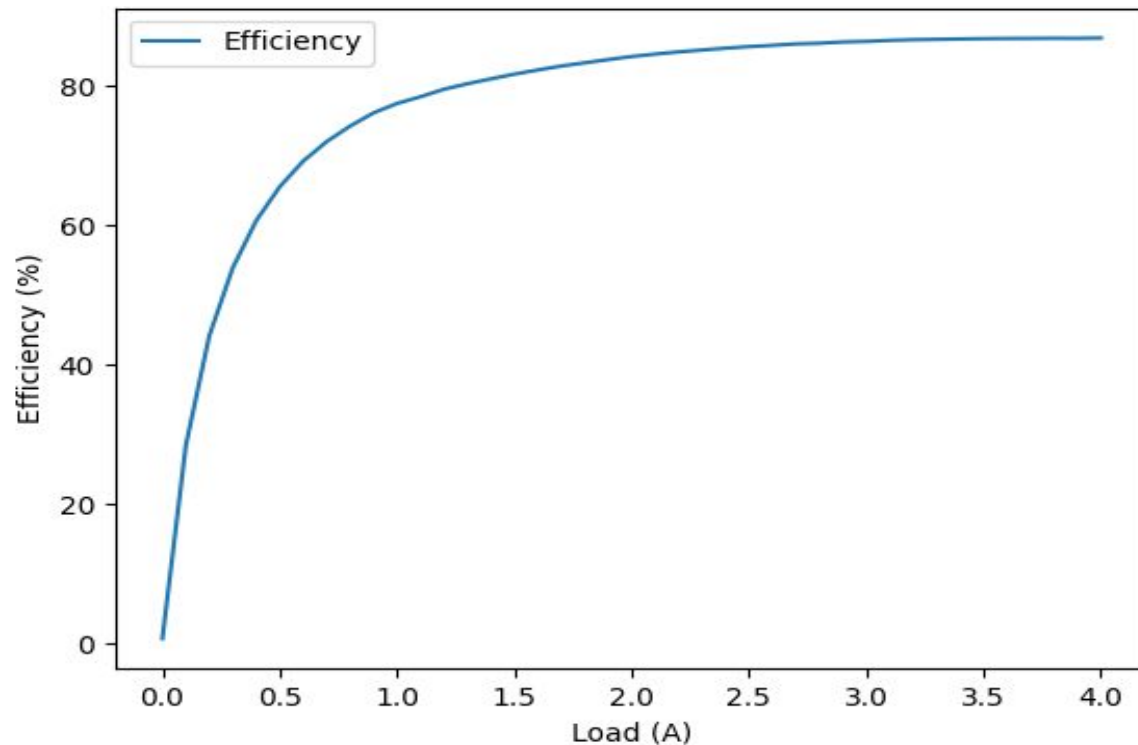


$V_{out} = 1.5V$
Transient 2.68A – 4A @ 10 A/ μ s
 $V_{pp} = 25\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 4.7\text{ }\mu\text{H}$, $C = 1x47\text{ }\mu\text{F}$

Ripple

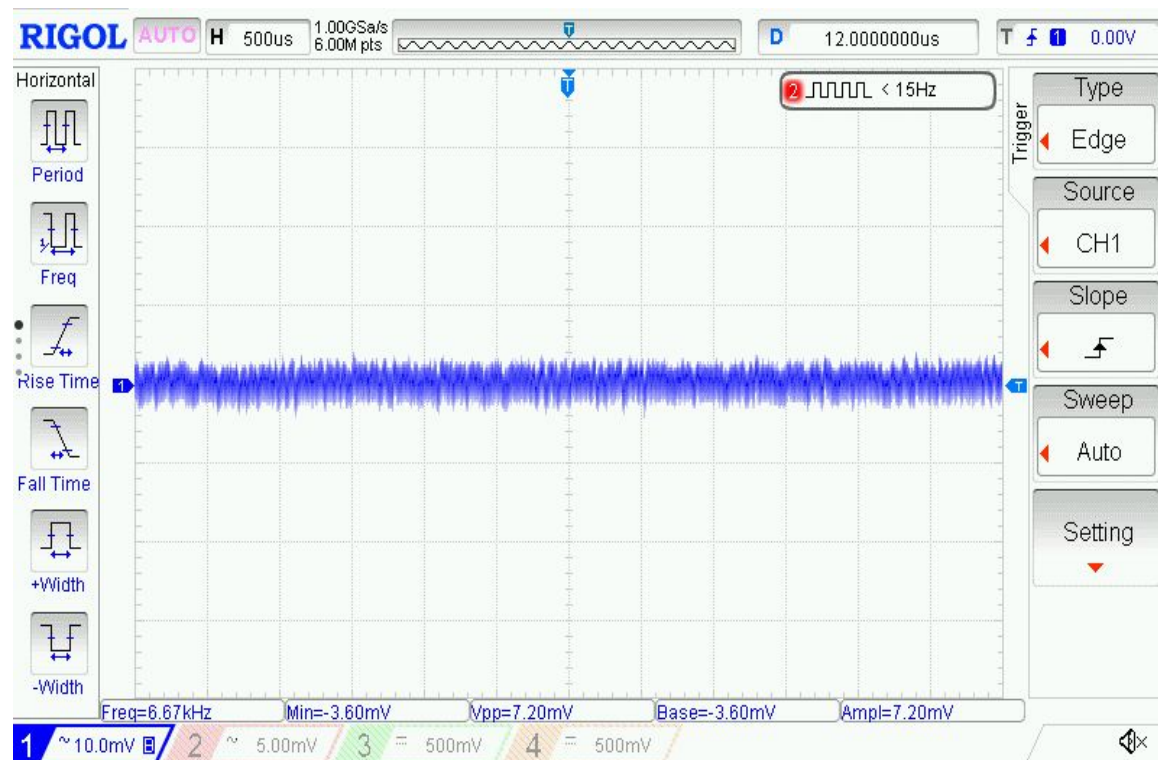

No Load
 $V_{PP} = 7.20 \text{ mV}$

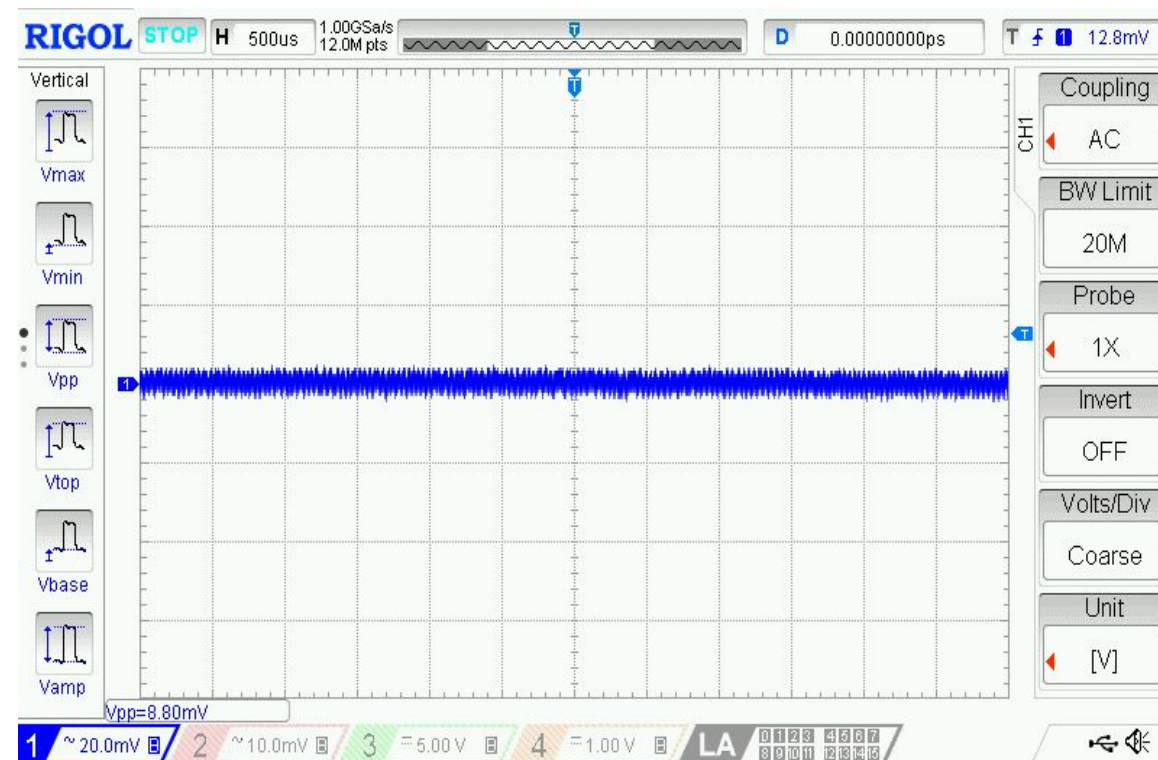



4 A Load
 $V_{PP} = 8.80 \text{ mV}$

MGTAVCC

0.88 V / 3.1 A


- C200 (Synchronous Buck)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744383560056
- $C = 9 \times 47 \mu\text{F}$

Efficiency & Transient

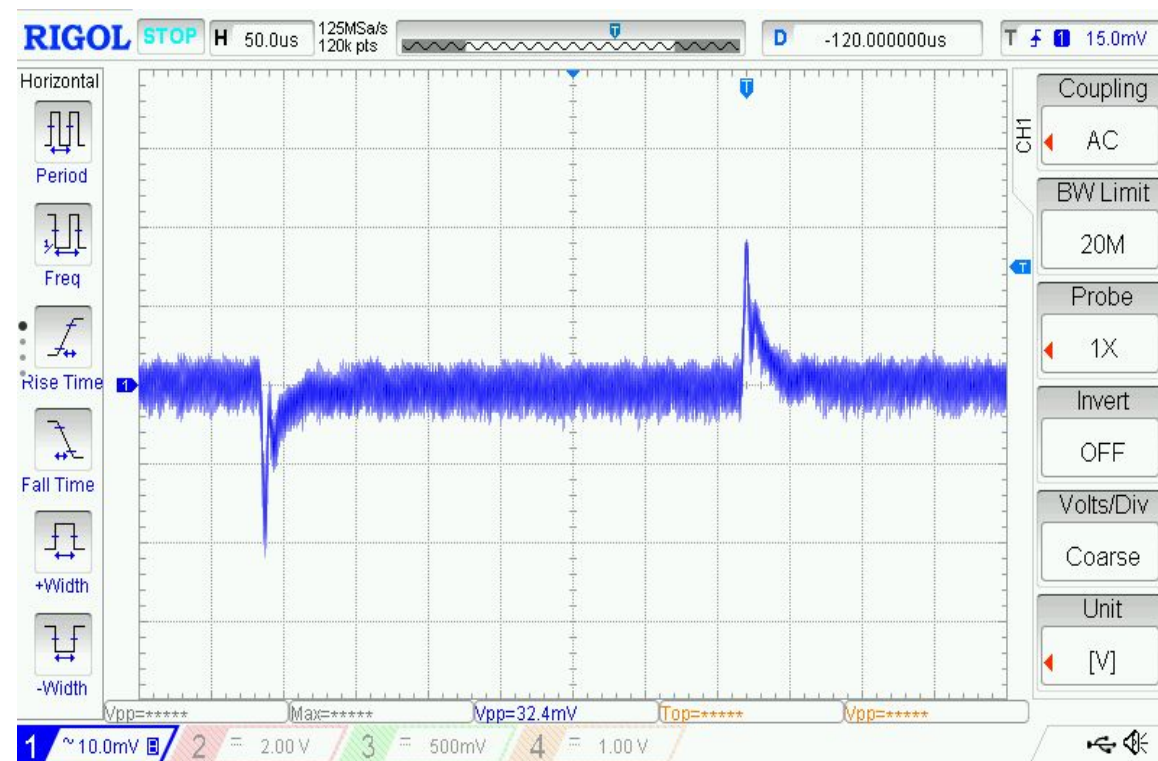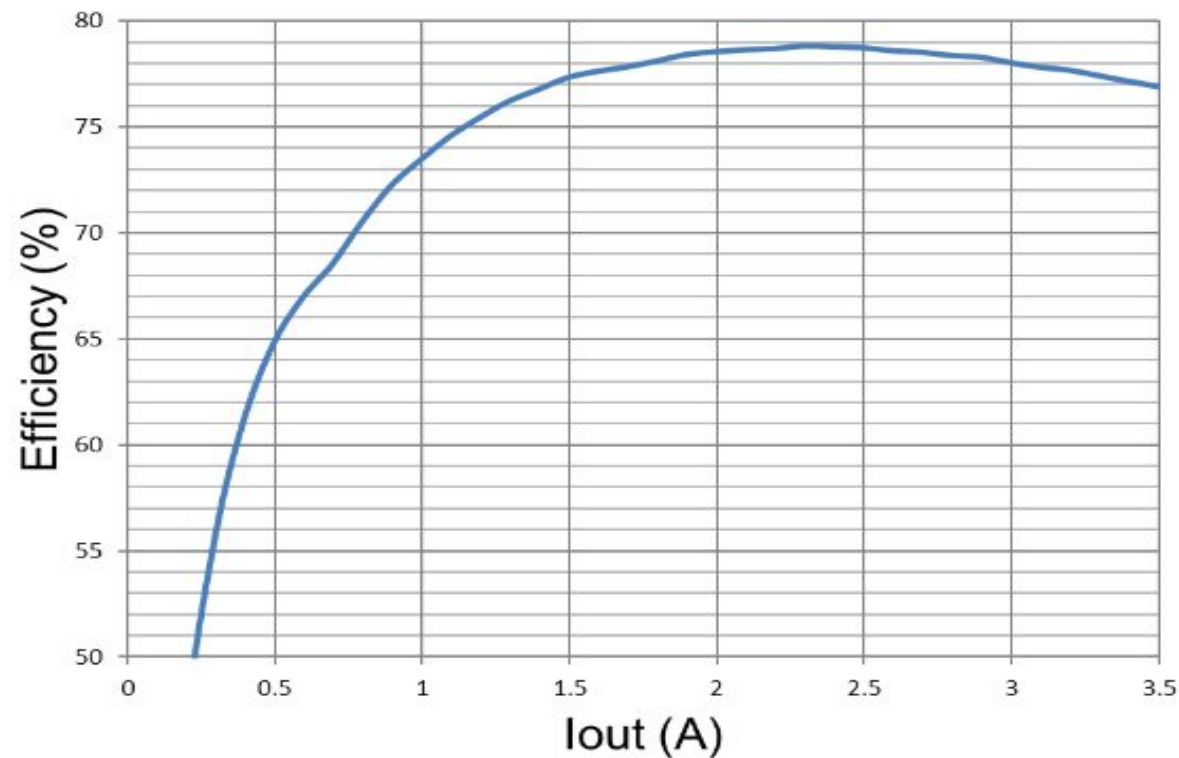


$V_{out} = 0.88 \text{ V}$
Transient 2.625A – 3.5A @ 10 A/ μ s
 $V_{pp} = 32.4 \text{ mV}$
 $F_{sw} = 0.571 \text{ MHz}$
 $L = 0.56 \text{ } \mu\text{H}$, $C = 9 \times 47 \text{ } \mu\text{F}$

Ripple

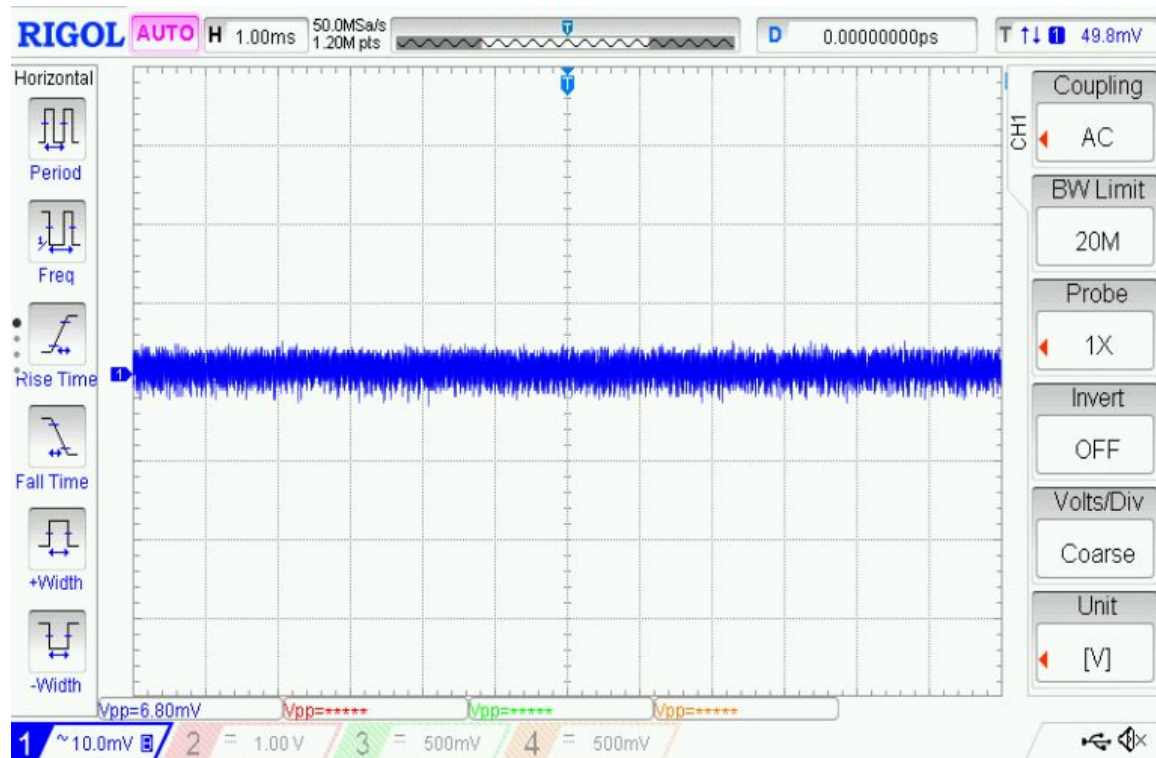

No Load
 $V_{PP} = 6.80 \text{ mV}$

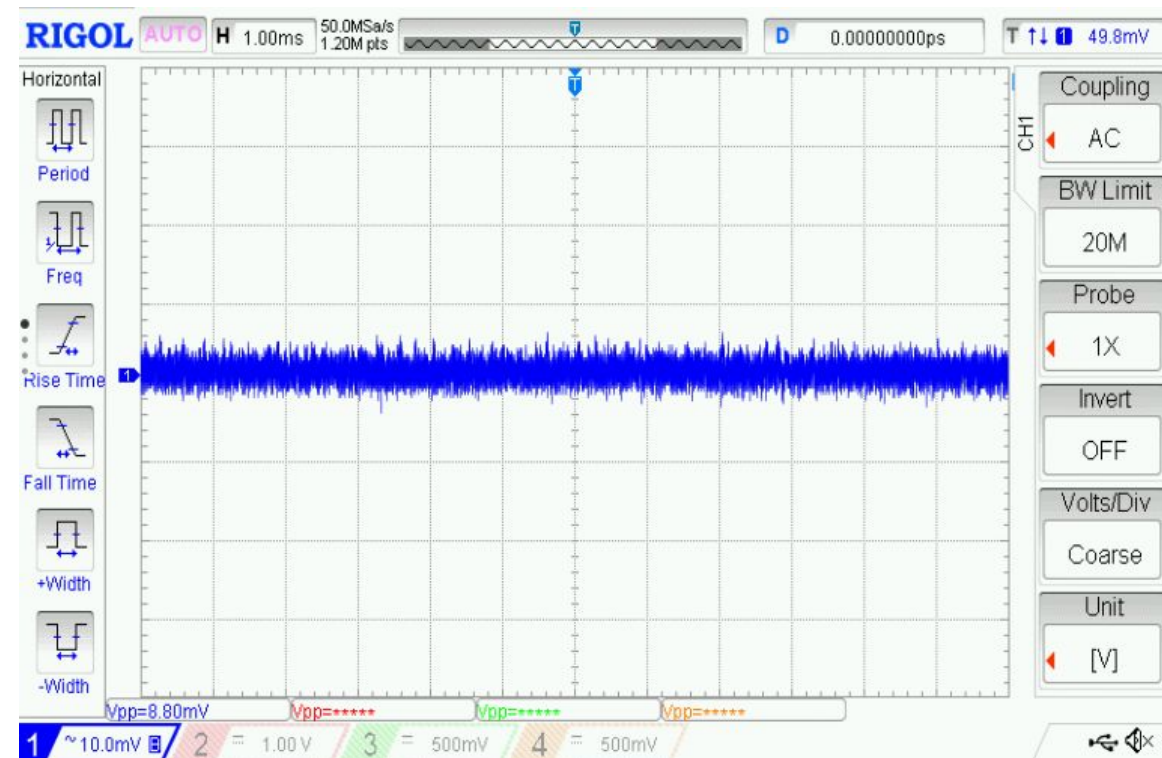

3.1 A Load
 $V_{PP} = 8.80 \text{ mV}$

$V_{out} = 0.88 \text{ V}$

MGTYVCCAUX

1.5 V / 0.29 A



- C750 (Load switch)

MGTAVTT

1.2 V / 4.81 A


- C150 (Asynchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 2.2 \text{ } \mu\text{H}$, P/N Wurth 744311220
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

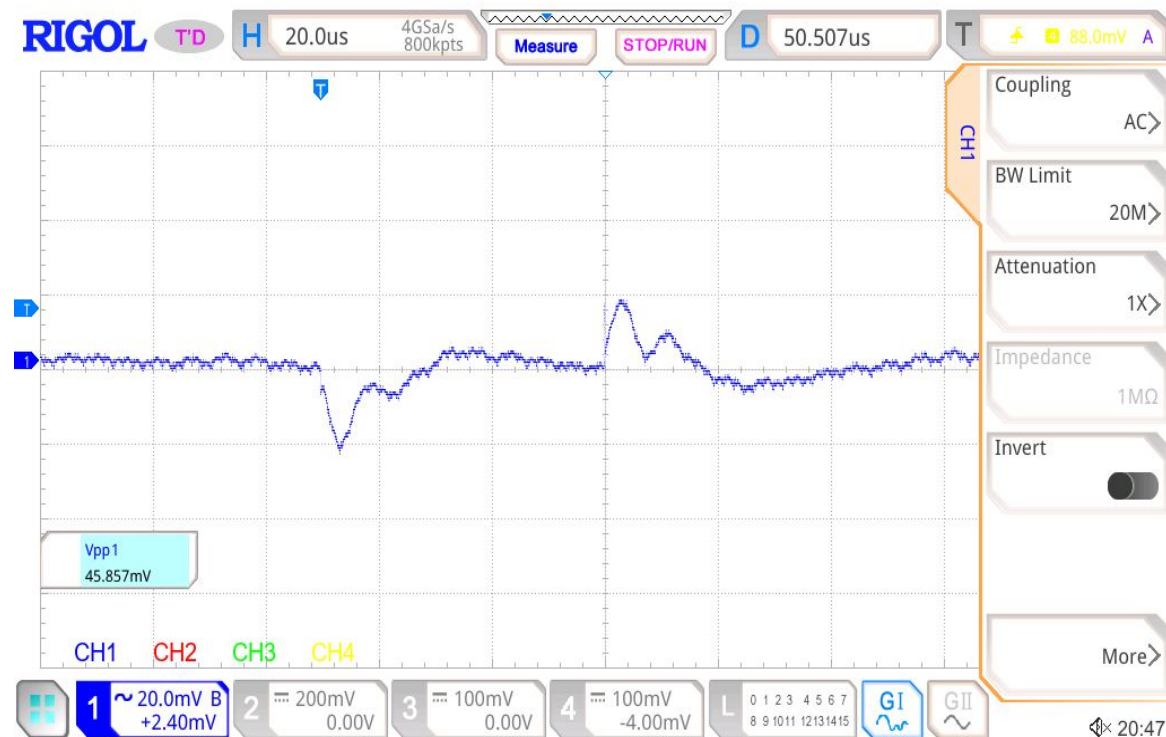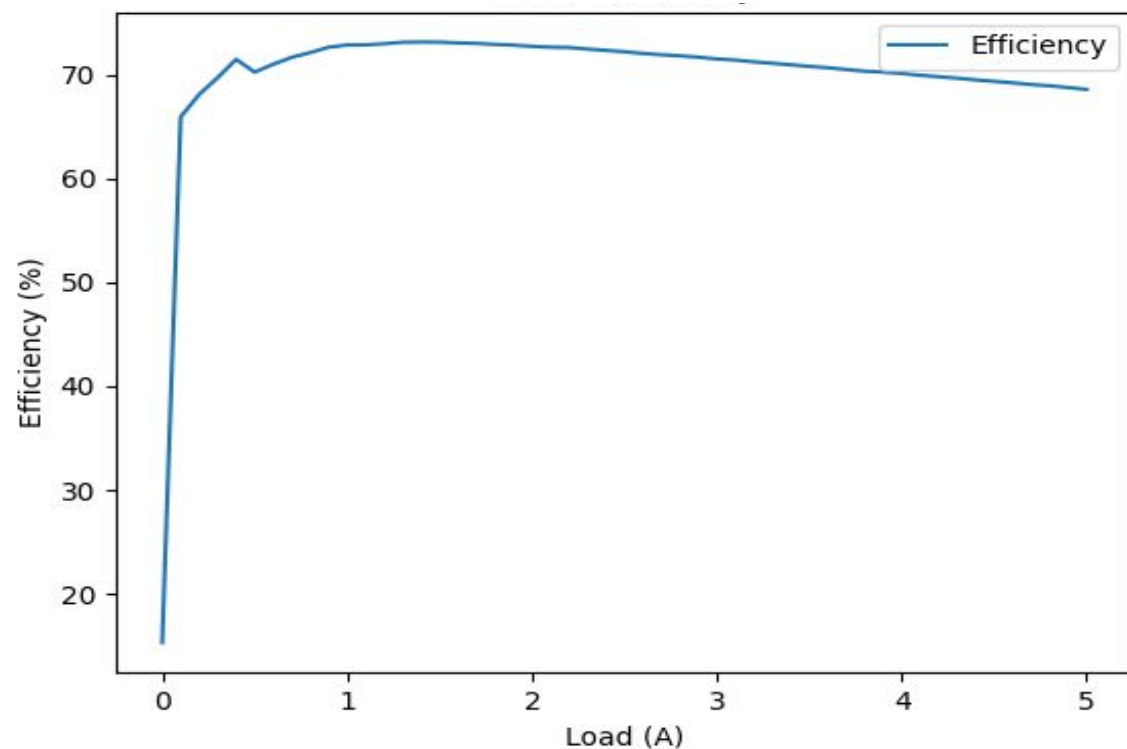


$V_{out} = 1.2\text{ V}$
 Transient 3.61 – 4.81A @ 10 A/ μ s
 $V_{PP} = 45.85\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 2.2\text{ }\mu\text{H}$, $C = 4 \times 47\text{ }\mu\text{F}$

Ripple

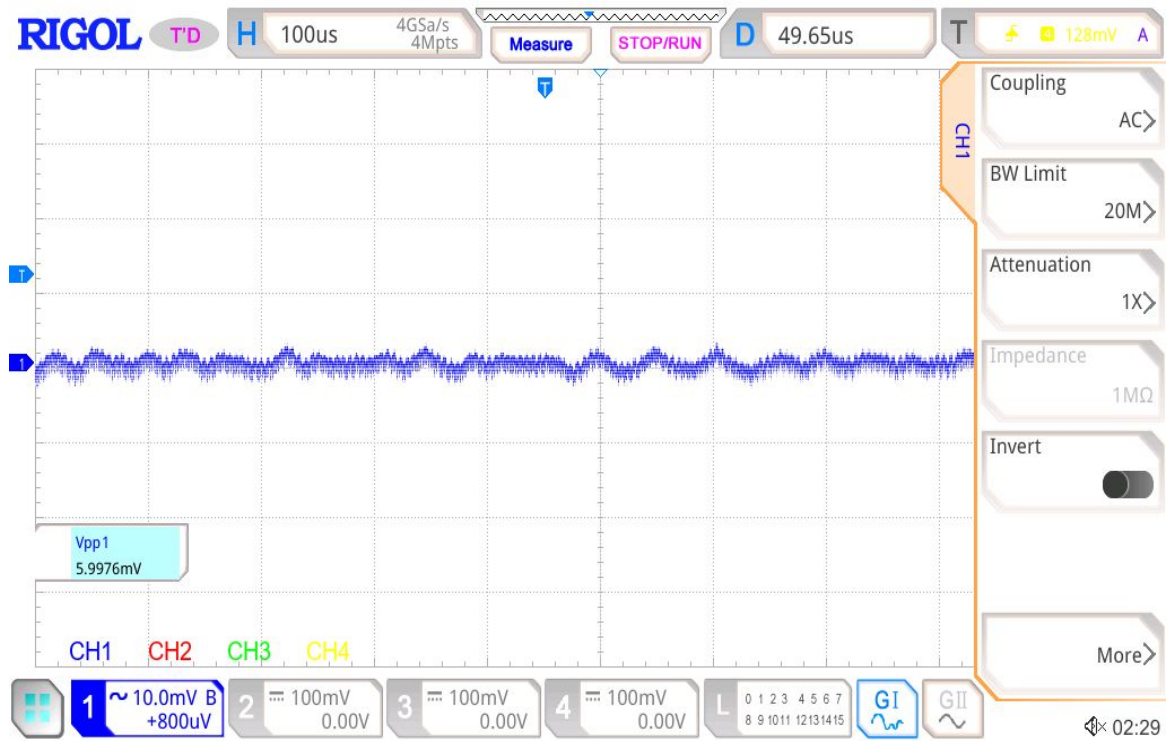

No Load
 $V_{PP} = 5.99 \text{ mV}$

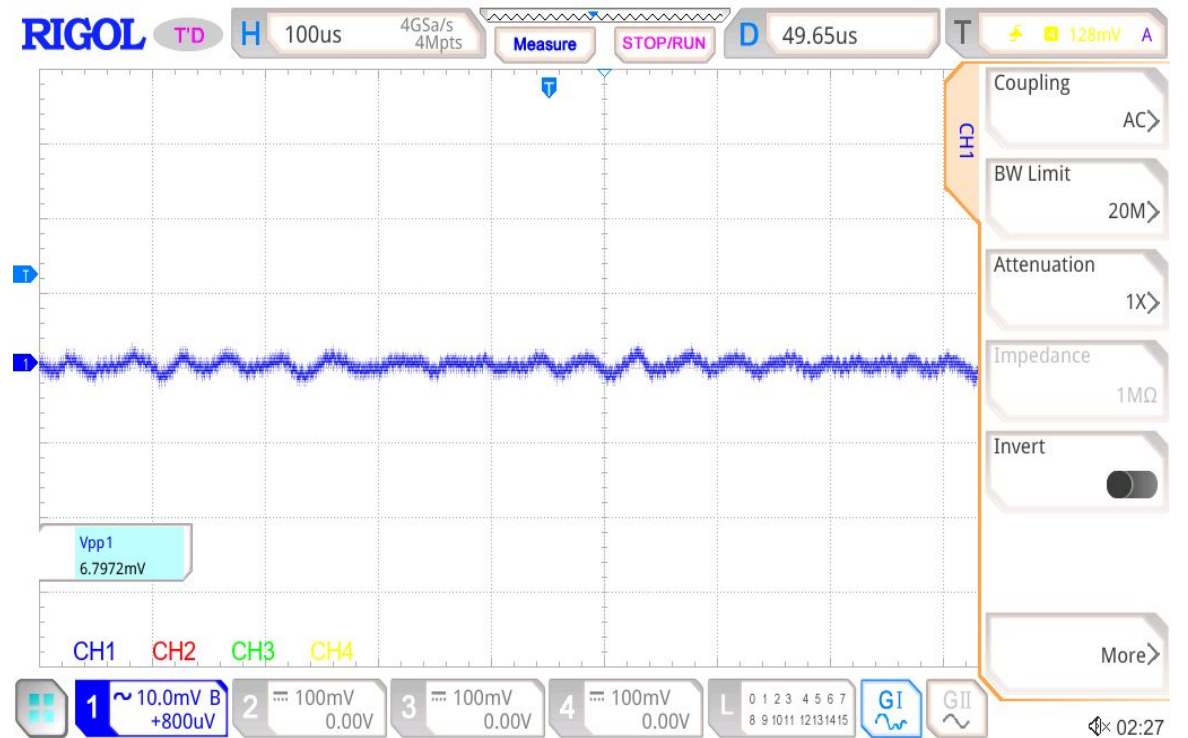

4.81 A Load
 $V_{PP} = 6.79 \text{ mV}$



$V_{out} = 1.2 \text{ V}$

VDDQ

1.2 V / 3 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1 \text{ } \mu\text{H}$, P/N Wurth 74438366010
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

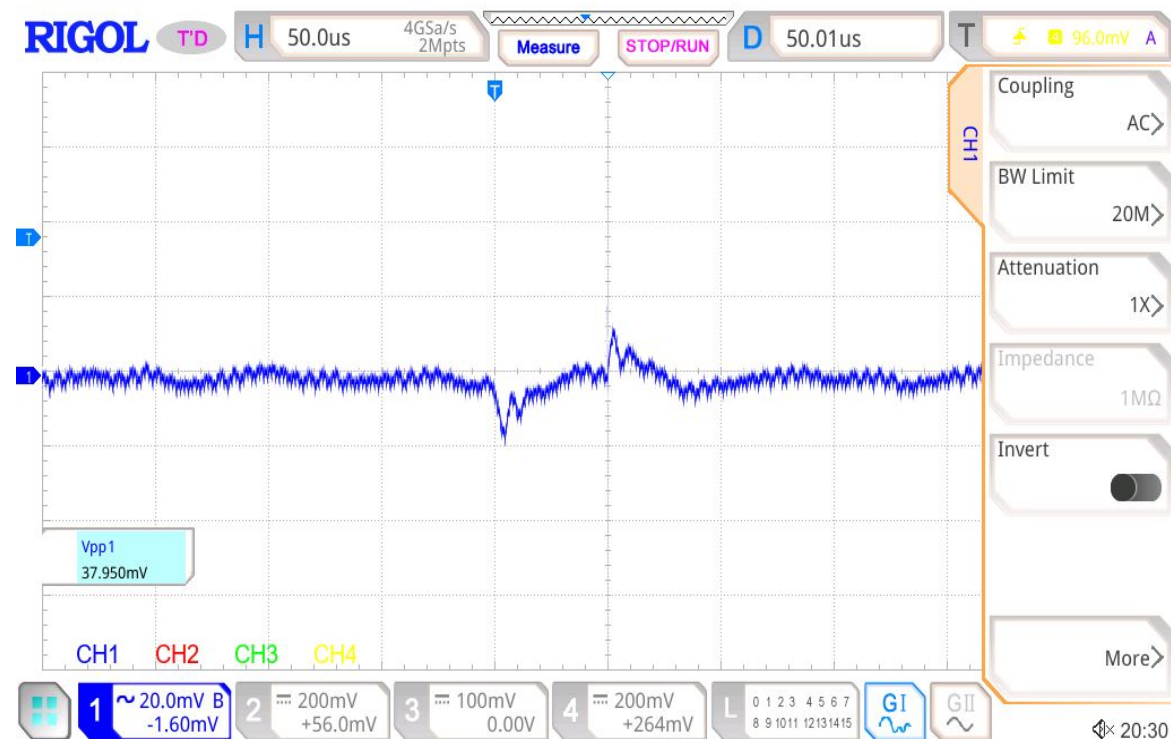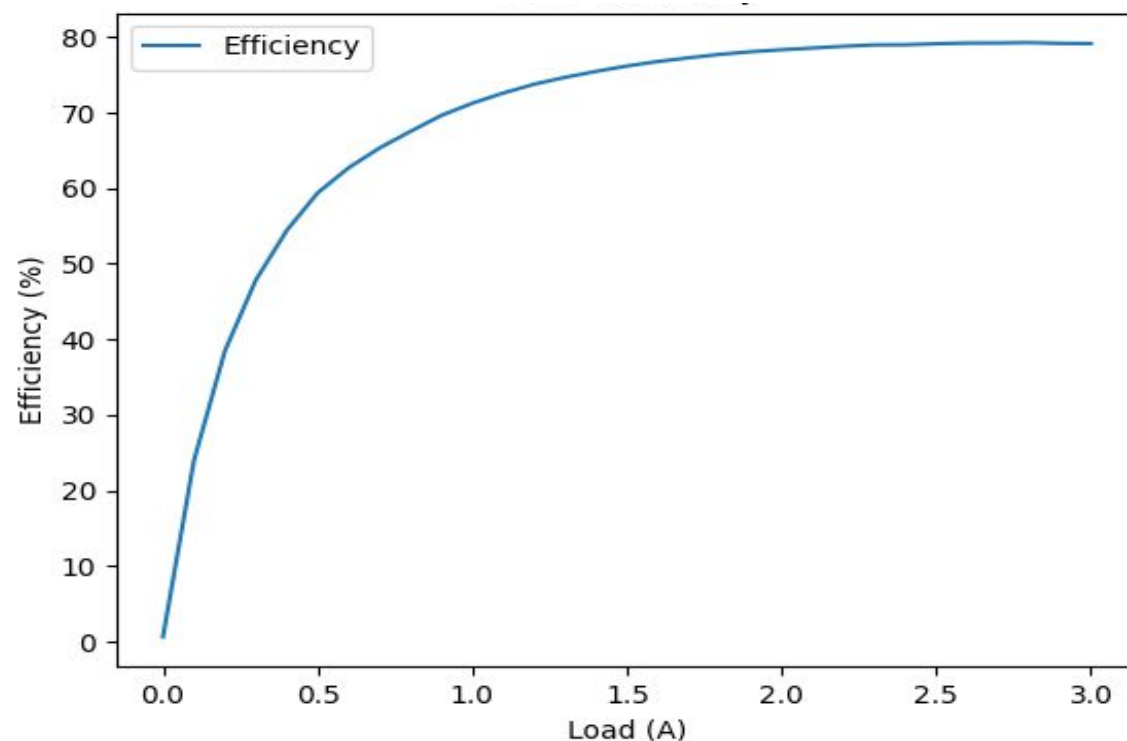


$V_{out} = 1.2\text{ V}$
Transient 0.3 – 3A @ 10 A/ μ s
 $V_{pp} = 37.95\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 1\text{ }\mu\text{H}$, $C = 4 \times 47\text{ }\mu\text{F}$

Ripple

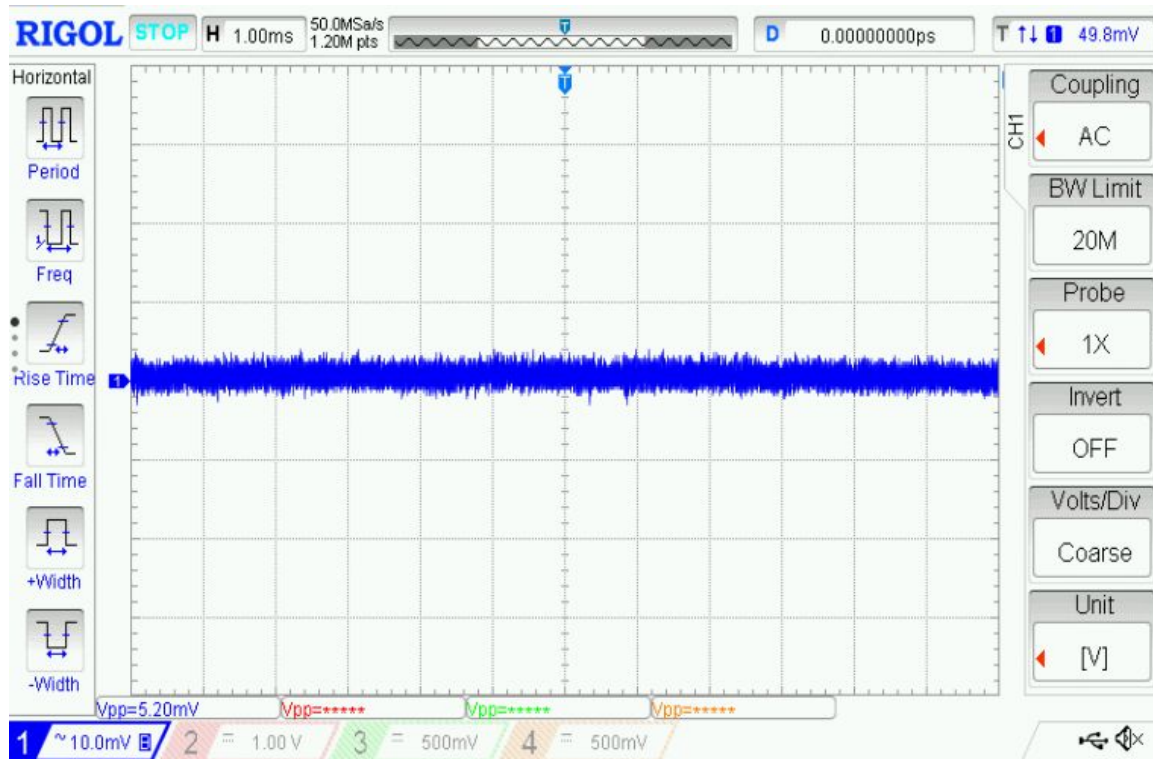

No Load
 $V_{PP} = 5.20 \text{ mV}$

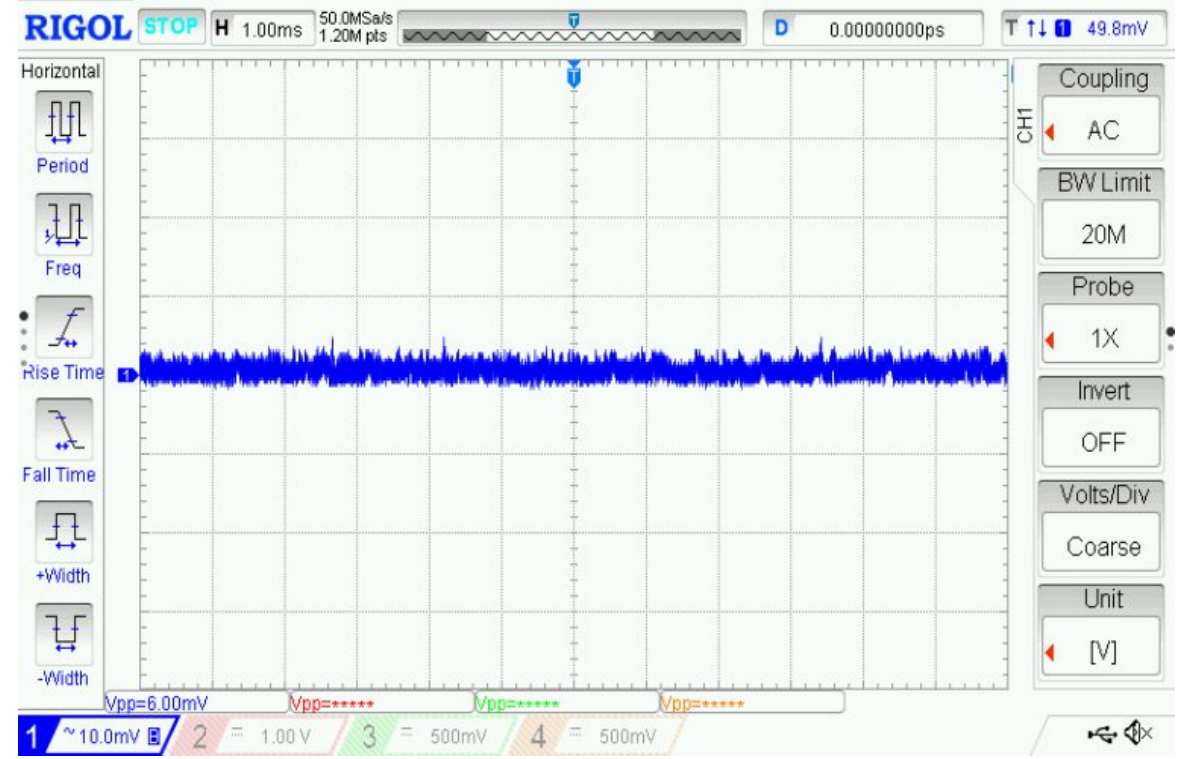

3 A Load
 $V_{PP} = 6.00 \text{ mV}$


$V_{out} = 1.2 \text{ V}$

VTT


0.6 V / 2 A

- C210 (VTT Terminator)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.33 \text{ } \mu\text{H}$, P/N Wurth 744393440033
- $C = 8 \times 47 \text{ } \mu\text{F}$


Efficiency & Transient

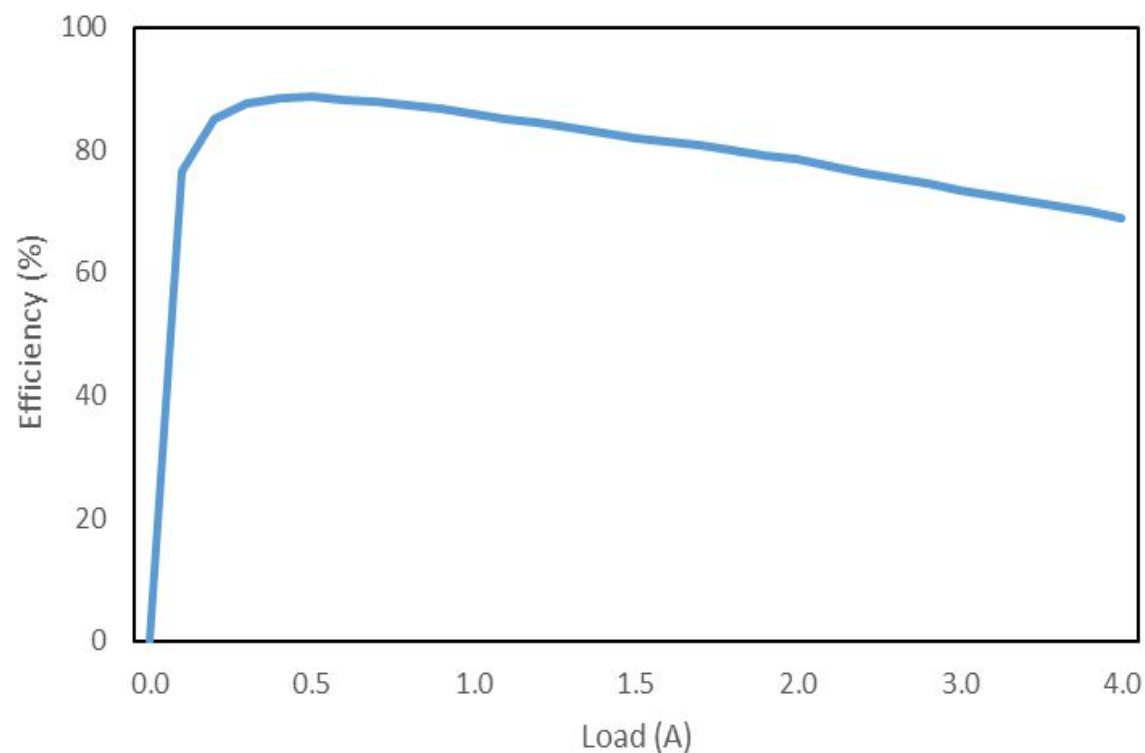

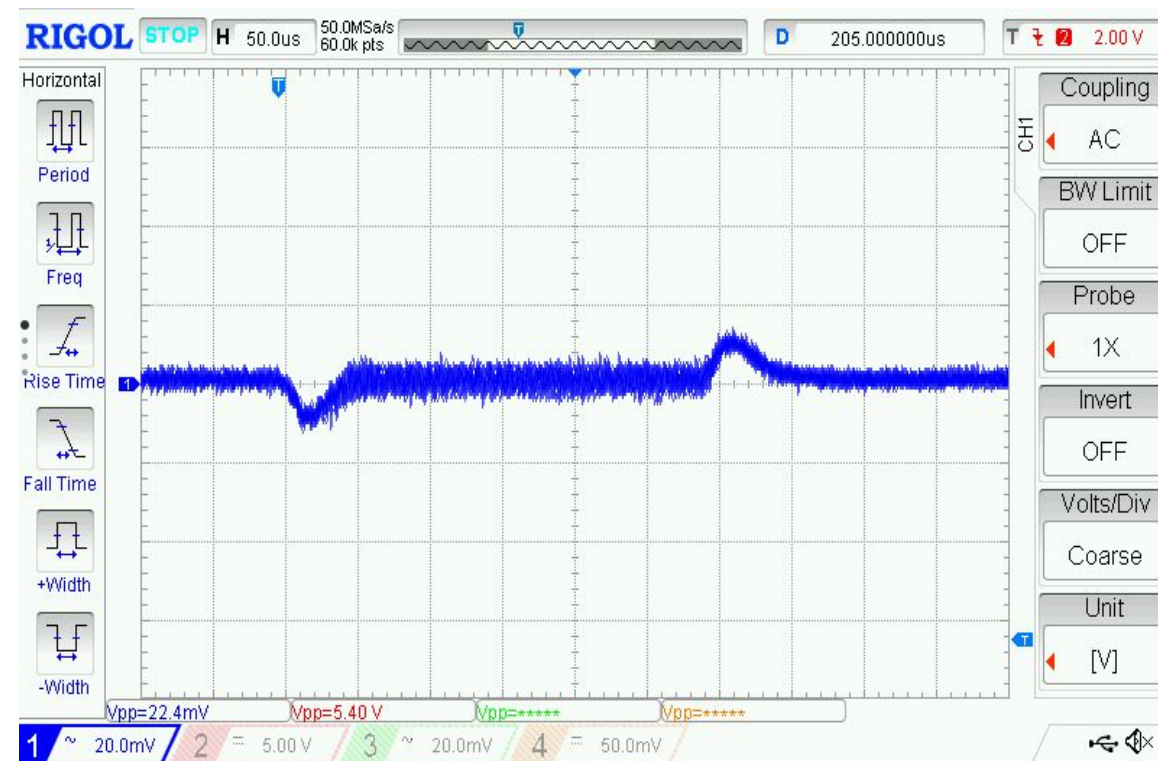
Vout = 0.6V
Transient 3 – 4A @ 10 A/ μ s
 $V_{PP} = 22.4$ mV
Fsw = 1 MHz
L = 0.33 μ H, C = 8x47 μ F



Ripple

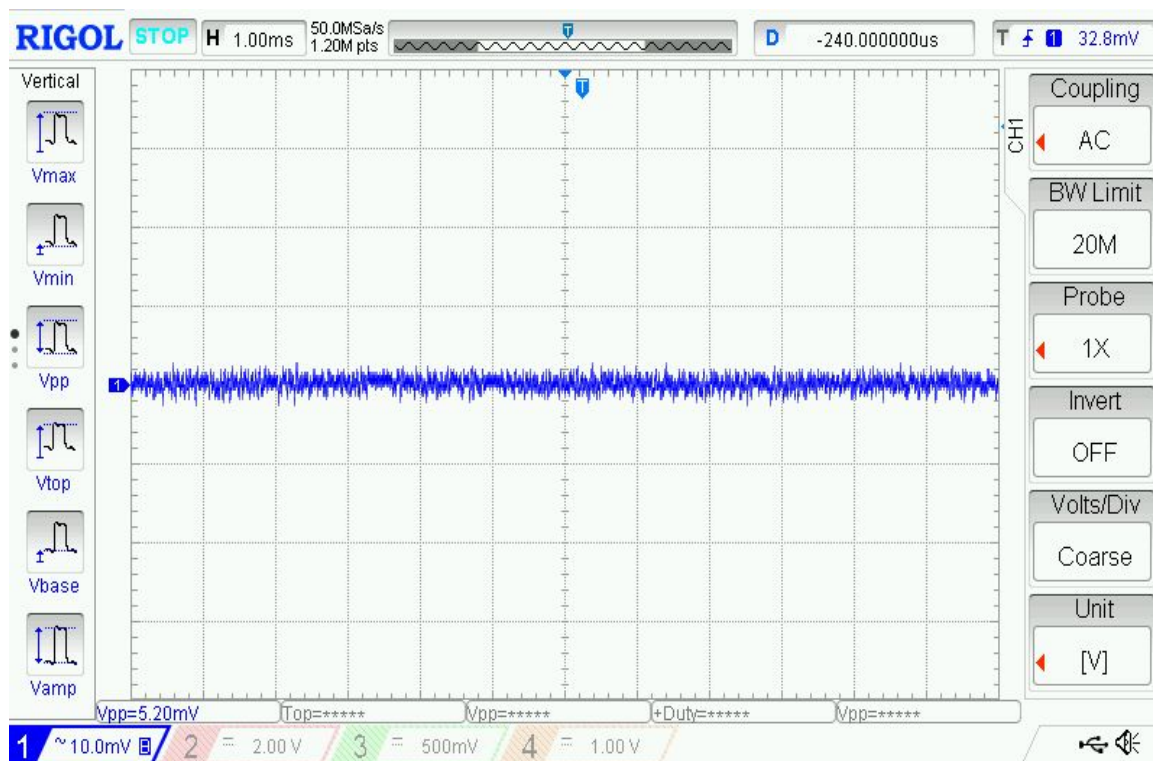


No Load
 $V_{PP} = 5.20 \text{ mV}$

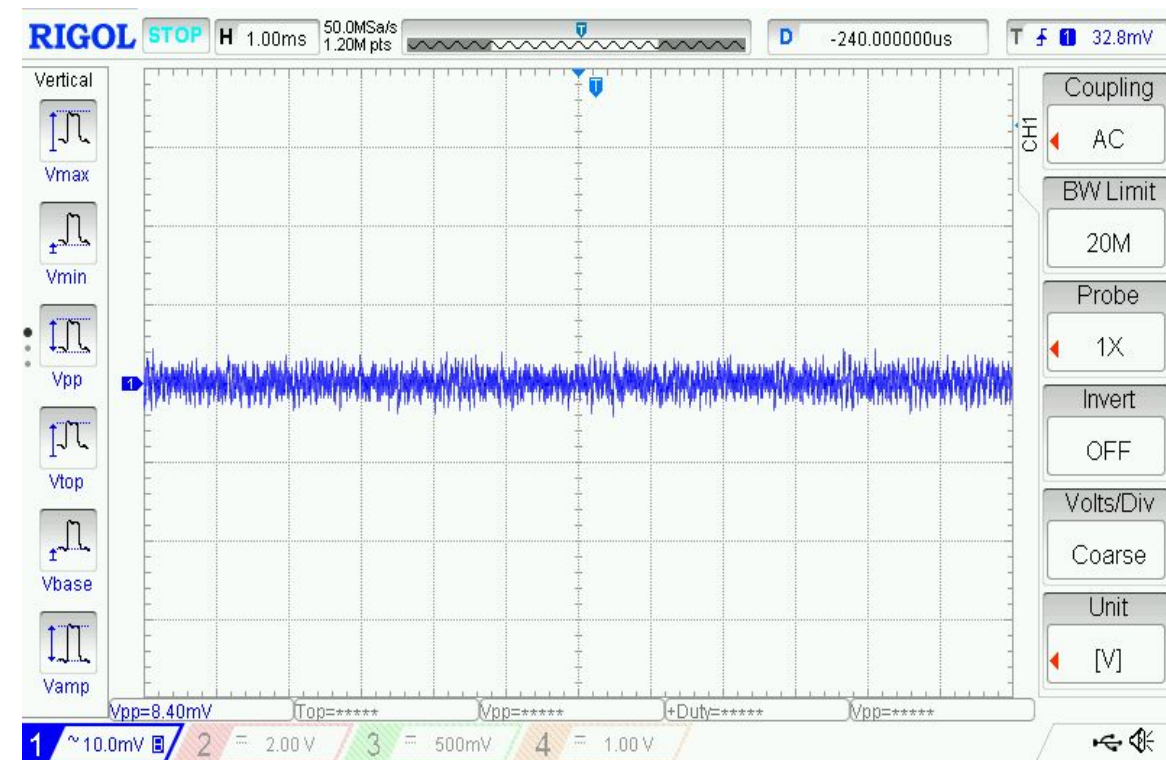

4 A Load
 $V_{PP} = 8.40 \text{ mV}$

$V_{out} = 0.6 \text{ V}$

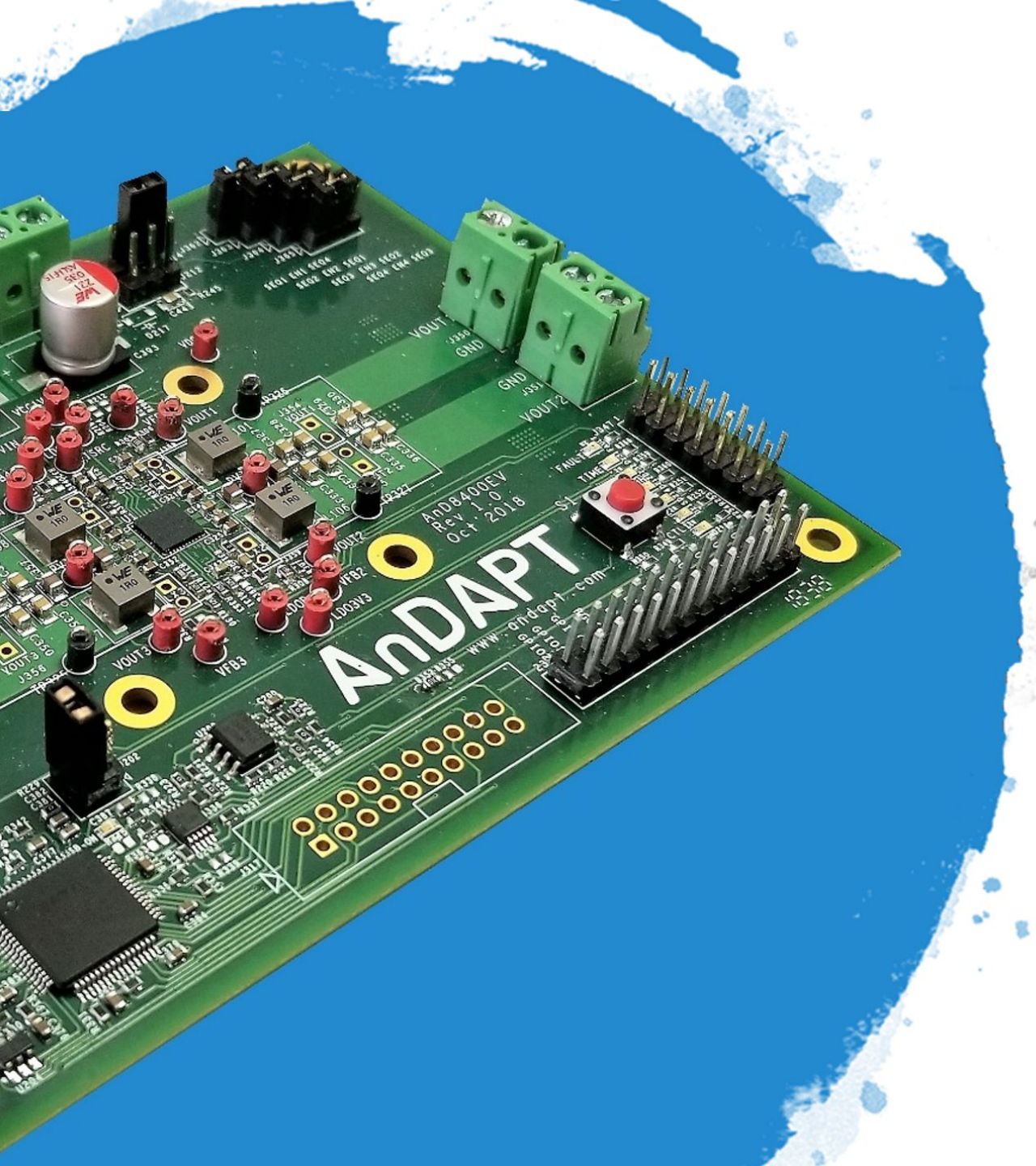

Thank You