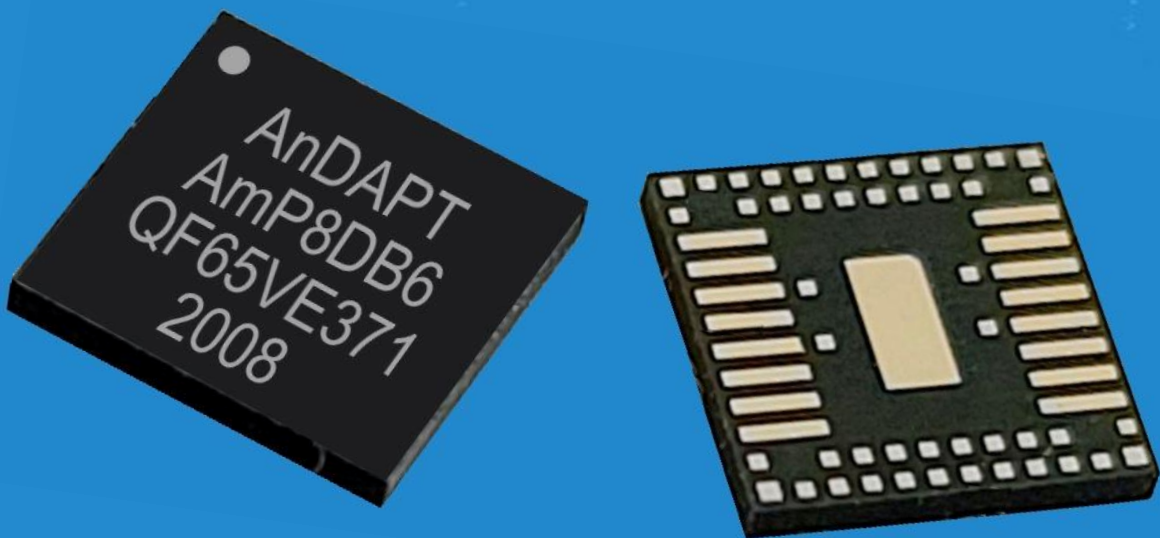





Xilinx Versal AI Core (Mid/High Voltage, Minimum Rails) Power Solution

Power Mapping

Versal AI Core Power Mapping Highlights

- Power tree mappings completed per data received from Xilinx Power Management team
- Both Typical and Upper use-cases are served by the same design
- Data gathered and bench tested by applications team at AnDAPT
 - Data meets or exceeds Xilinx power and timing specifications
- Total 9 power rails covered by 2x AmP ICs including memory and termination rails
- VCCINT (core rail) draws current from 132 A to 165 A and thus will be served using an external IC enabled/disabled by AmP IC
- Total solution area (excluding external core rail) is 1092.92 mm²
- Presentation contains thermal views of both ICs

Xilinx Versal AI Core Power Tree

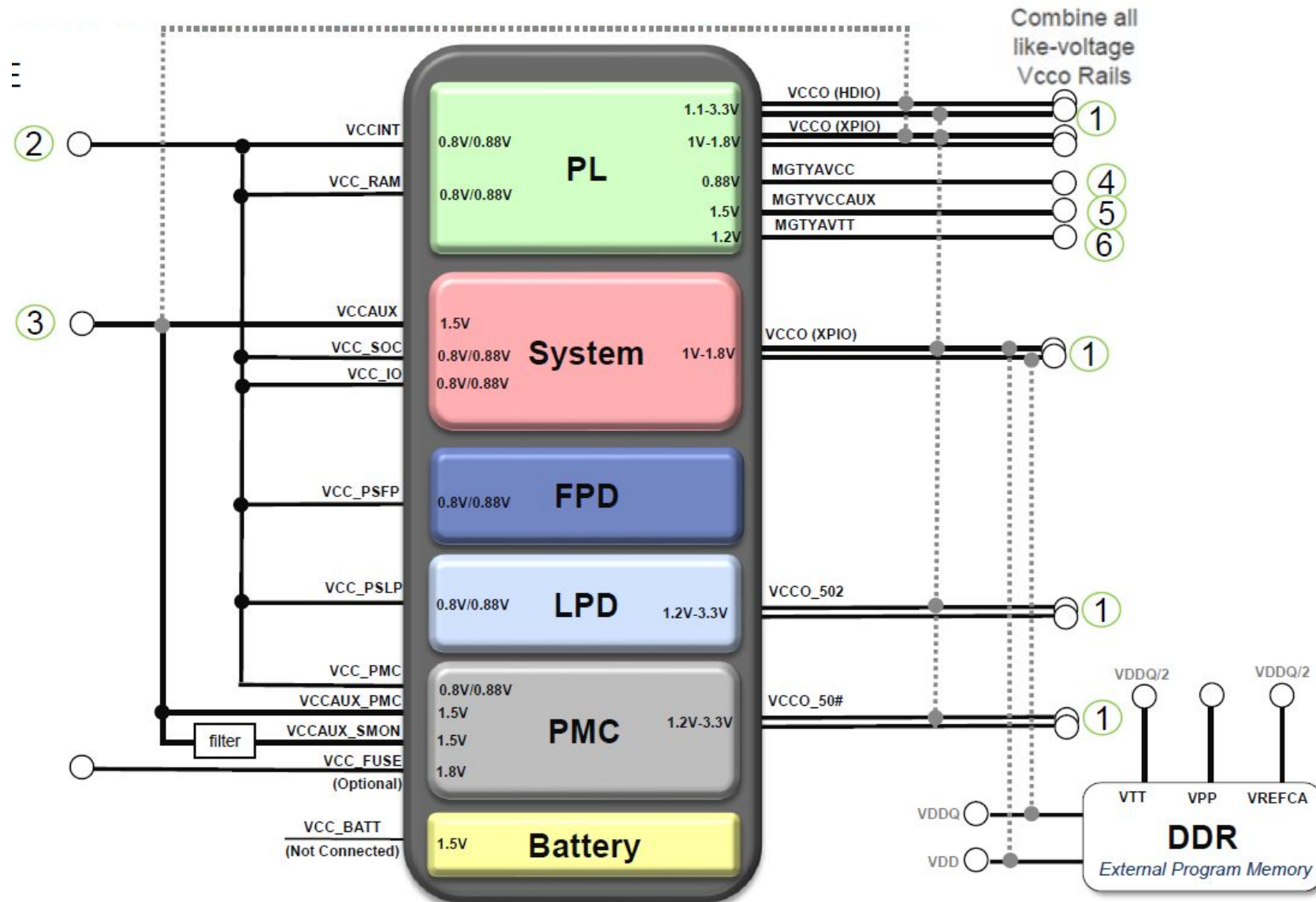

Versal AI Core Power Rails: Mid/High Voltage, Minimum Rails (Typical & Upper)

Sequence	Rail Name	Voltage (V)	AI Core	
			Typical (A)	Upper (A)
Rail 1	VCCINT/VCCINT_IO/VCCRAM, VCC_SOC, VCC_PSLP, VCC_PSFP, VCC_PMC	0.8V/0.88V	132.01	165.01
Rail 2	VCCAUX, VCCAUX_PMC, VCCAUX_SMON	1.5V	3.12	3.9
Rail 3	MGTAVCC	0.88V	2.47	3.08
Rail 4	MGTAVAUX	1.5V	0.23	0.29
Rail 5	MGTAVTT	1.2V	3.85	4.81
Rail 6	VCCO_PMIO[0...]	1.1V-3.3V, 1V-1.8V, 1.2V-3.3V	3.39	4.24
Current Total (A)			138.52	173.15


Power Tree Mapping: Versal AI Core (Mid/High Voltage, Minimum Rails)

#	Rail	Seq	Power Component	Type	Upstream Rail	Vinput (V)	Vout (V)	Iout (A)	AnDAPT PMIC
1	VCCO_XPIO (VCCO_XPIO, VCCO_HDIO)	1	Sync Buck	C200	PVIN	12	1.5	6	ARD_X_VRACRB_IC1
2	VCCO_502 (VCCO_502, VCCO_50X)	1	Sync Buck	C200	PVIN	12	1.5	4.3	
3	VCCINT (VCCINT, VCC_RAM, VCC_SOC, VCC_IO, VCC_PSFP, VCC_PSLP, VCC_PMC)	2	Ext IC	-	PVIN	12	0.8/0.88	165	
4	VCCAUX (VCCAUX, VCCAUX_PMC, VCCAUX_SMON)	3	Sync Buck	C200	PVIN	12	1.5	3.9 + 0.3	
5	MGTYAVCC	4	Sync Buck	C200	PVIN	12	0.88	3.1	
6	MGTYVCCAUX	5	LDO	C710	VCCAUX	1.5	0.88	0.3	ARD_X_VRACRB_IC2
7	MGTYAVTT	6	Sync Buck	C200	PVIN	12	1.2	4.9	
8	VDDQ	7	Sync Buck	C200	PVIN	12	1.2	3 + 2	
9	VTT	8	VTT Terminator	C210	VDDQ	1.2	0.6	2	


PVIN = 12V

Total estimated solution area = 1092.92 mm²

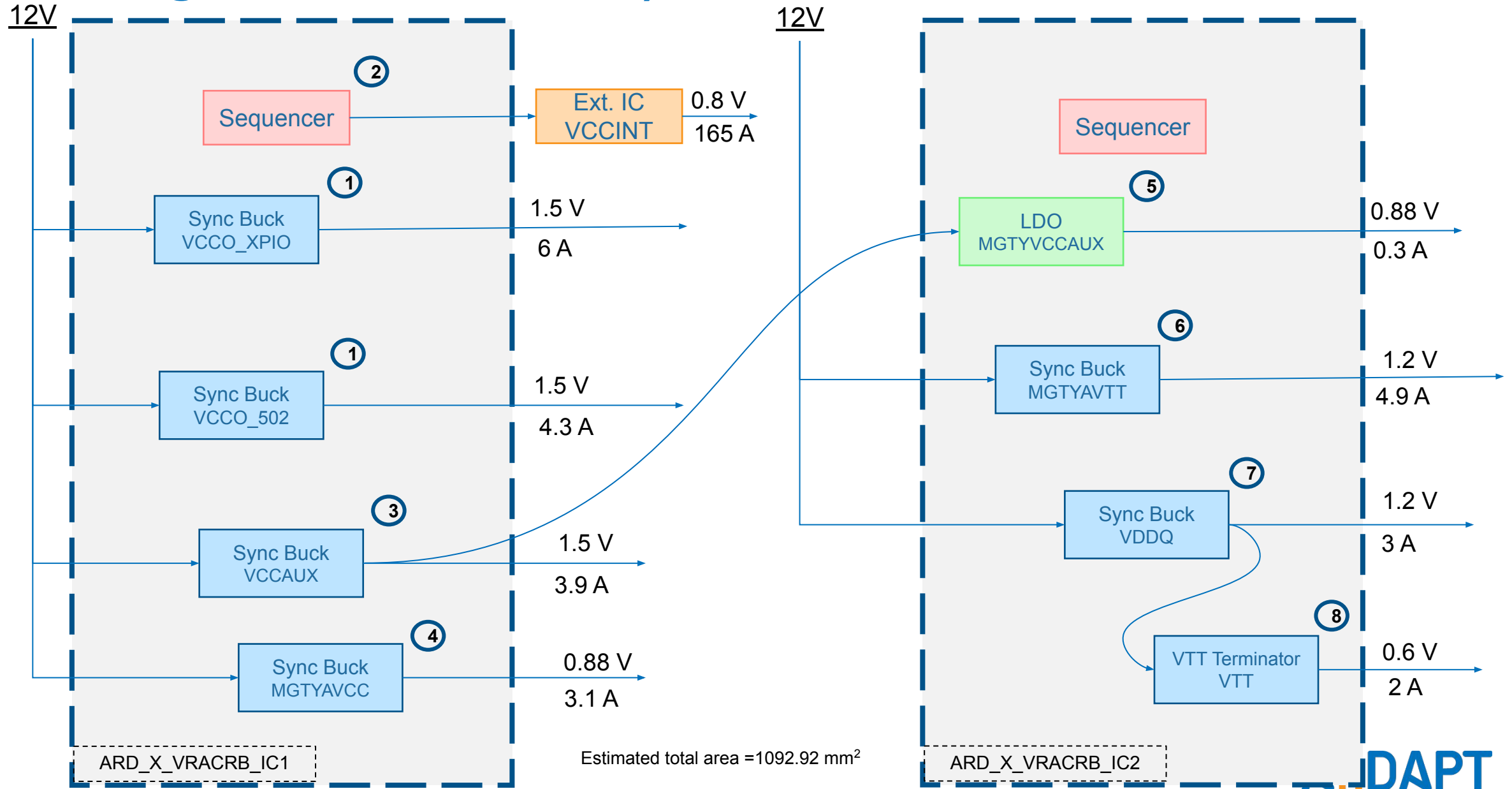
Power Tree Mapping: Versal AI Core (Mid/High Voltage, Minimum Rails)




Mapping (WebAmP View) Design –IC1

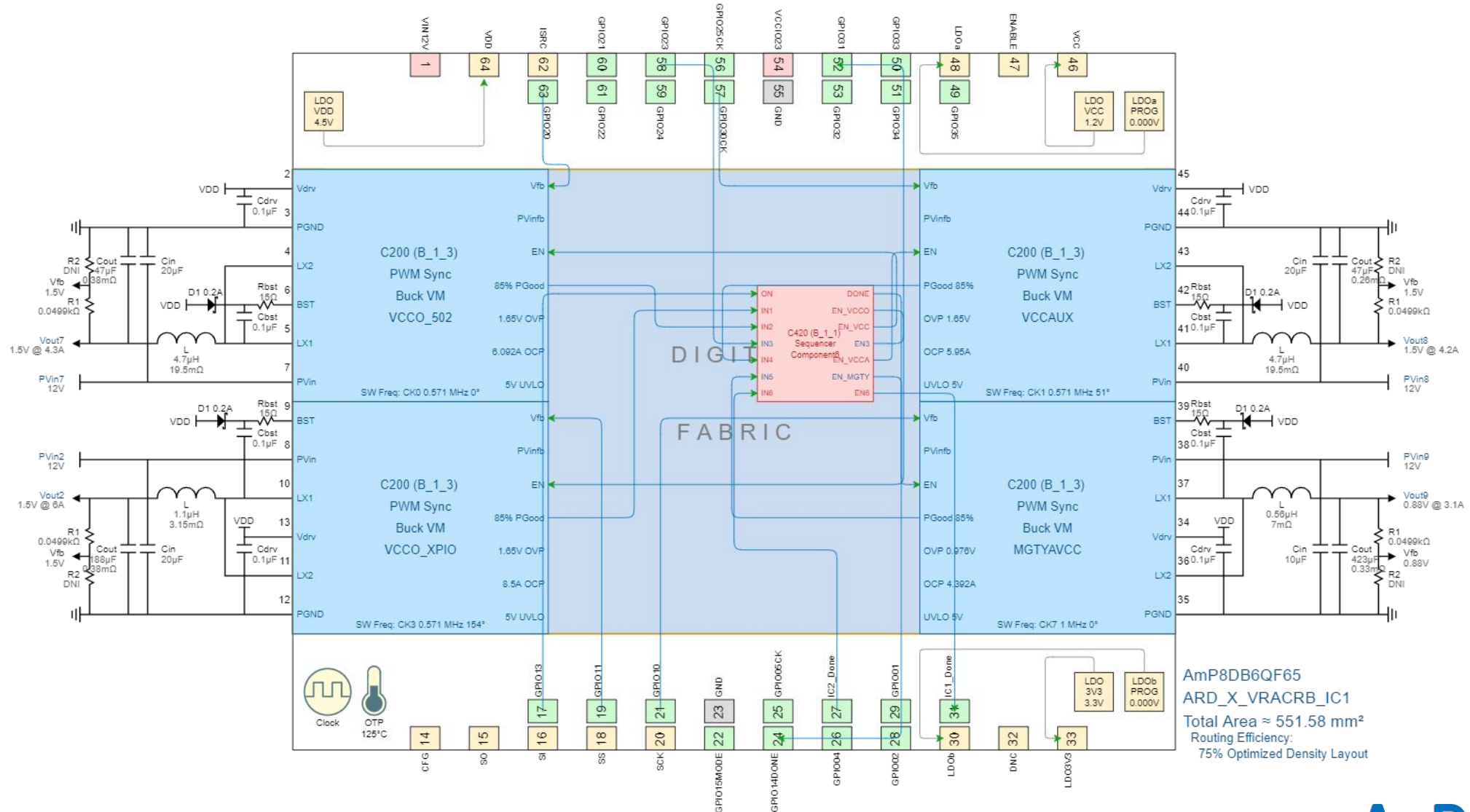


Mapping (Thermal View) –IC1

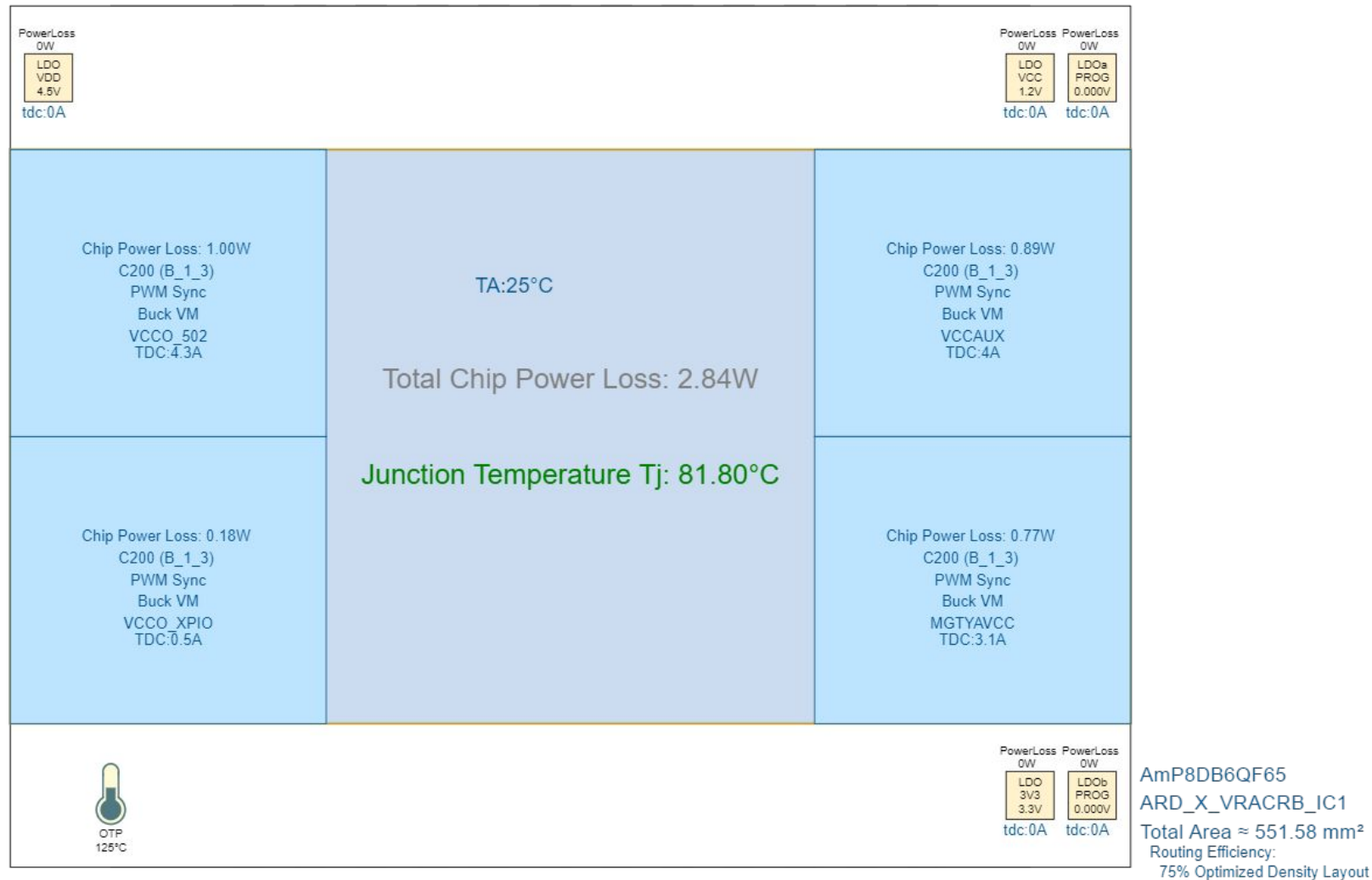


Mapping (WebAmP View) Design –IC2

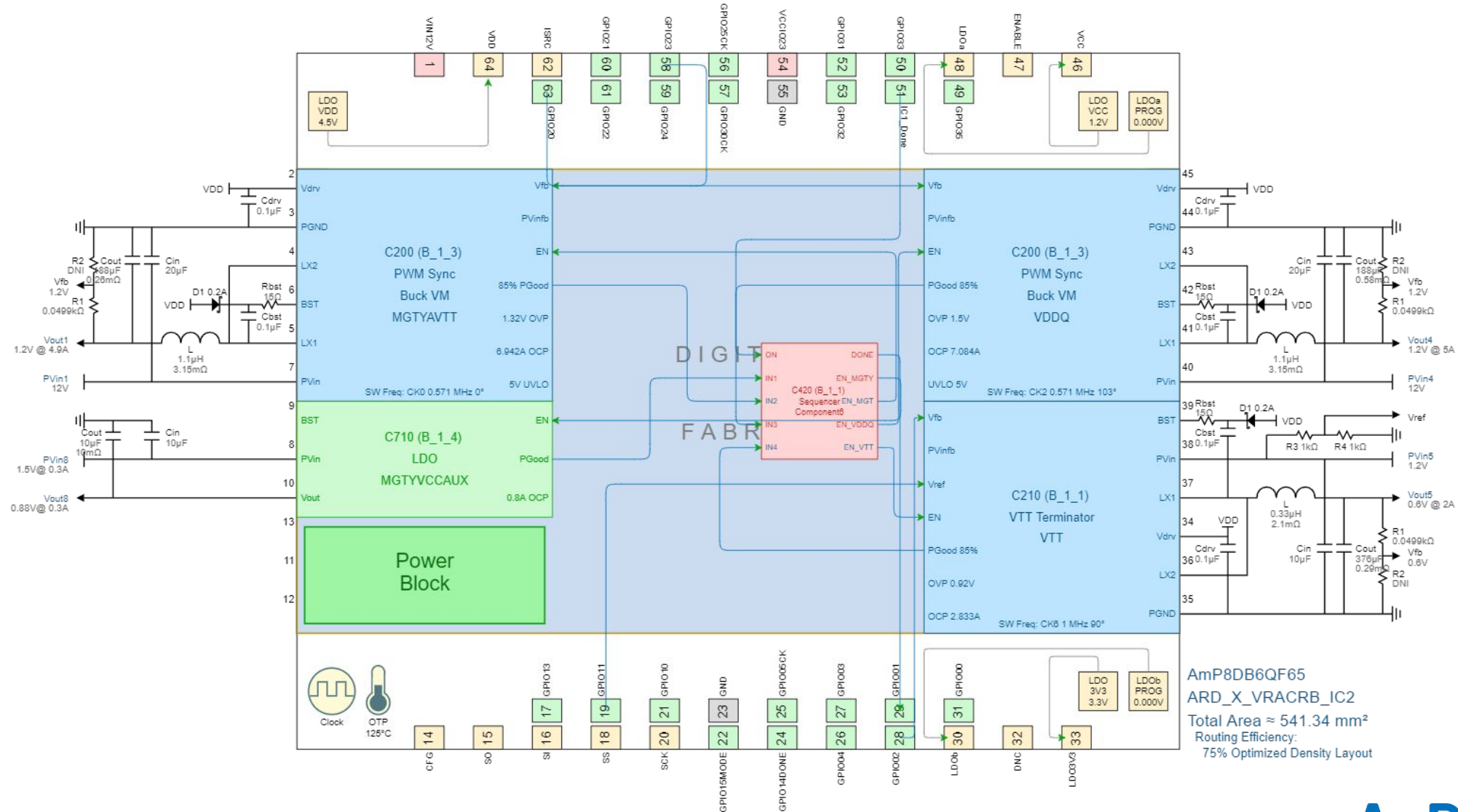

Mapping (Thermal View) –IC2

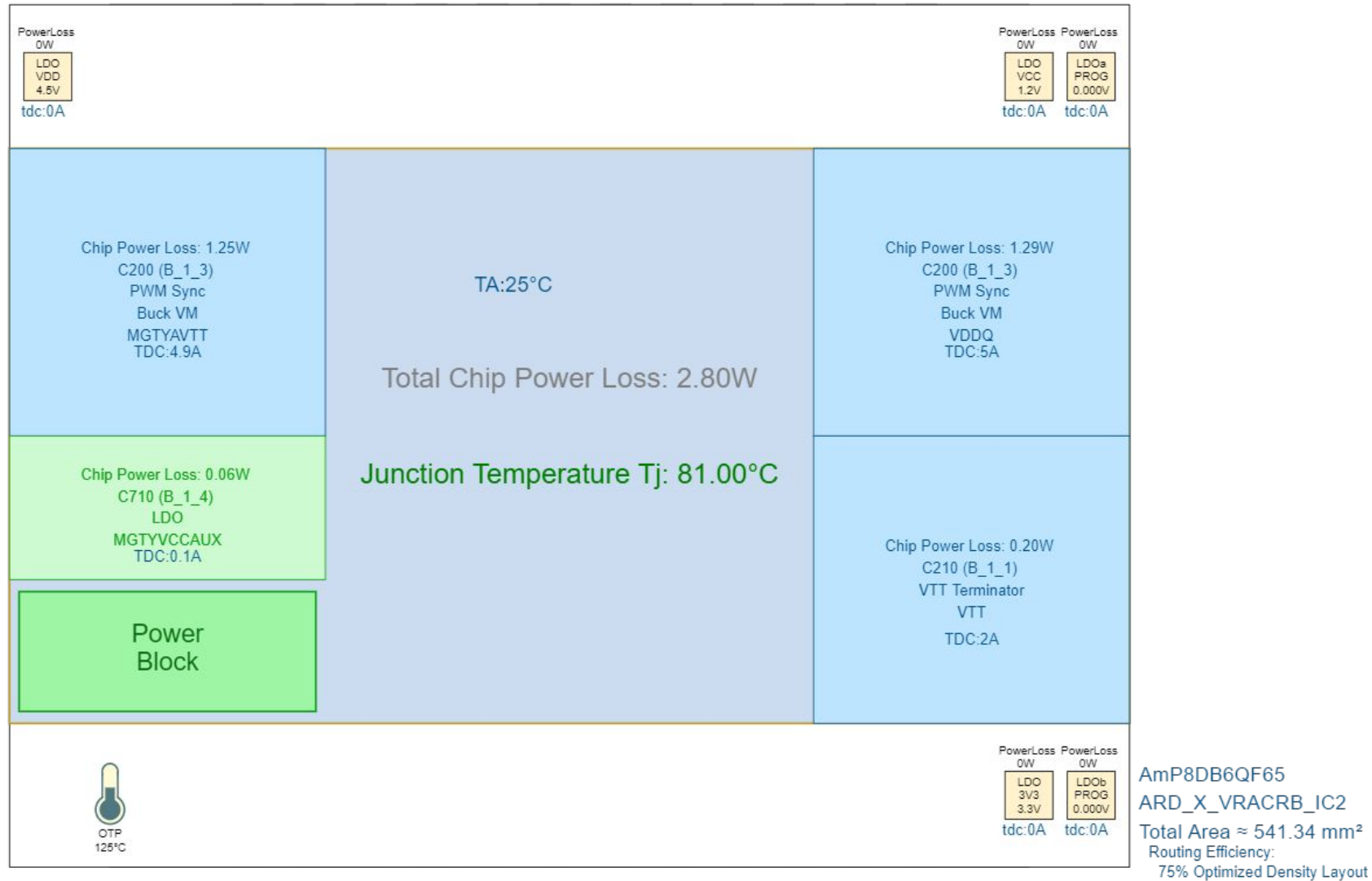

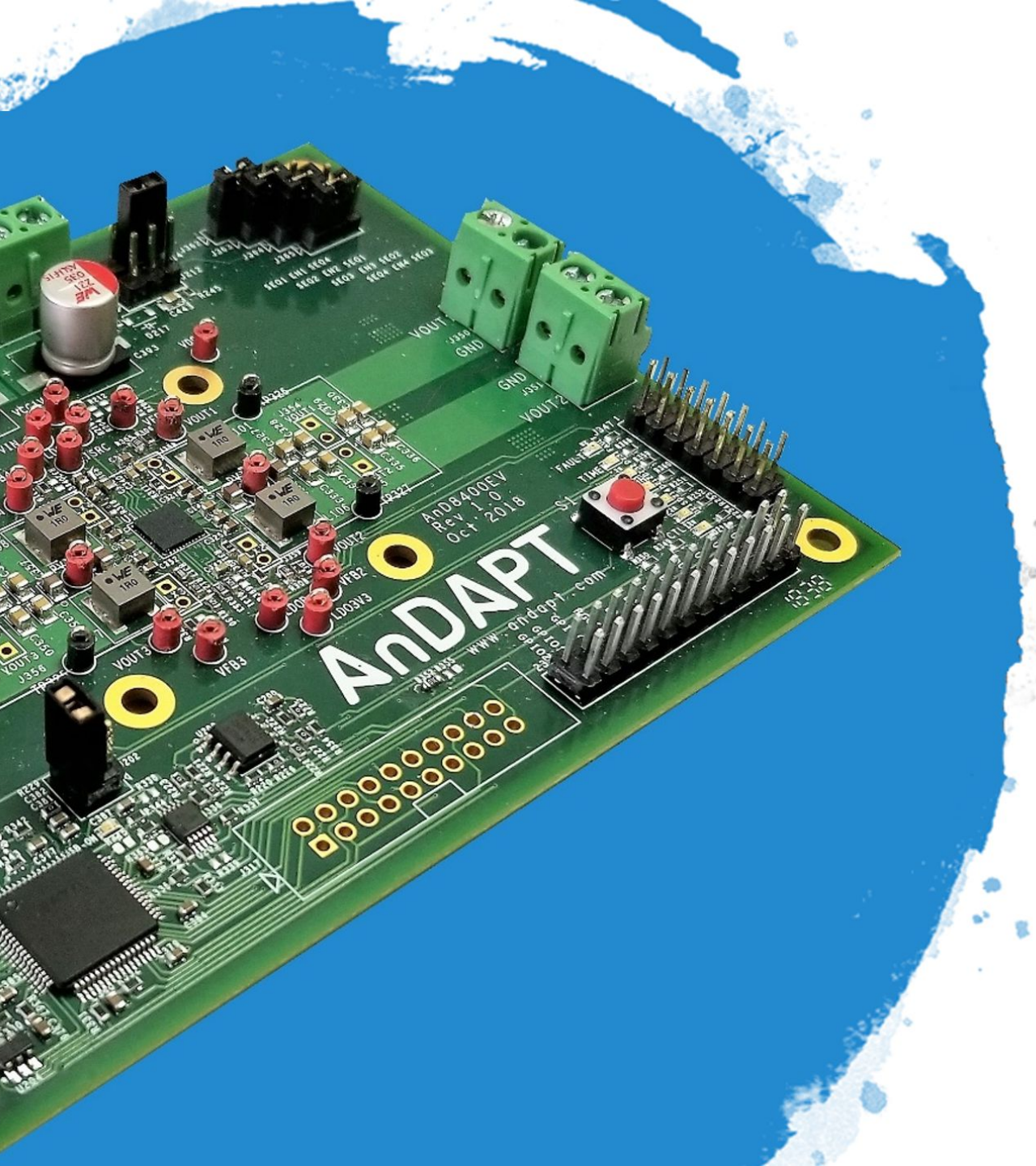

Test Data


Versal AI Core

VCCO_XPIO

1.5 V / 6 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1.1 \text{ } \mu\text{H}$, P/N Wurth 744314110
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

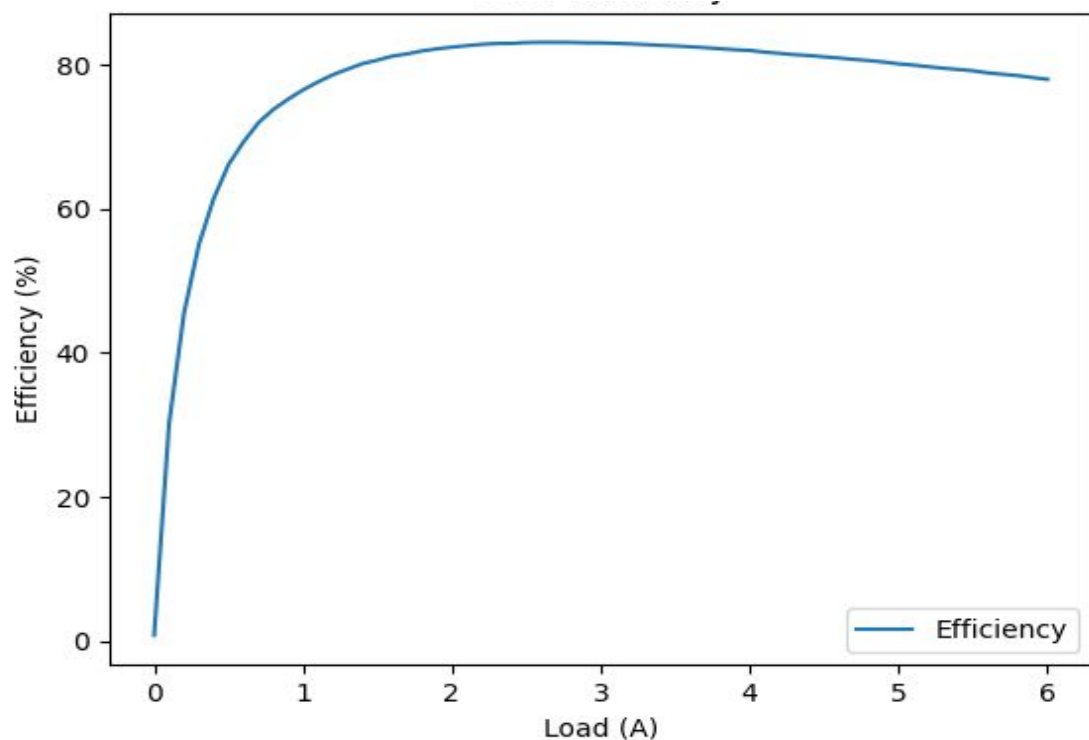


$V_{out} = 1.5V$
Transient 4.5 – 6 A@10 A/ μ s
 $V_{PP} = 27.18 \text{ mV}$
 $F_{sw} = 0.571 \text{ MHz}$
 $L = 1.1 \text{ } \mu\text{H}$, $C = 4 \times 47 \text{ } \mu\text{F}$

Ripple

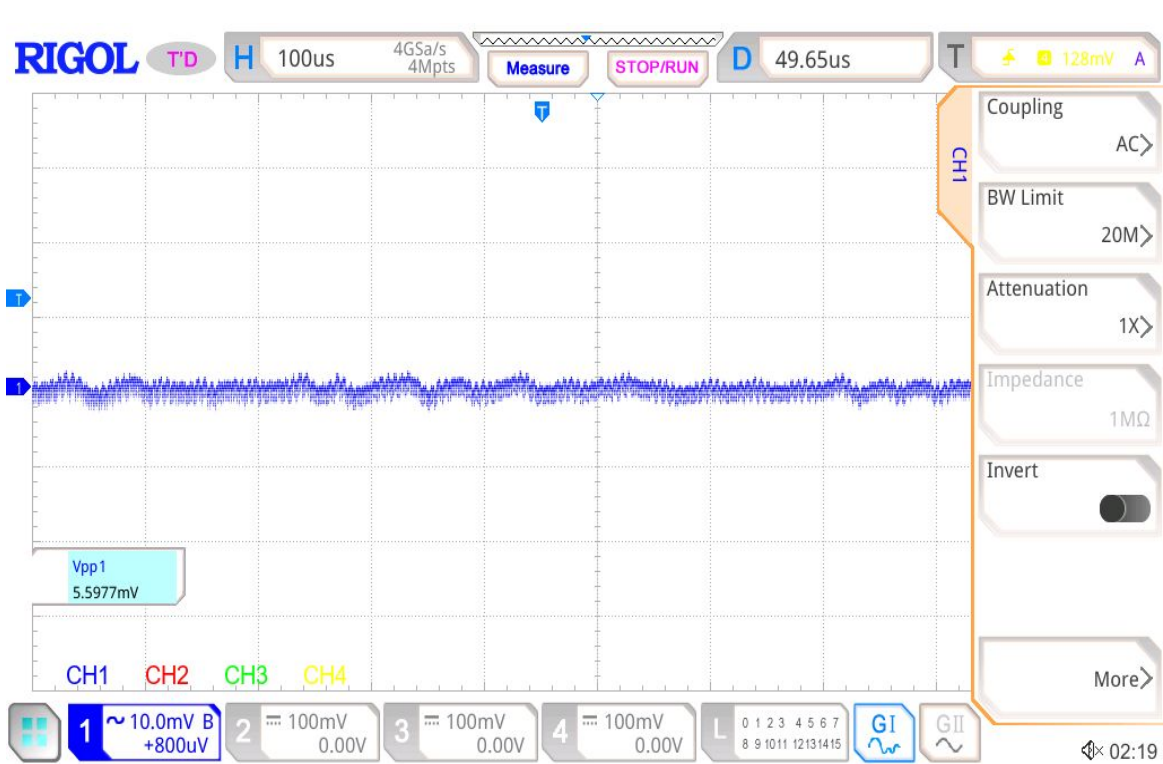

No Load
 $V_{PP} = 5.59 \text{ mV}$

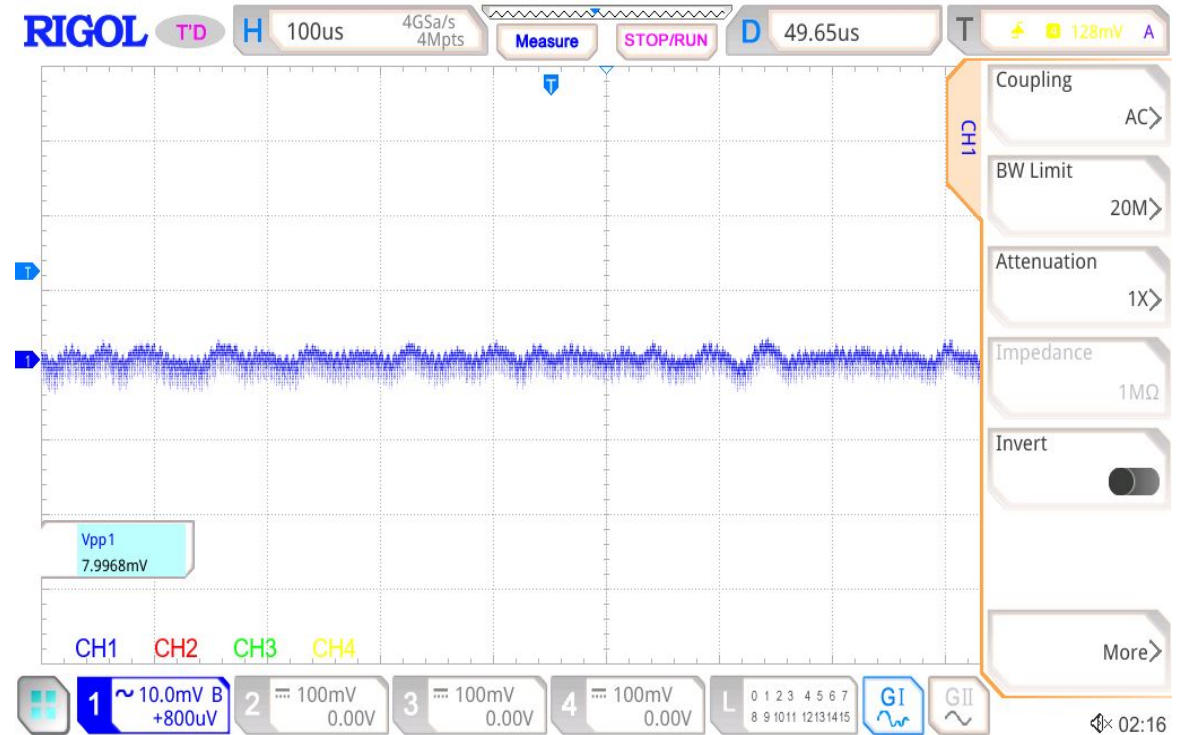

6 A Load
 $V_{PP} = 7.99 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

VCCO_502

1.5 V / 4.3 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \text{ } \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

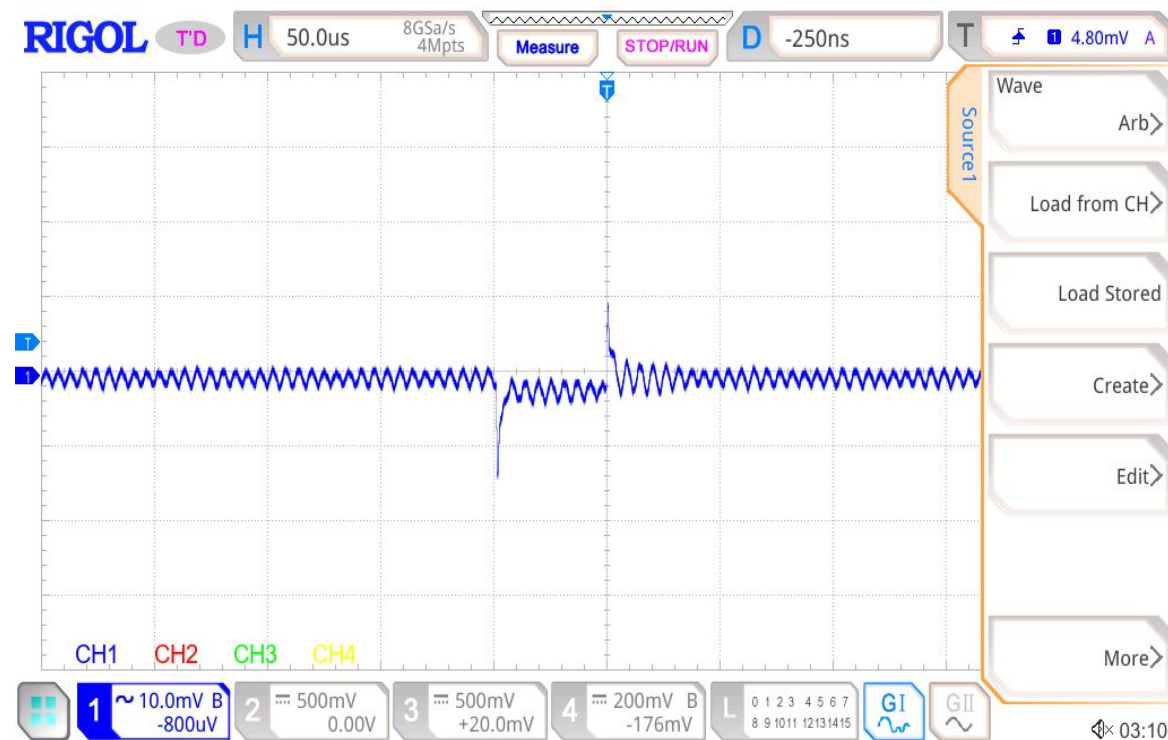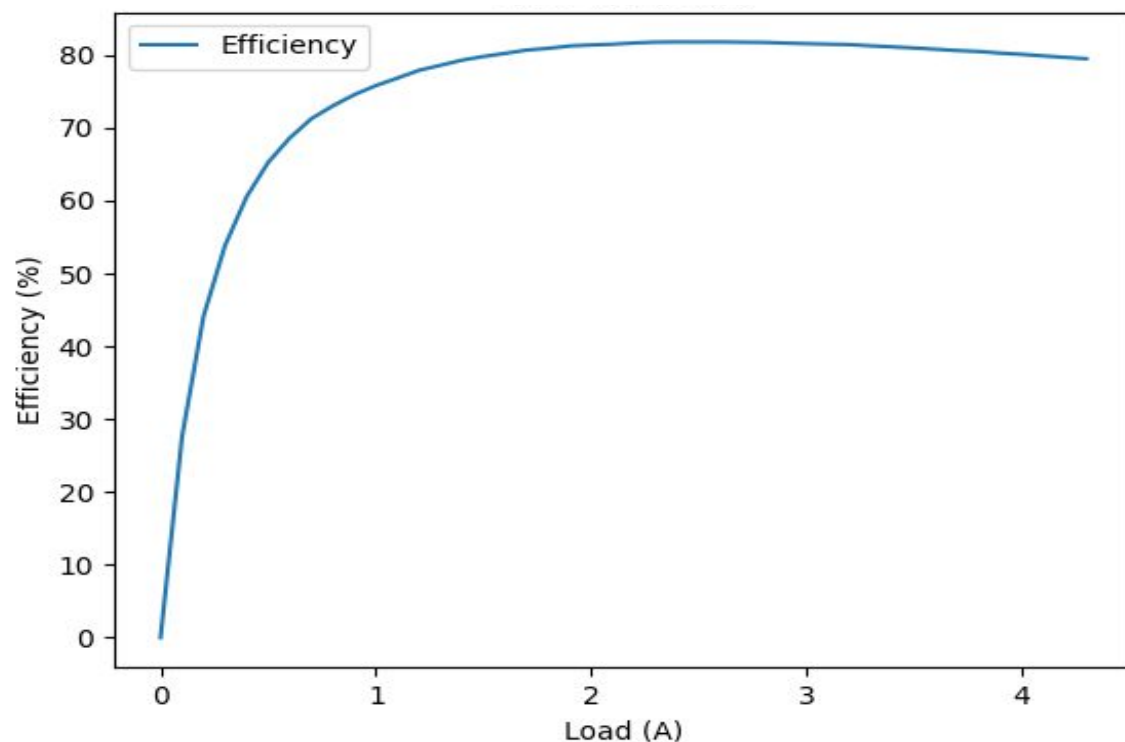


V_{out} = 1.5V
Transient 2.88A – 4.3A @ 10 A/μs
V_{pp} = 25 mV
F_{sw} = 0.571 MHz
L = 4.7 μH, C = 1x47 uF

Ripple

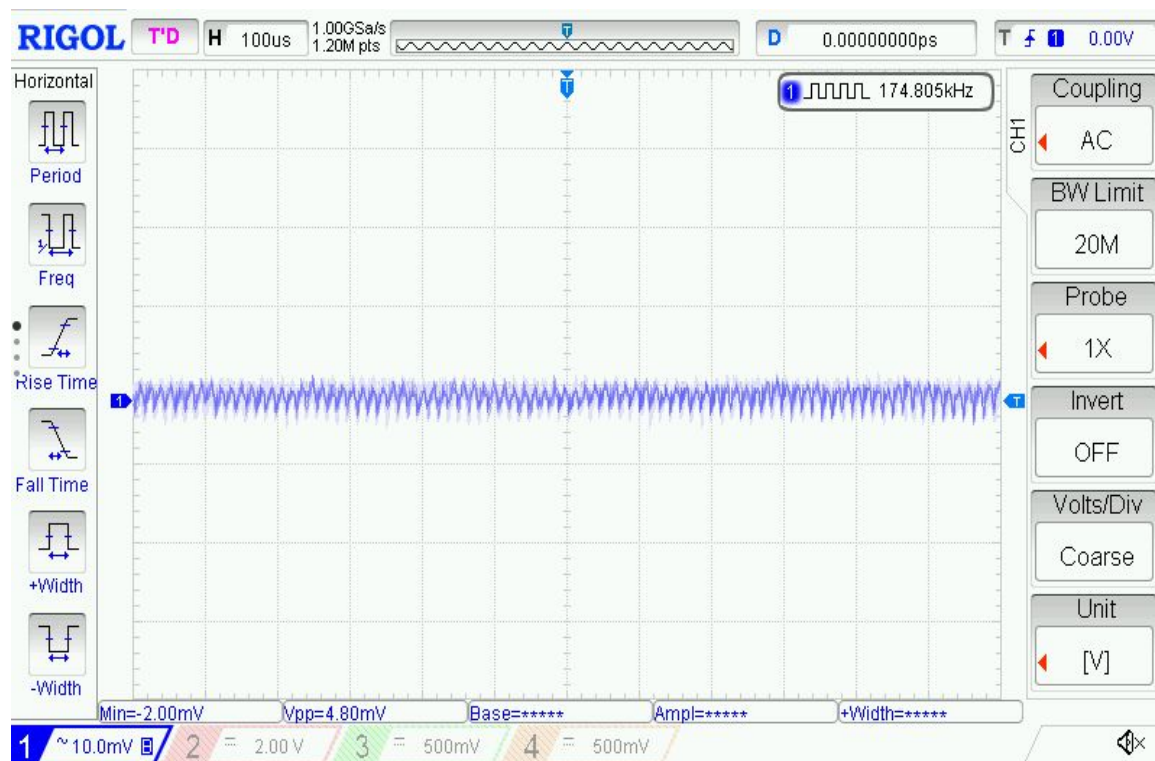

No Load
 $V_{PP} = 4.80 \text{ mV}$

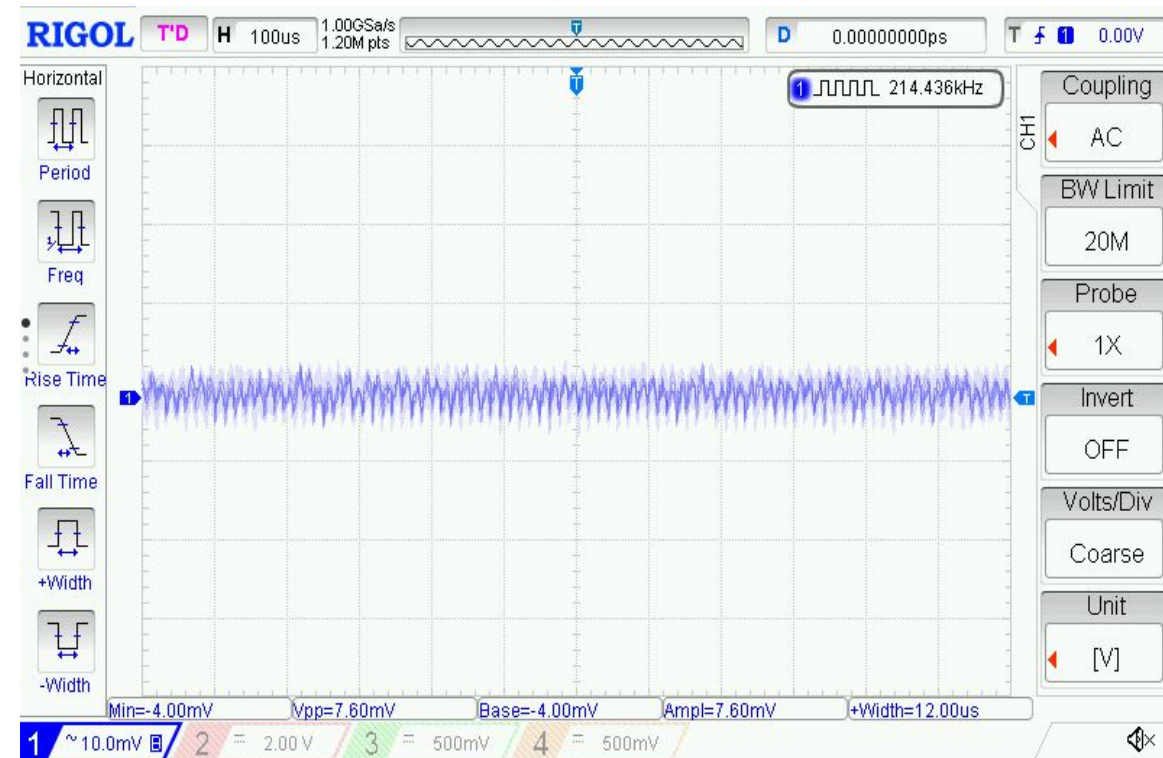

4.3 A Load
 $V_{PP} = 7.60 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

VCCAUX

1.5 V / 4.2 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \text{ } \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

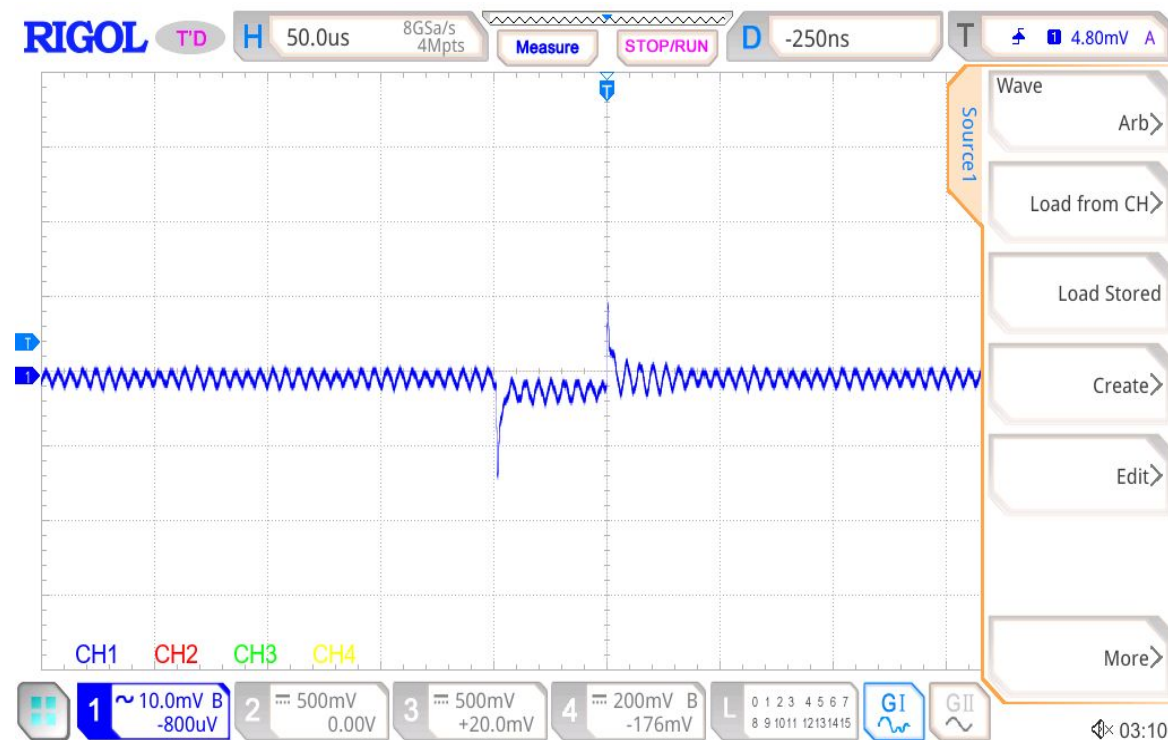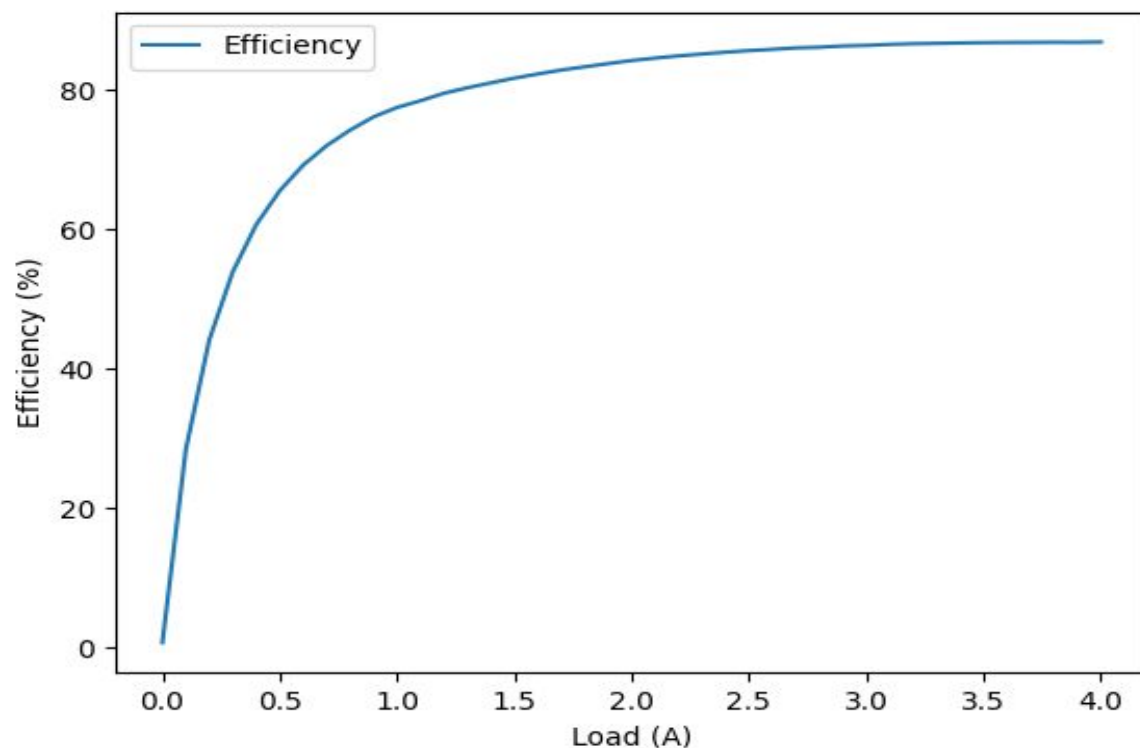


$V_{out} = 1.5\text{ V}$
Transient 2.81A – 4.2A @ 10 A/ μ s
 $V_{PP} = 25\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 4.7\text{ }\mu\text{H}$, $C = 1 \times 47\text{ }\mu\text{F}$

Ripple

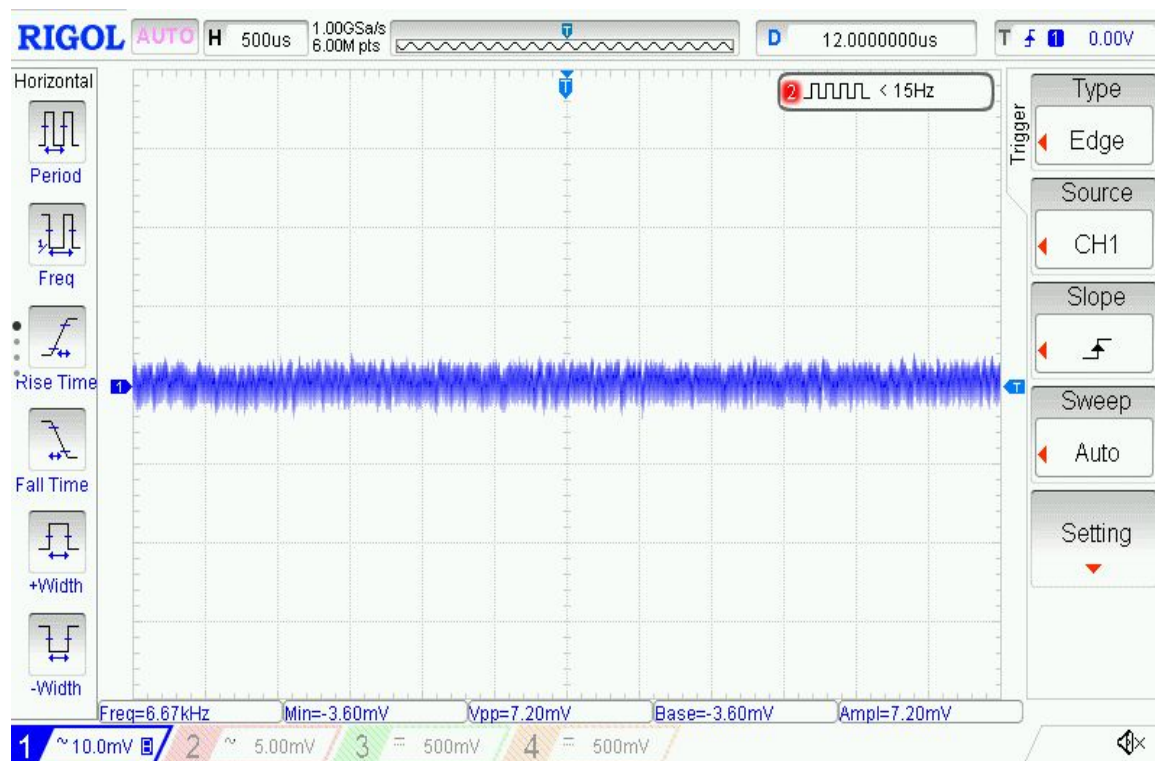

No Load
 $V_{PP} = 7.20 \text{ mV}$

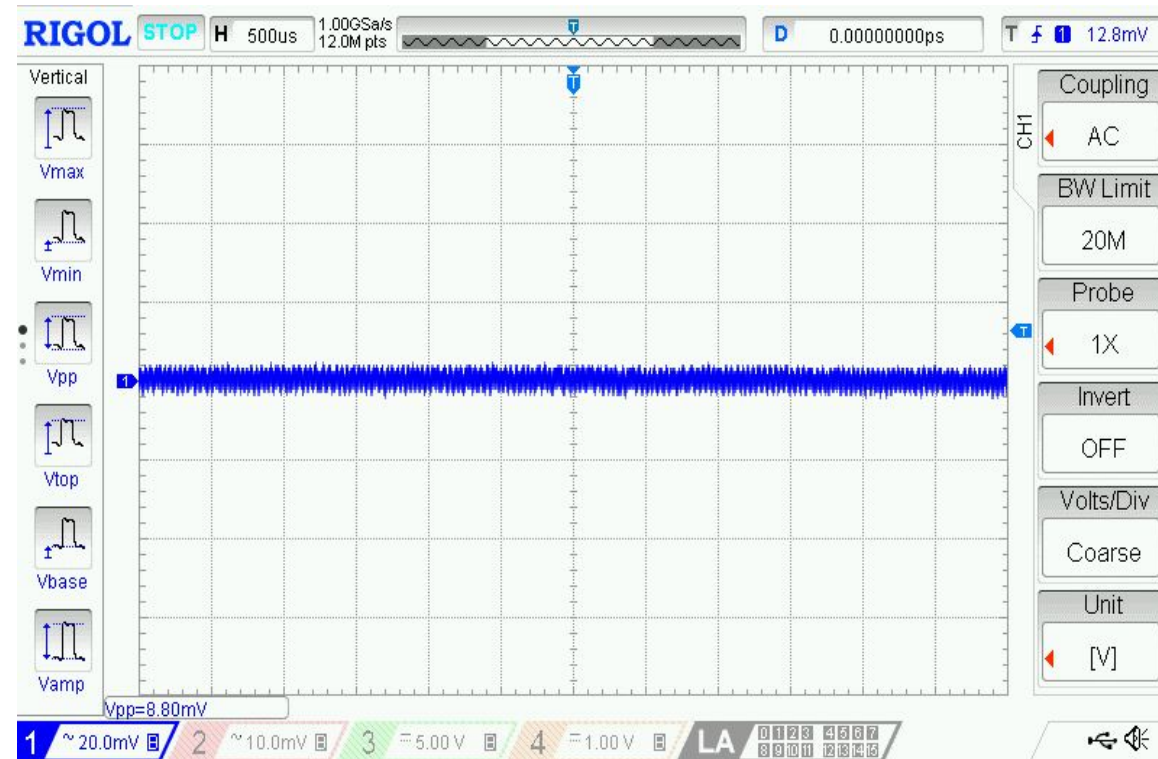



4.2 A Load
 $V_{PP} = 8.80 \text{ mV}$

MGTAVCC

0.88 V / 3.1 A


- C200 (Synchronous Buck)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744383560056
- $C = 9 \times 47 \mu\text{F}$

Efficiency & Transient

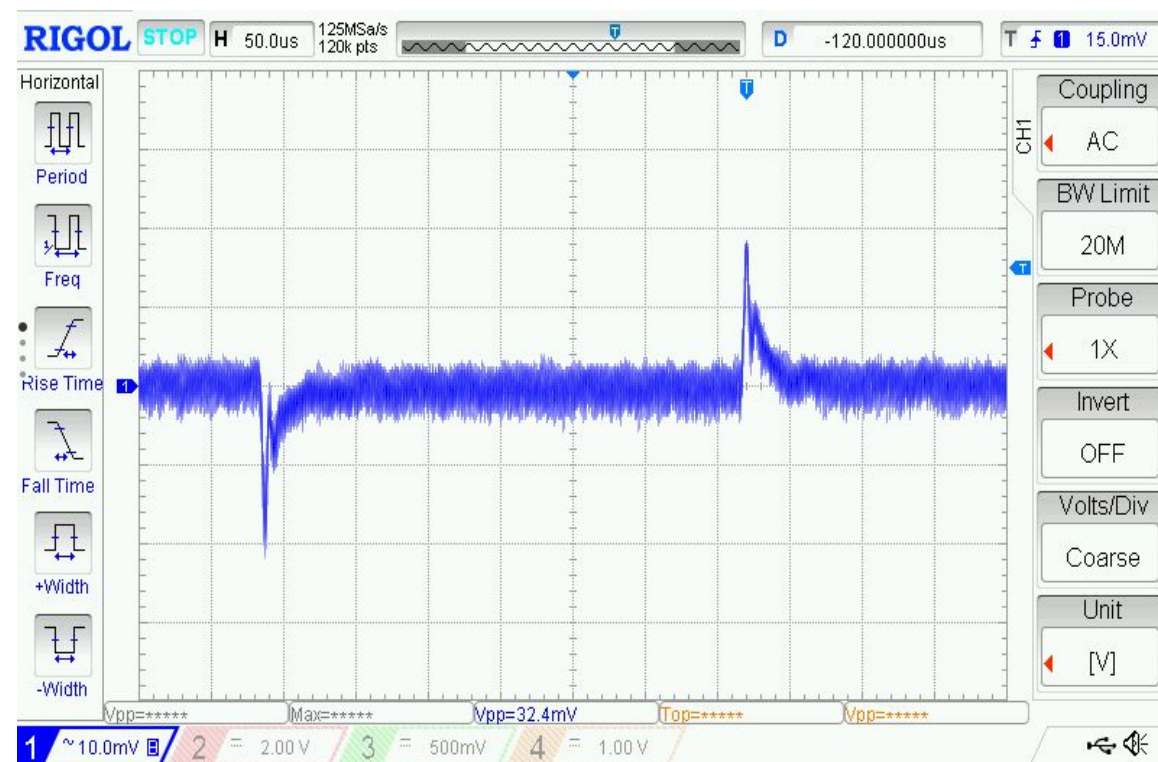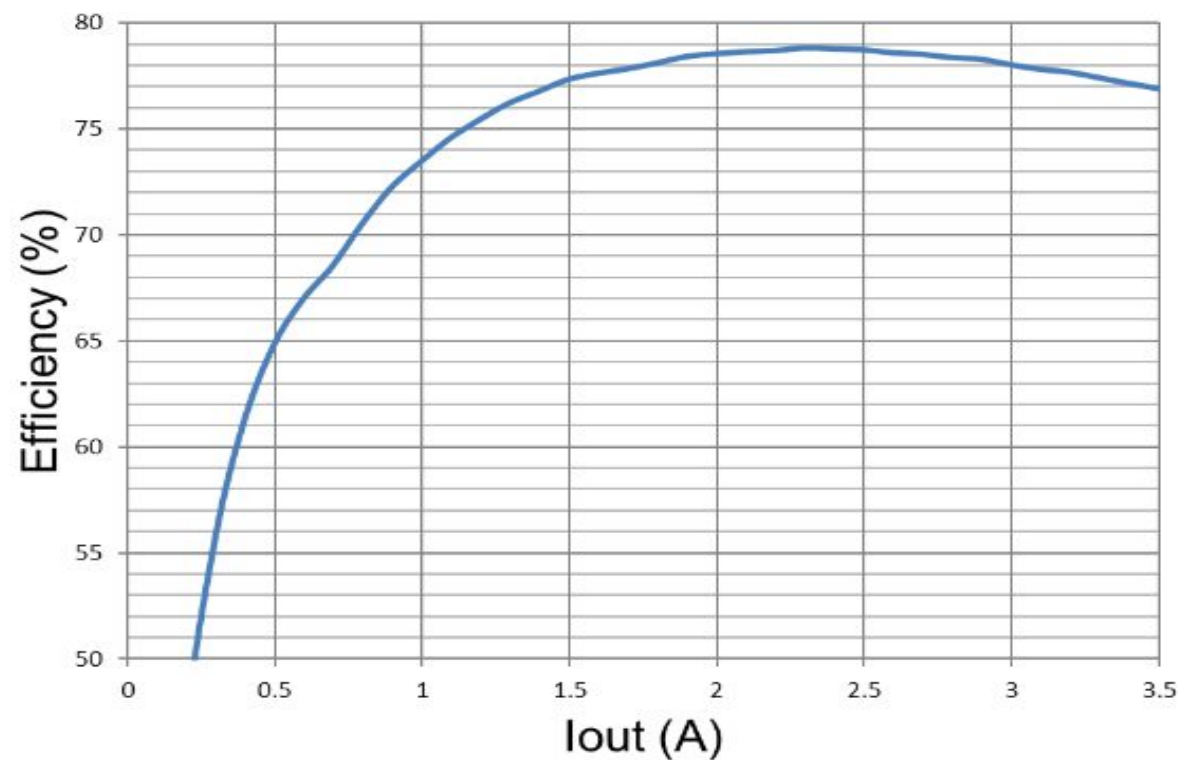


Vout = 0.88 V
Transient 2.625A – 3.5A @ 10 A/μs
 $V_{PP} = 32.4$ mV
Fsw = 1 MHz
L = 0.56 μH, C = 9x47 uF

Ripple

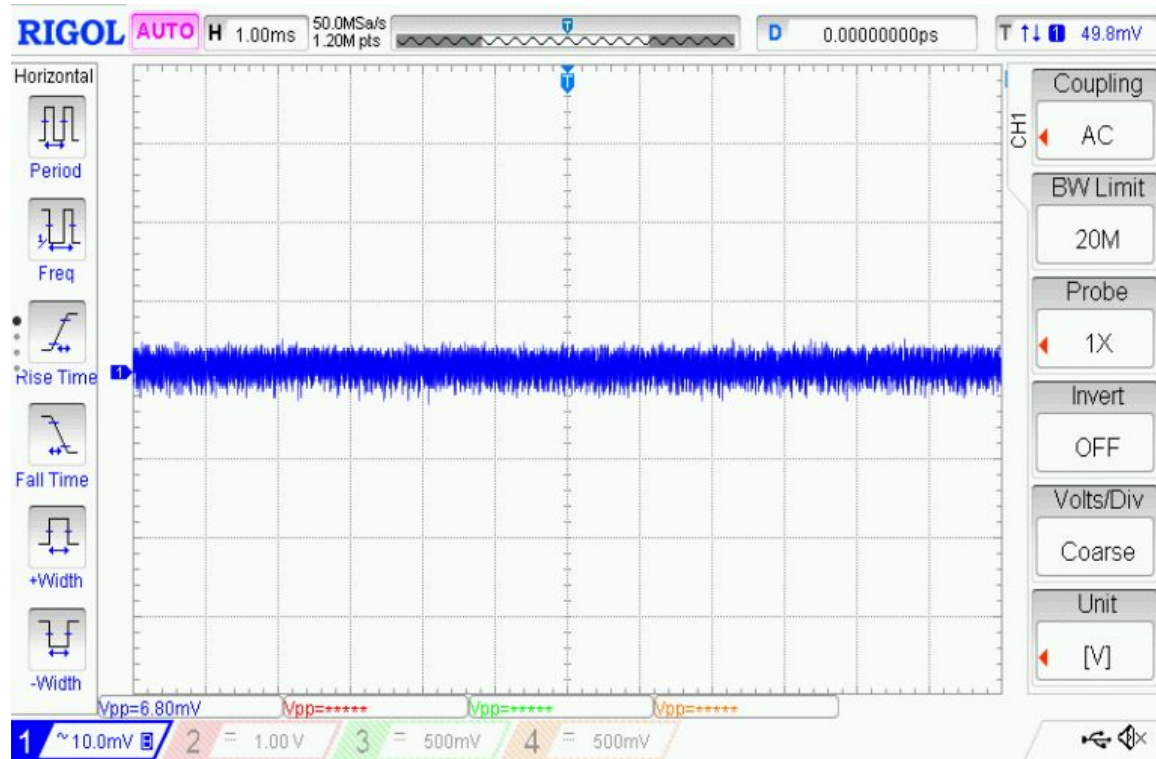

No Load
 $V_{PP} = 6.80 \text{ mV}$

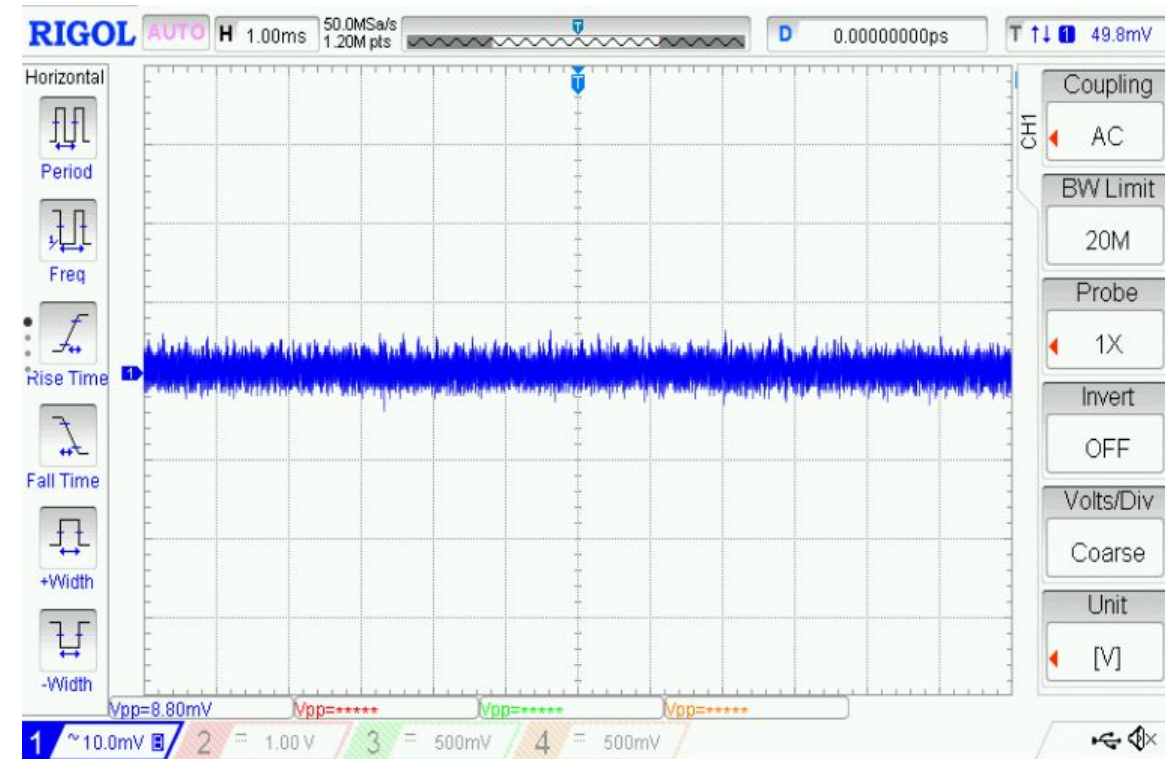

3.1 A Load
 $V_{PP} = 8.80 \text{ mV}$


$V_{out} = 0.88 \text{ V}$

MGTYVCCAUX

0.88 V / 0.3 A


- C710 LDO

Transient

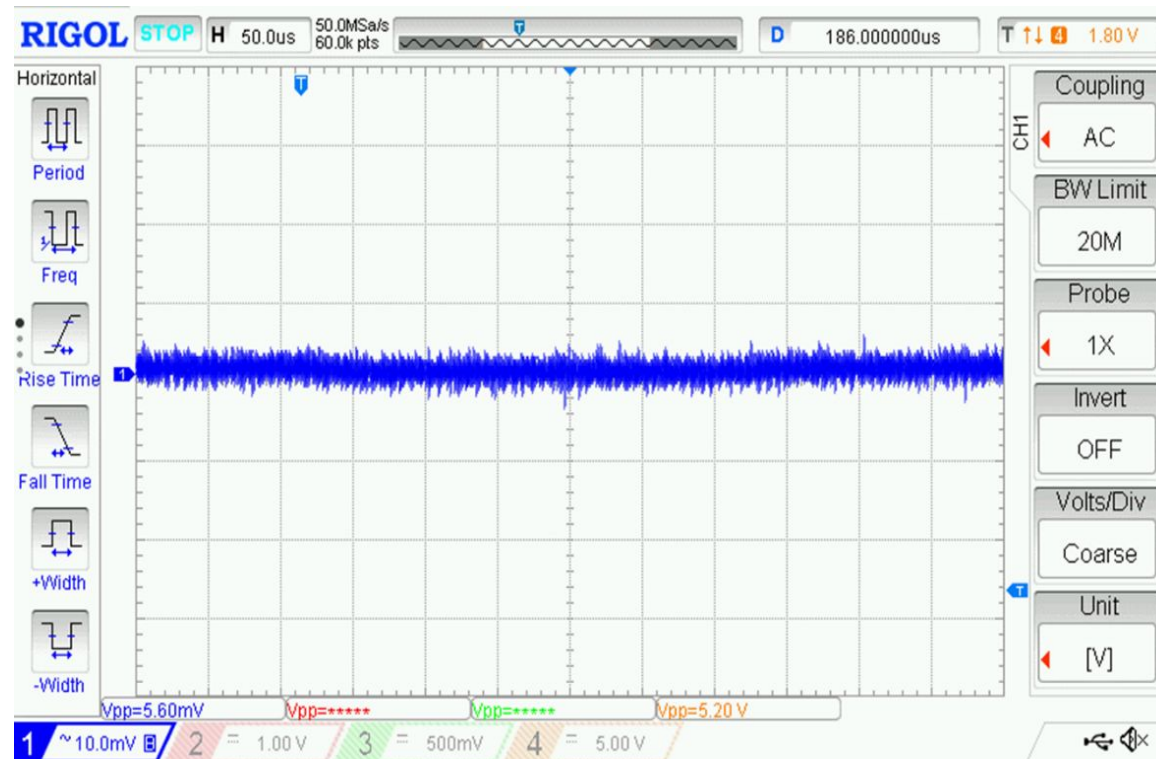


$V_{out} = 0.88 \text{ V}$
Transient $0.21 \text{ A} - 0.35 \text{ A} @ 2.5 \text{ A}/\mu\text{s}$
 $V_{PP} = 5.6 \text{ mV}$

Ripple

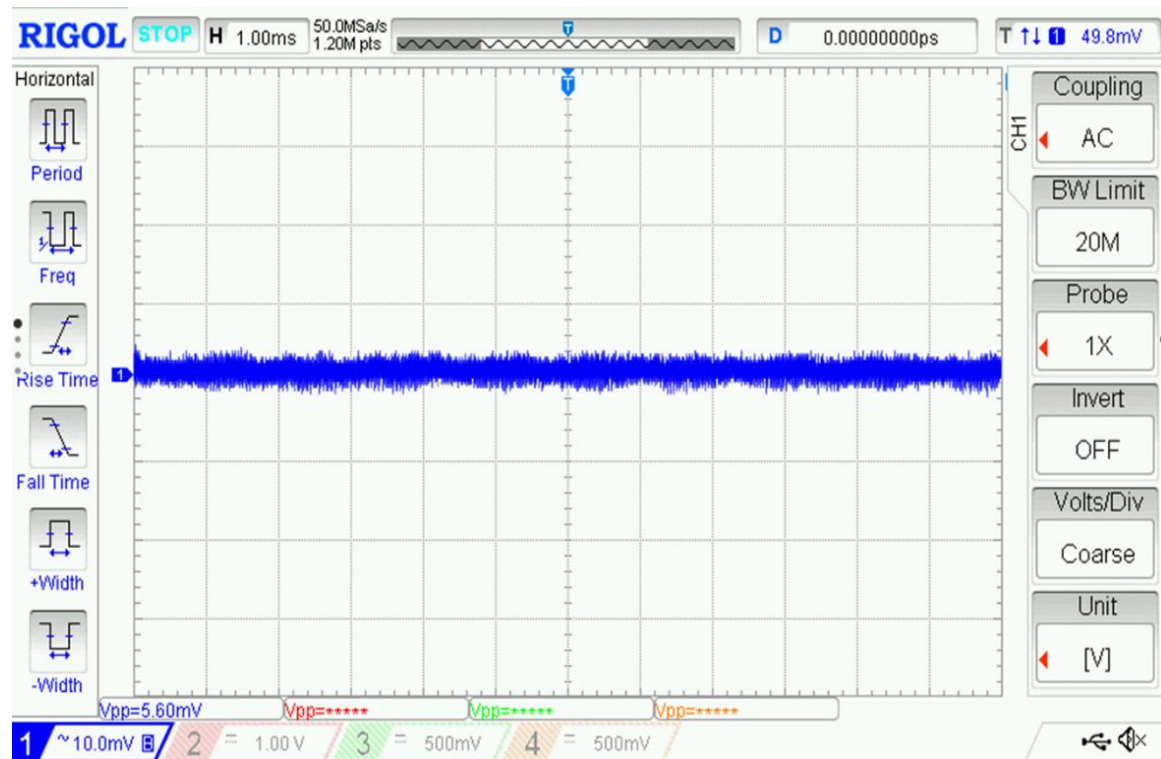

No Load
 $V_{PP} = 5.6 \text{ mV}$

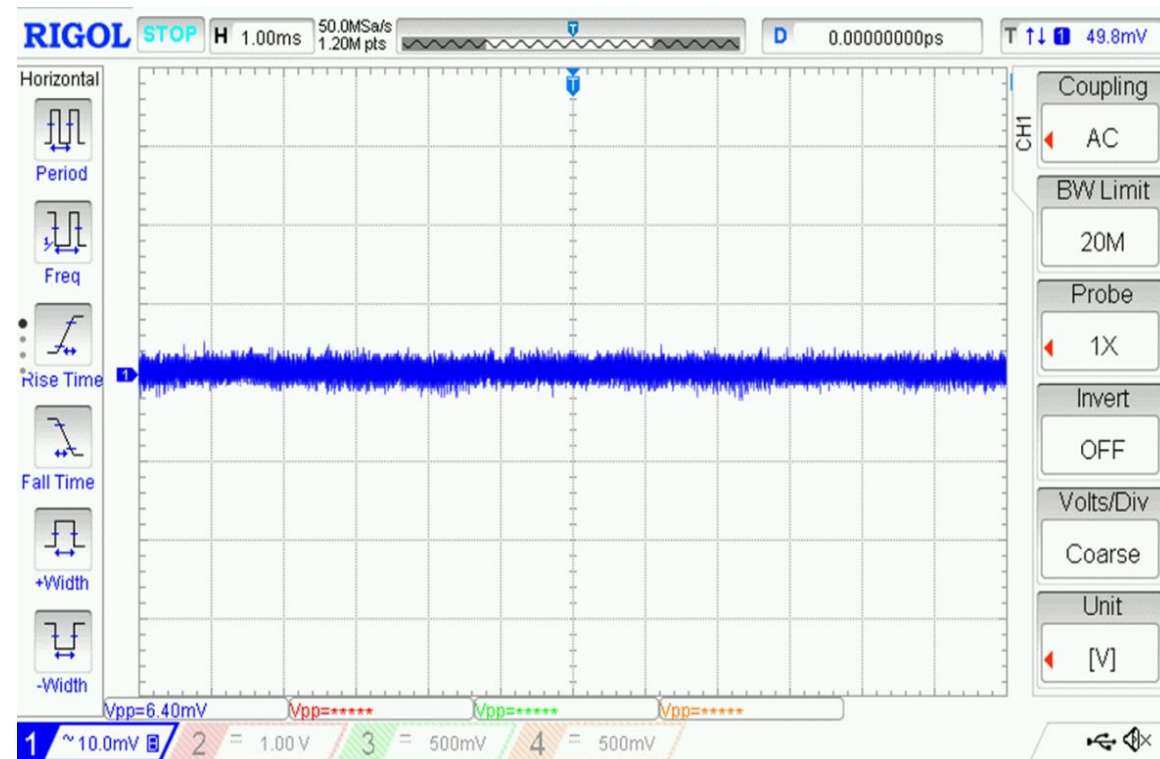

$V_{out} = 0.88 \text{ V}$



0.3 A Load
 $V_{PP} = 6.4 \text{ mV}$

MGTYAVTT

1.2 V / 4.9 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1.1 \text{ } \mu\text{H}$, P/N Wurth 744314110
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

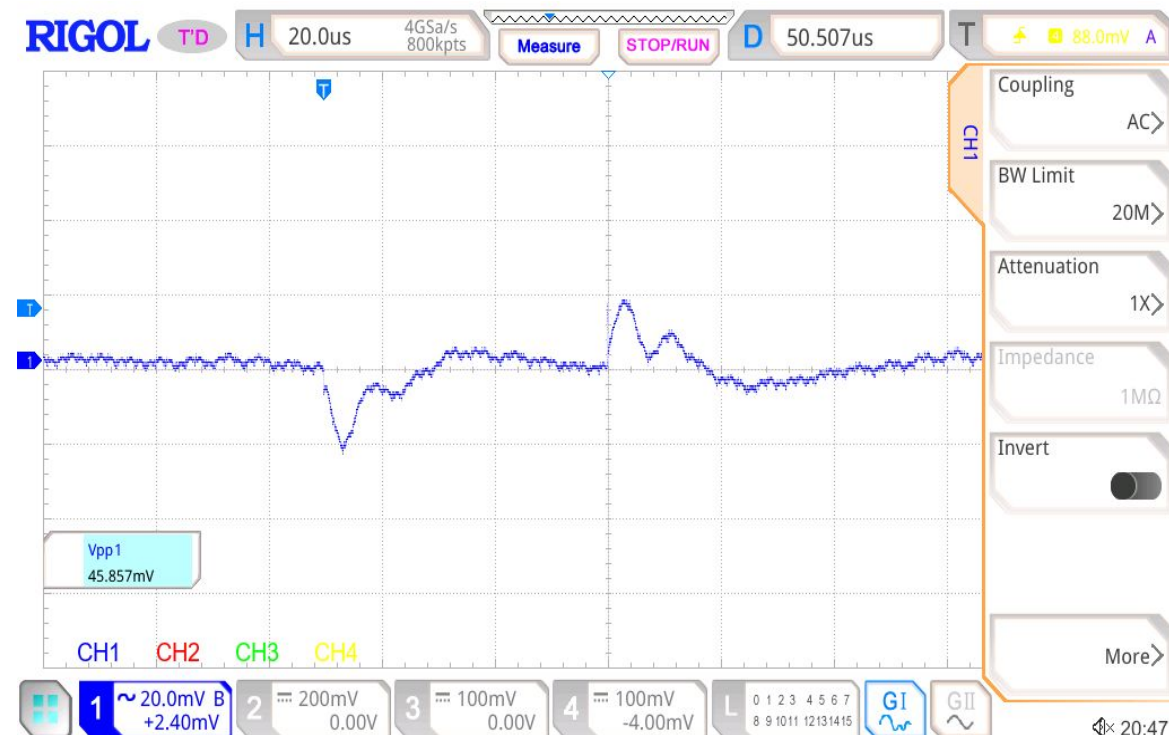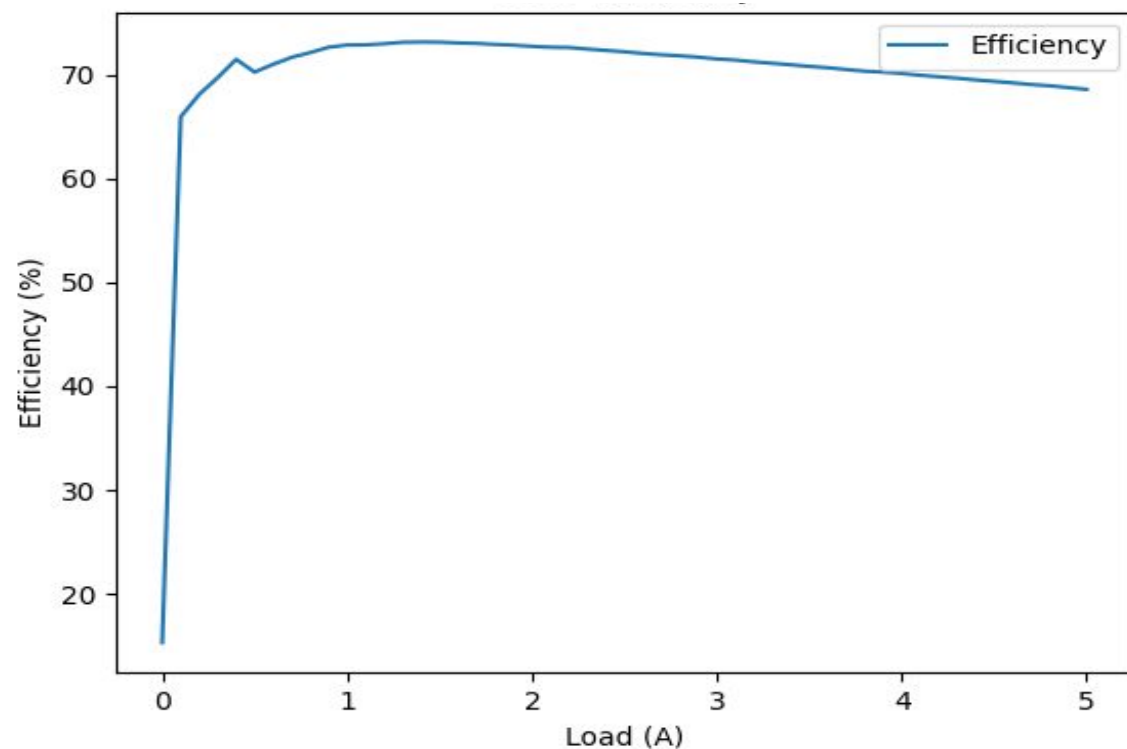


$V_{out} = 1.2\text{ V}$
 Transient 3.675 – 4.9A @ 10 A/ μ s
 $V_{PP} = 45.85\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 1.1\text{ }\mu\text{H}$, $C = 4 \times 47\text{ }\mu\text{F}$

Ripple

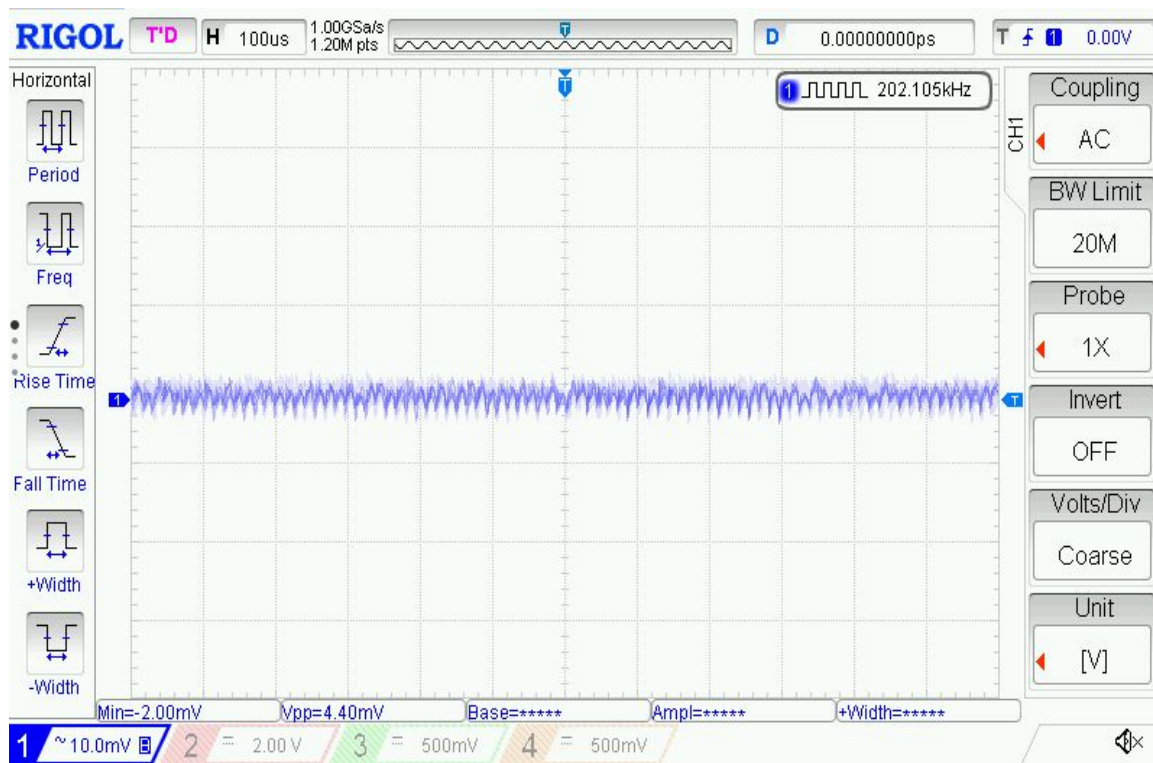

No Load
 $V_{PP} = 4.40 \text{ mV}$

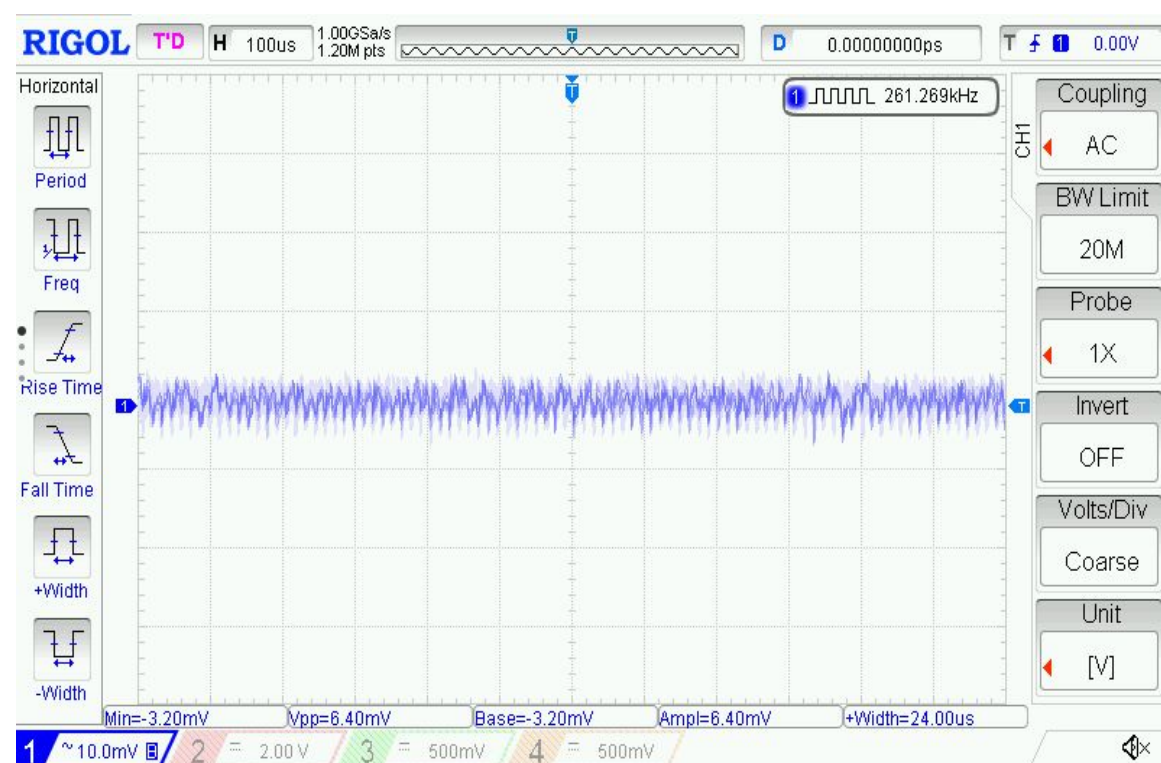

4.9 A Load
 $V_{PP} = 6.40 \text{ mV}$



$V_{out} = 1.2 \text{ V}$

VDDQ

1.2 V / 5 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1.1 \mu\text{H}$, P/N Wurth 744314110
- $C = 4 \times 47 \text{ uF}$

Efficiency & Transient

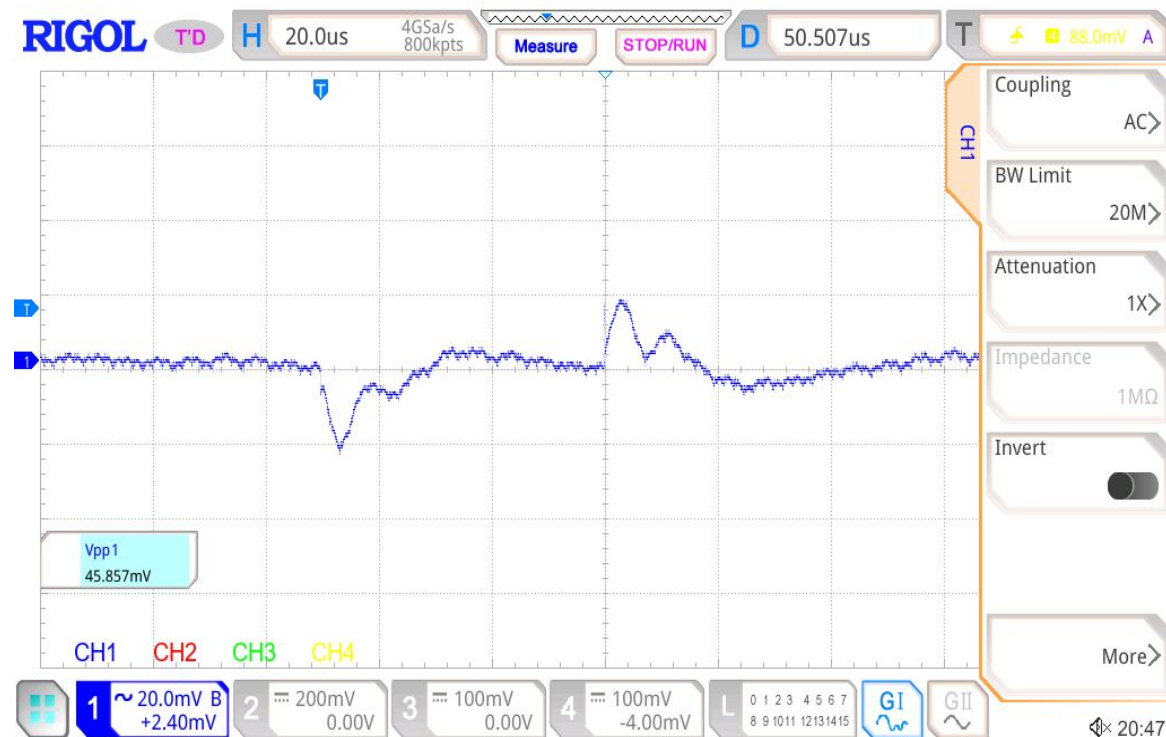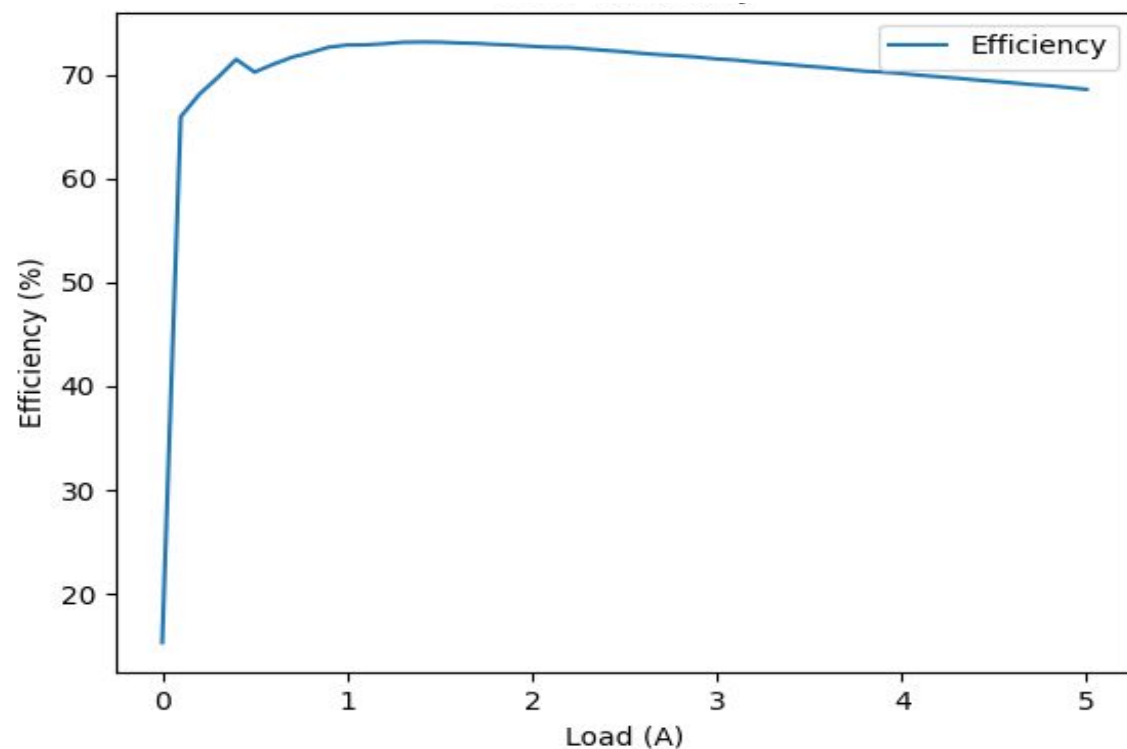


$V_{out} = 1.2\text{ V}$
Transient 3.75 – 5A @ 10 A/ μ s
 $V_{PP} = 45.85\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 1.1\text{ }\mu\text{H}$, $C = 4 \times 47\text{ }\mu\text{F}$

Ripple

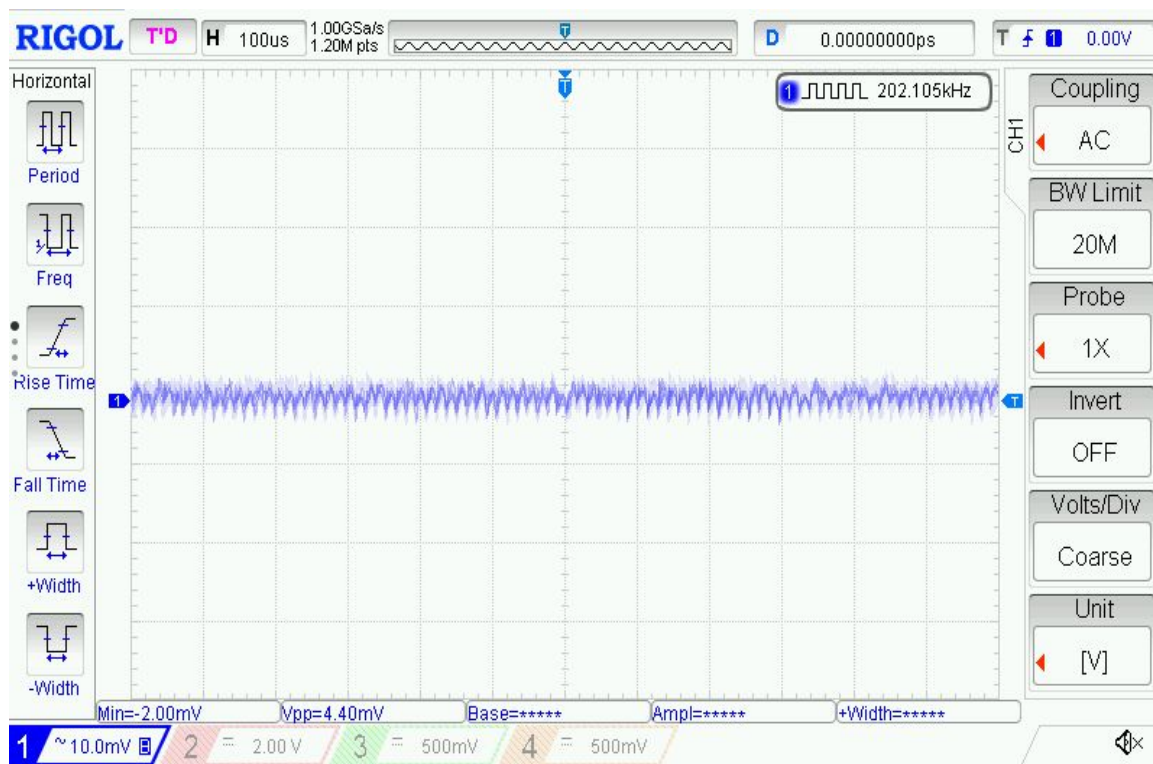

No Load
 $V_{PP} = 4.40 \text{ mV}$

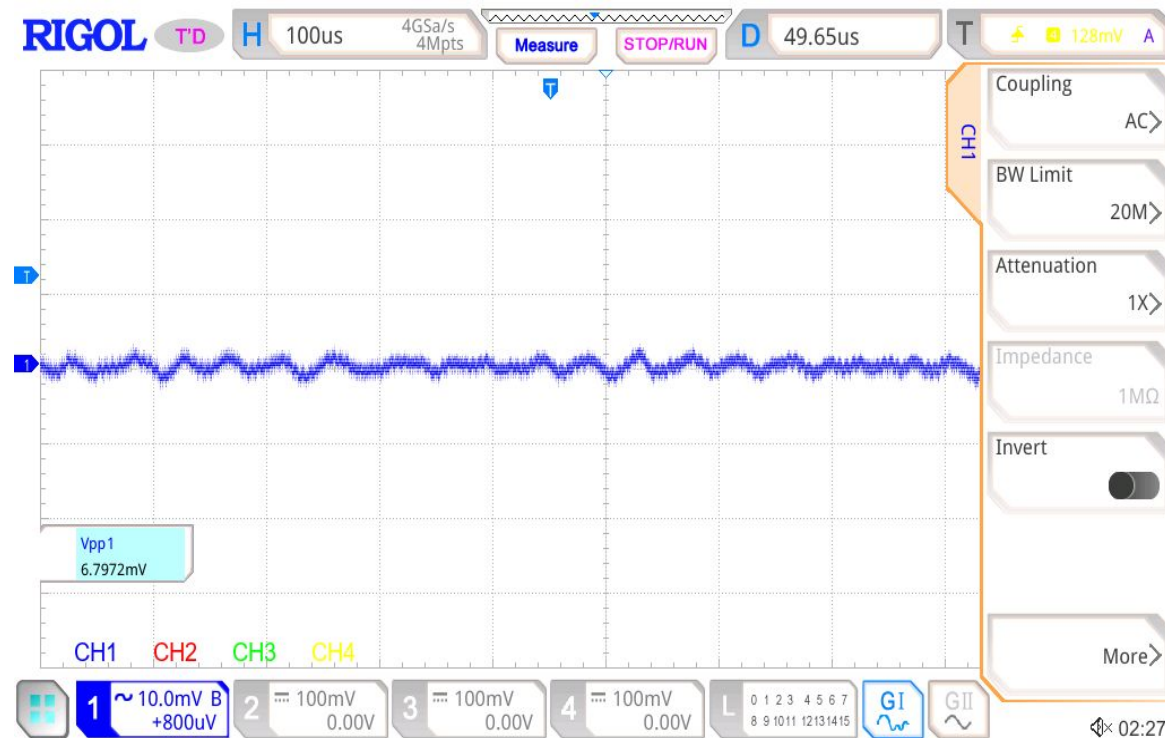

$V_{out} = 1.2 \text{ V}$


5 A Load
 $V_{PP} = 6.79 \text{ mV}$

VTT


0.6 V / 2 A

- C210 (VTT Terminator)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.33 \text{ } \mu\text{H}$, P/N Wurth 744393440033
- $C = 8 \times 47 \text{ } \mu\text{F}$


Efficiency & Transient

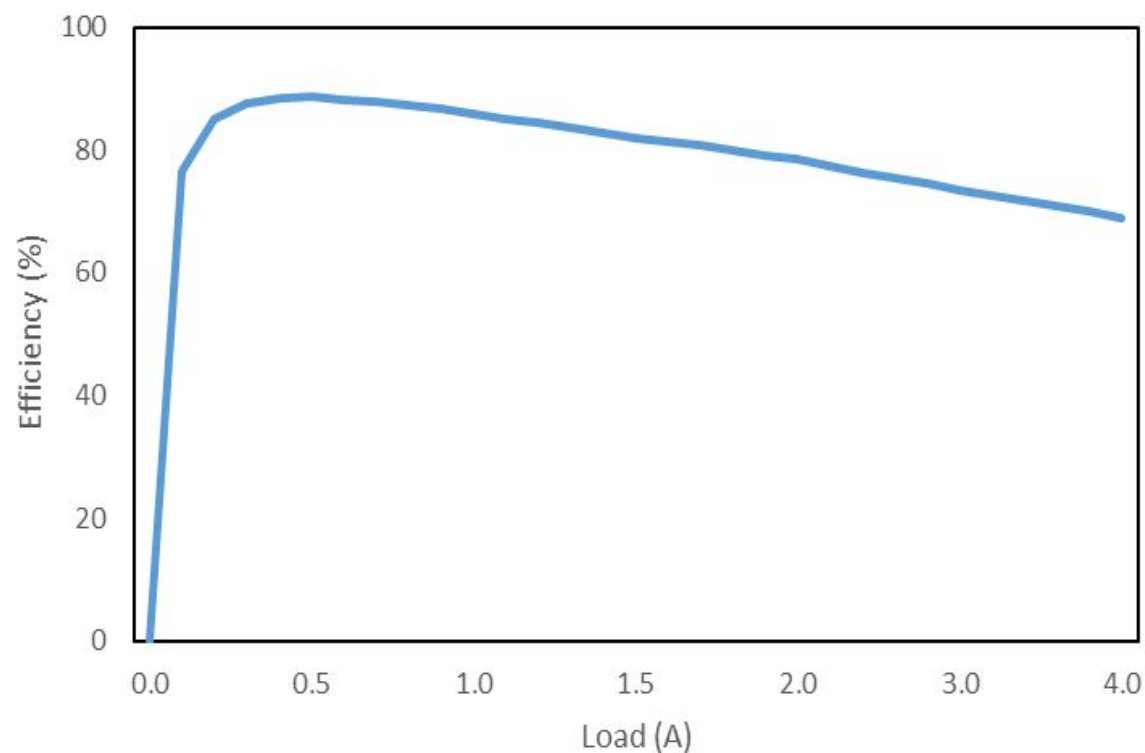

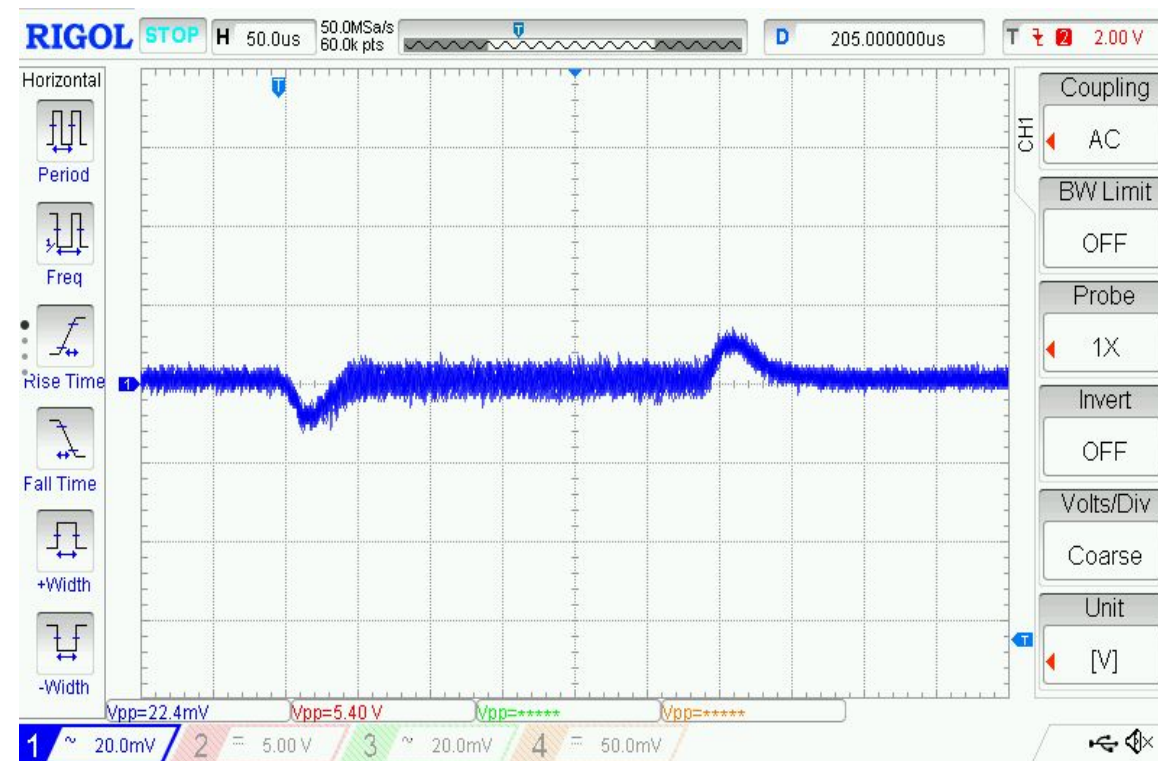
Vout = 0.6V
Transient 3 – 4A @ 10 A/ μ s
 $V_{PP} = 22.4$ mV
Fsw = 1 MHz
L = 0.33 μ H, C = 8x47 μ F




Ripple

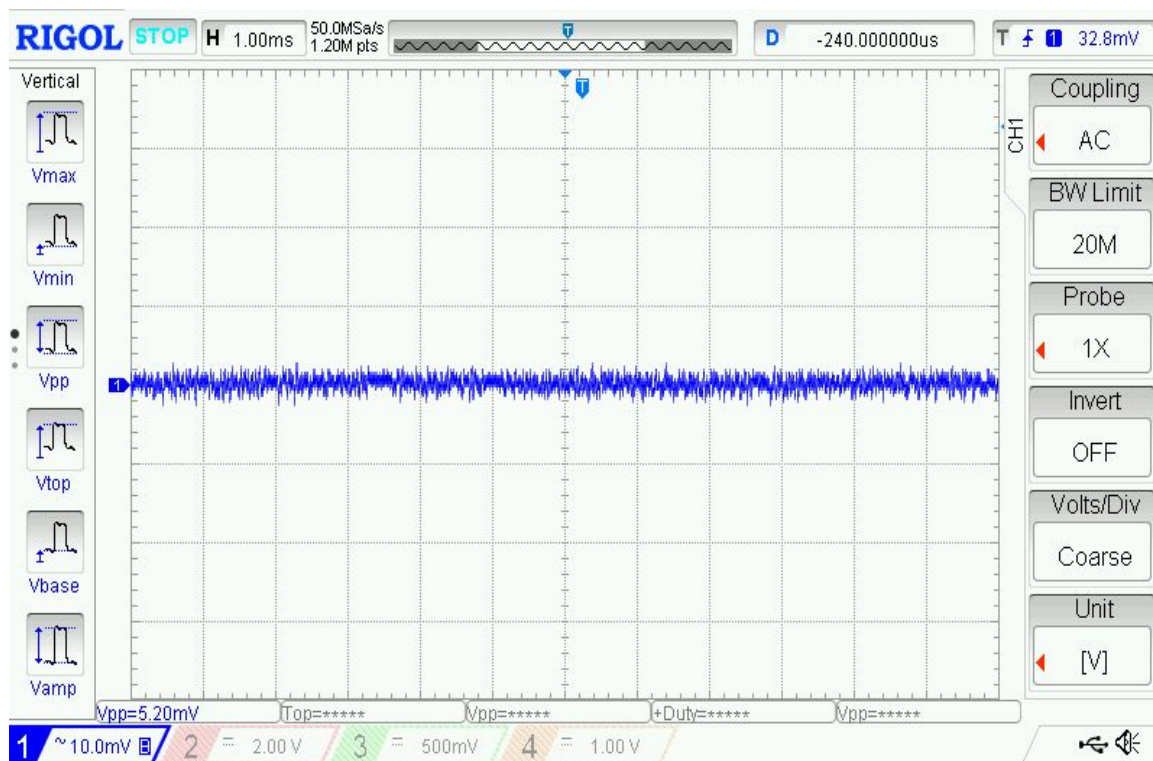

No Load
 $V_{PP} = 5.20 \text{ mV}$

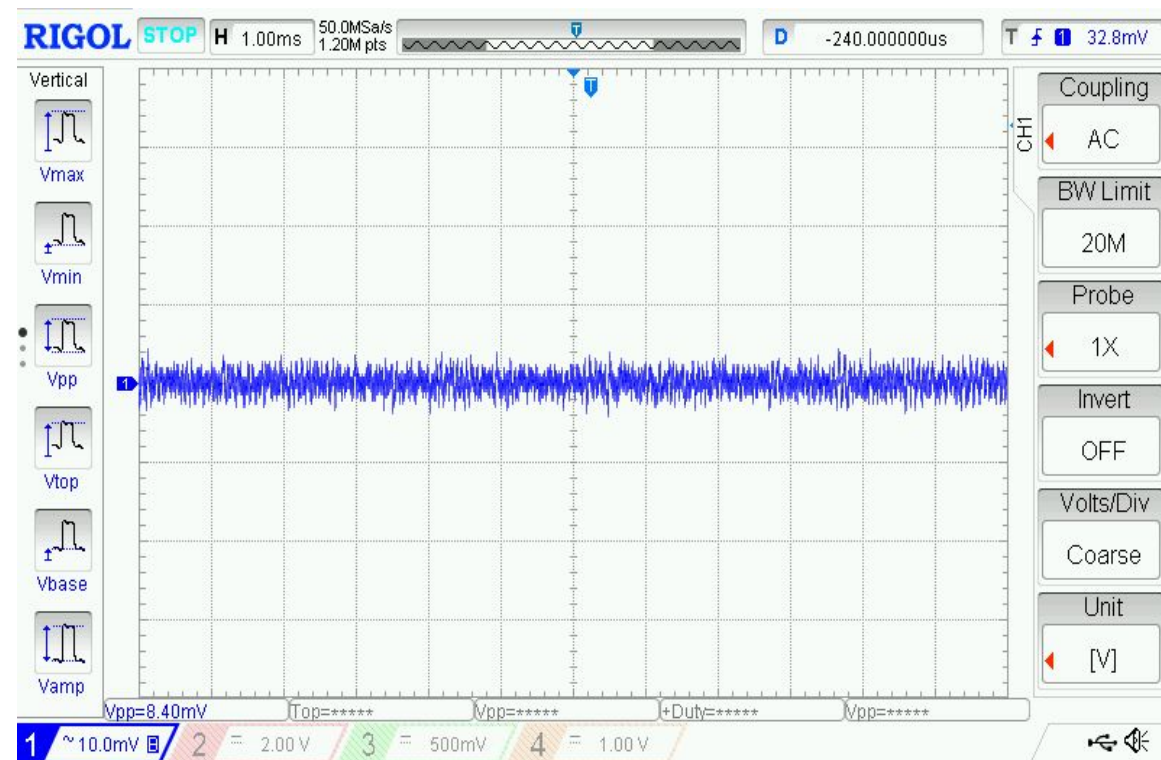

4 A Load
 $V_{PP} = 8.40 \text{ mV}$

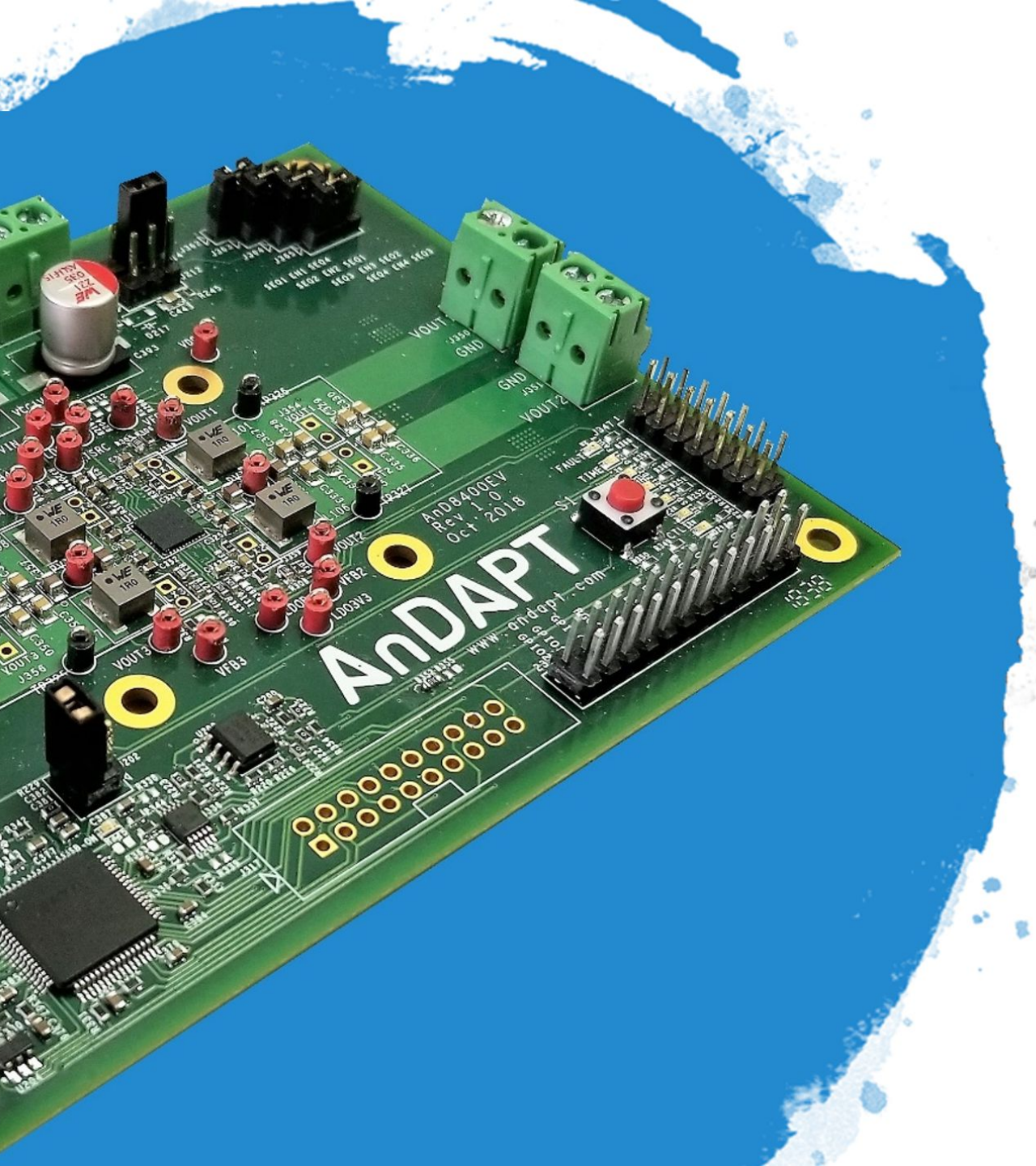

Thank You