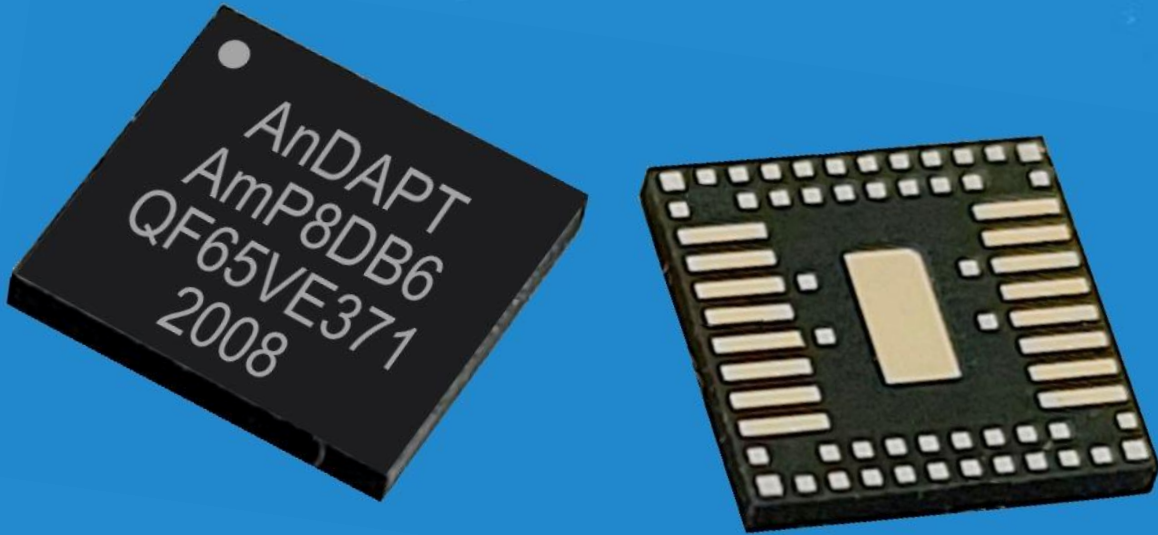


Xilinx Versal Premium –M Devices (Minimum Rails) Lower Loading Use-case

Power Mappings




Contents

- Versal Premium power maps
- AnDAPT integrated power supply design
- Bench data including efficiency, transients, ripple (no load and full-load) for each power rail
- AnDAPT PMICs meet or exceed all power performance specs provided by Xilinx

Xilinx Versal Premium Power Tree

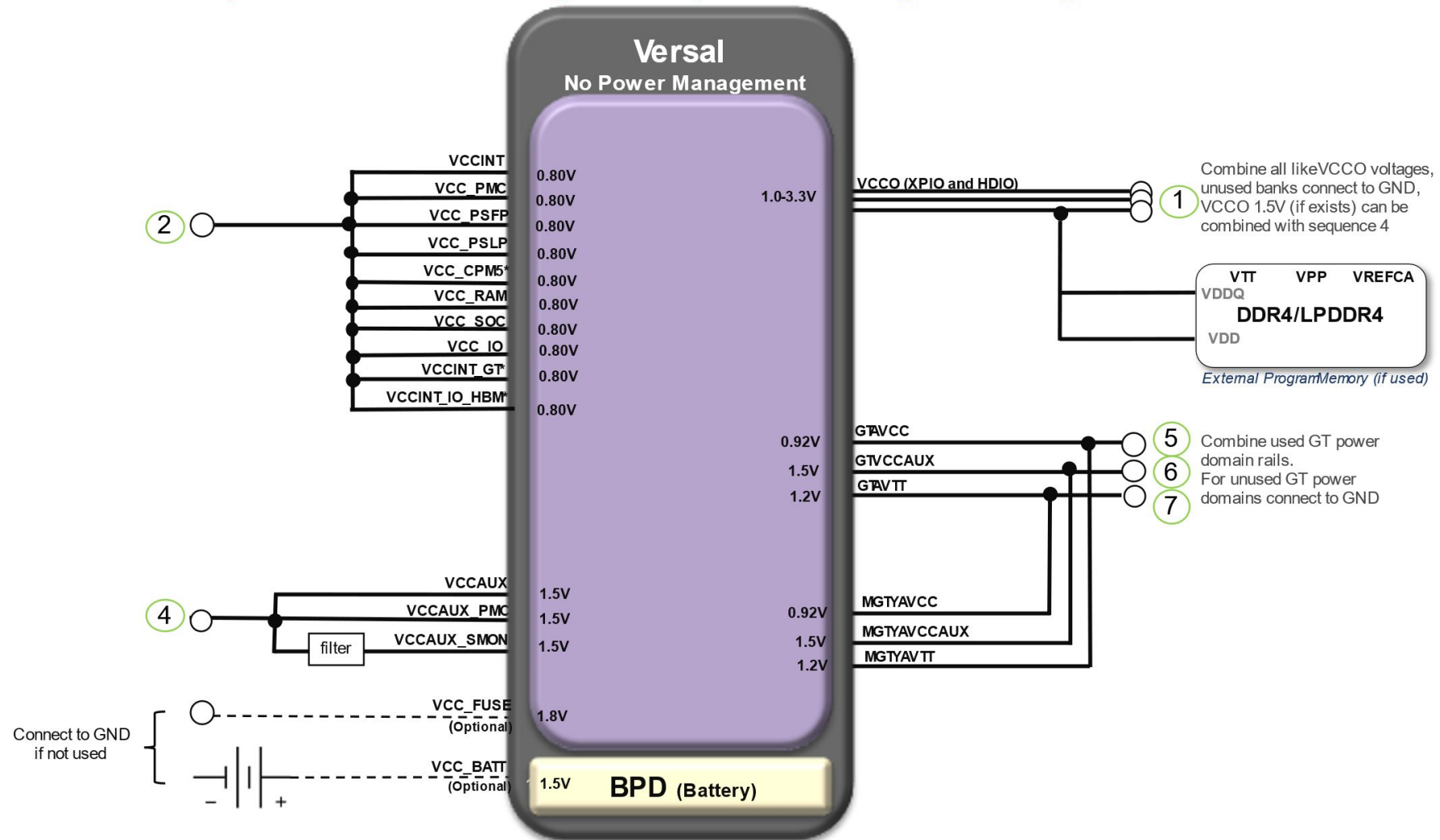Minimum Rails (No Power Management) – Mid/High Voltage





Power Tree Mapping: Versal Premium –M (Minimum Rails, Lower Loading)


#	Rail	Seq	Power Component	Type	Upstream Rail	Vinput (V)	Vout (V)	Iout (A)	AnDAPT PMIC
1	VCCO_HDIO (VCCO_HDIO, VCCO_500, VCCO_501, VCCO_502, VCCO_503)	1	C200	Integ. Sync Buck	PVIN	12	1.8	0.1-3	ARD_X_VRPM_A_IC1
2	VCCO_XPIO	1	C200	Integ. Sync Buck	PVIN	12	1.5	0.1-3	
3	VCCINT (VCCINT, VCC_PMC, VCC_PSLP, VCC_PSLP, VCC_CPM5, VCC_RAM, VCC_GT, VCC_SOC, VCC_IO)	2	Ext.	Ext.	PVIN	12	0.8/0.88	80-180	
4	VCCAUX (VCCAUX, VCCAUX_PMC, VCCAUX_SMON)	2	C200	Integ. Sync Buck	PVIN	12	1.5	1.5-10	
5	MGTYAVCC (MGTYAVCC, GTAVCC)	3	C200	Sync Buck	PVIN	12	0.88/0.92	6-15	ARD_X_VRPM_A_IC2
6	MGTYAVCCAUX (MGTYAVCCAUX, GTAVCCAUX)	4	C200	Integ. Sync Buck	PVIN	12	1.5	1	
7	MGTYAVTT (MGTYAVTT, GTAVTT)	5	C220	Sync Buck High Current	PVIN	12	1.2	8-24	

PVIN = 12V


Power Tree Mapping- Design Lower Loading

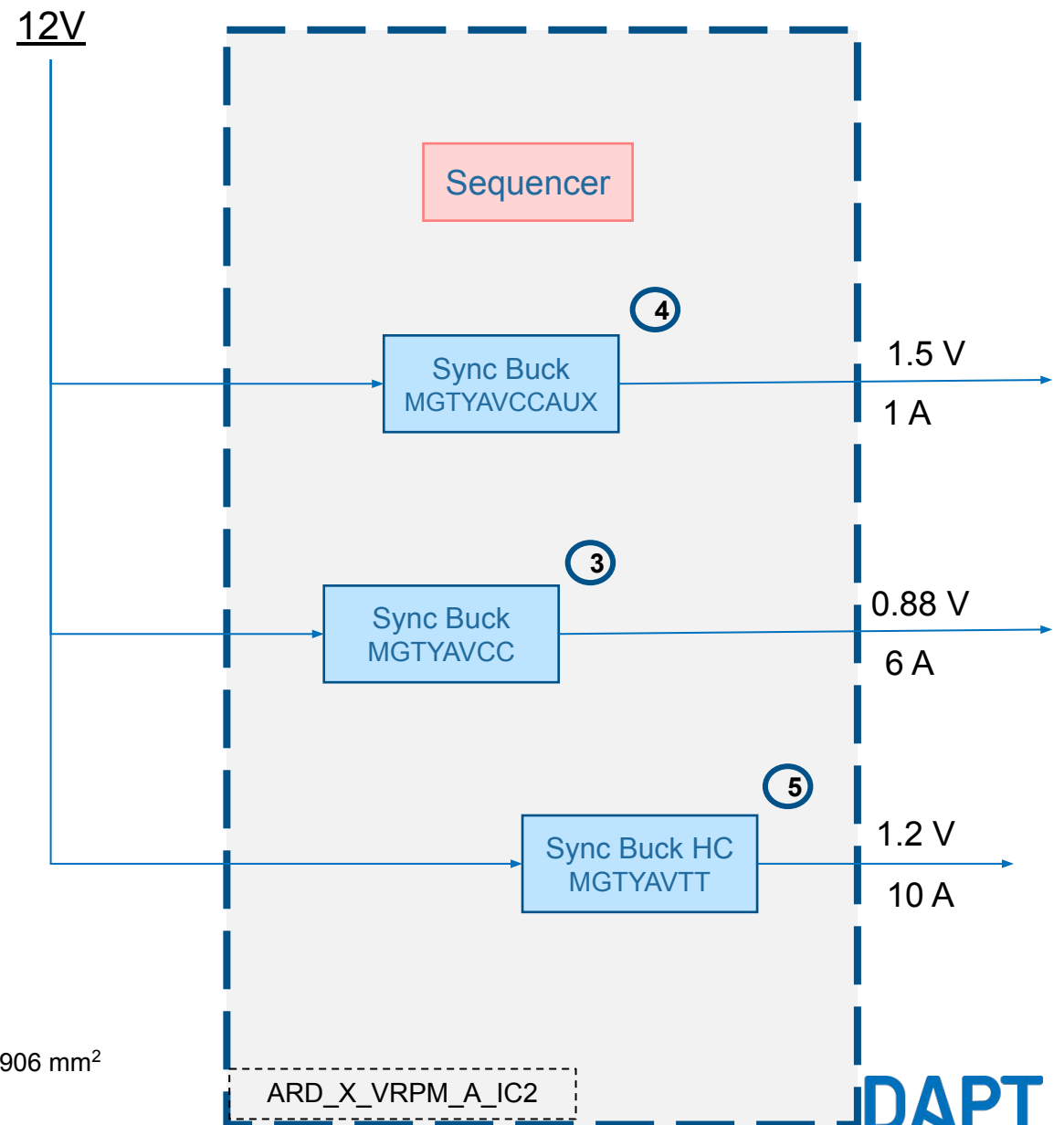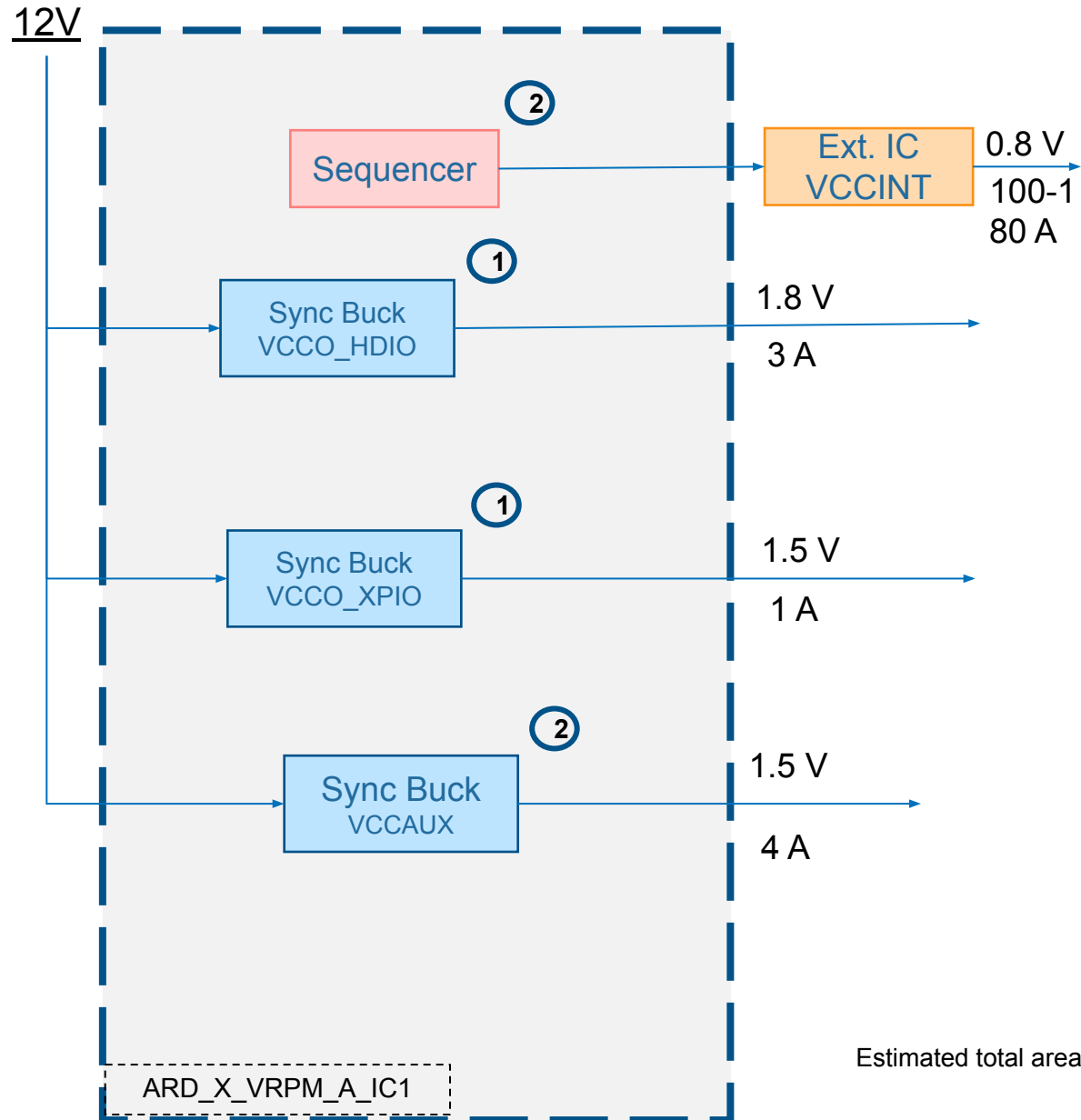

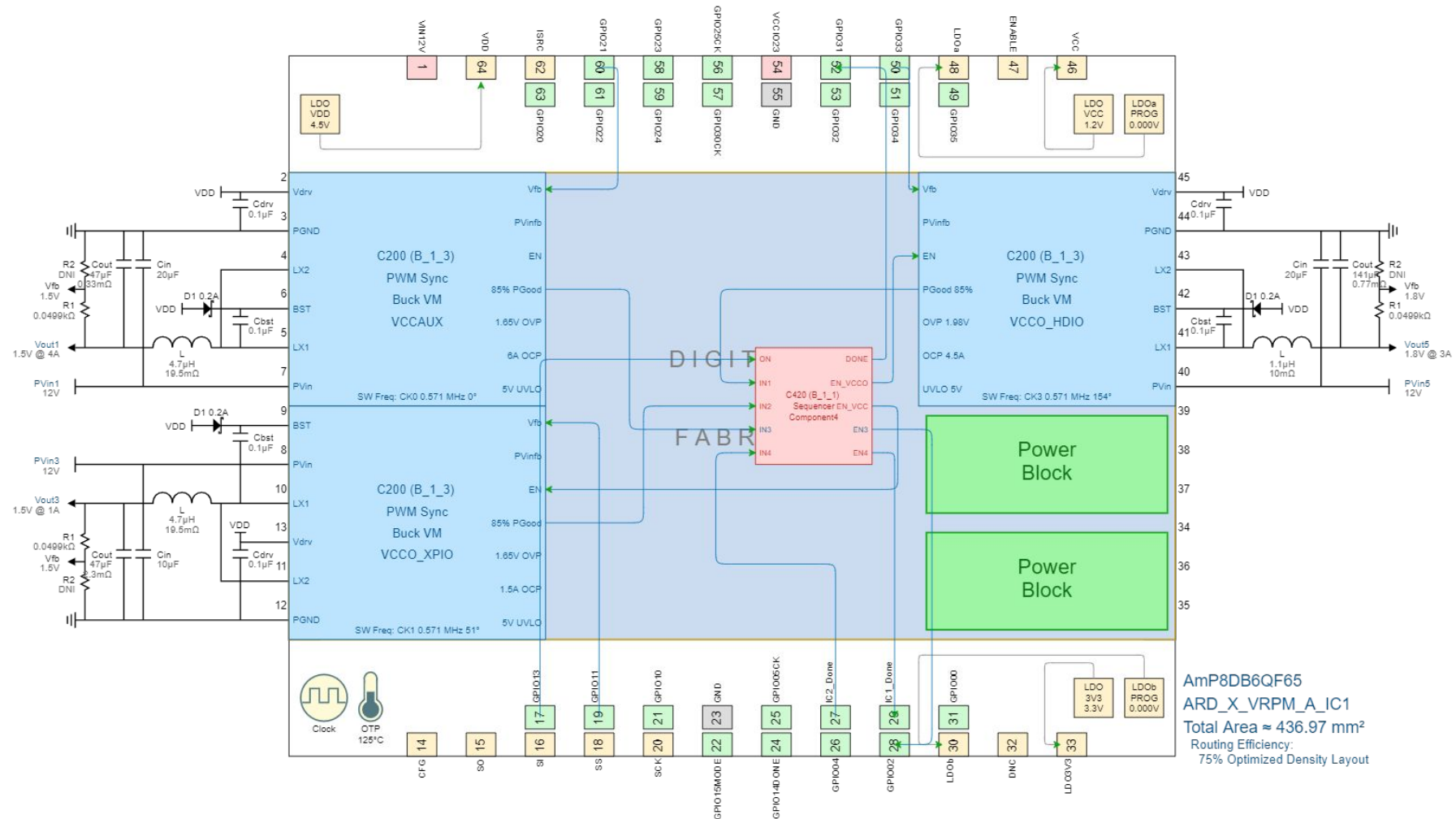
Mapping (WebAmP View) Design Lower Loading –IC1




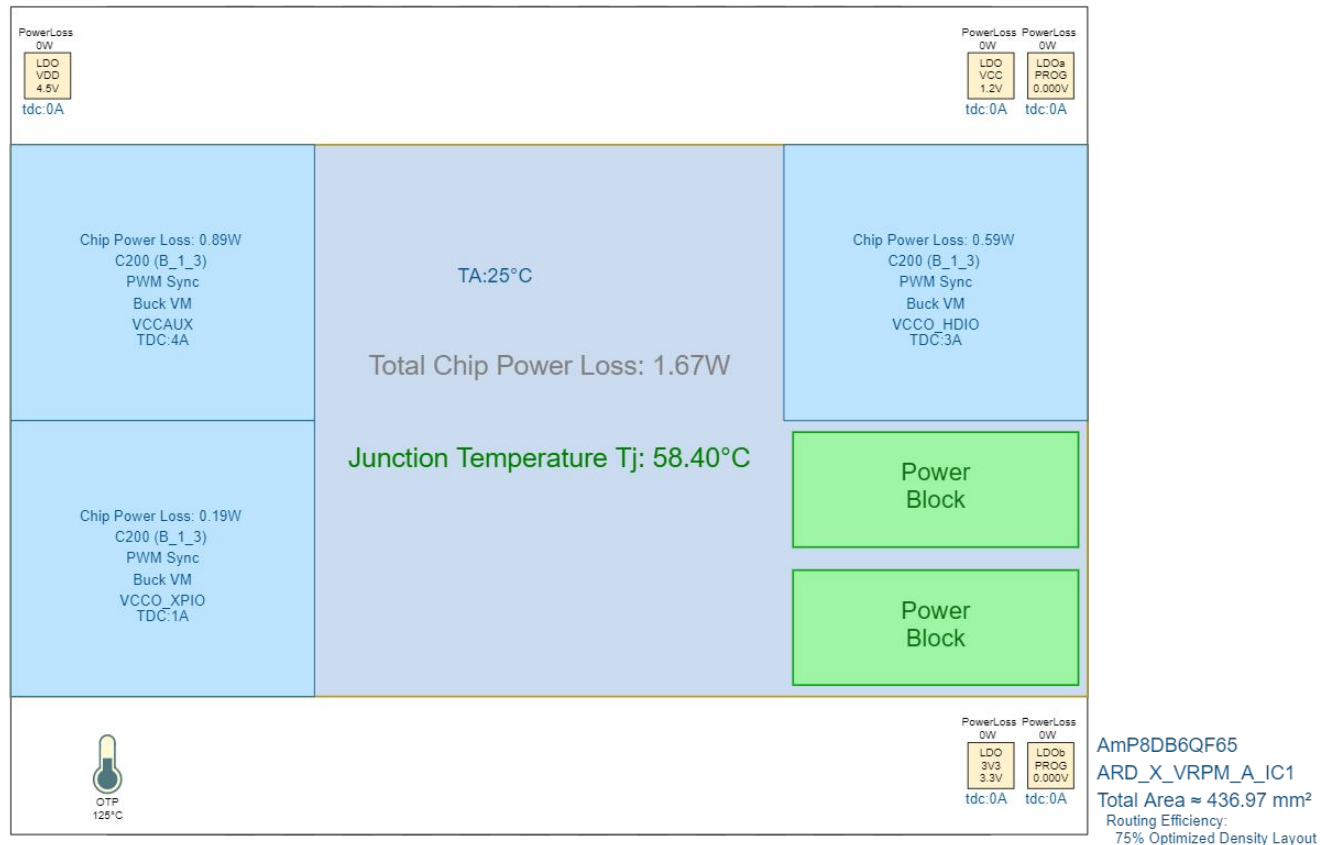Mapping (Thermal View) Design Lower Loading –IC1



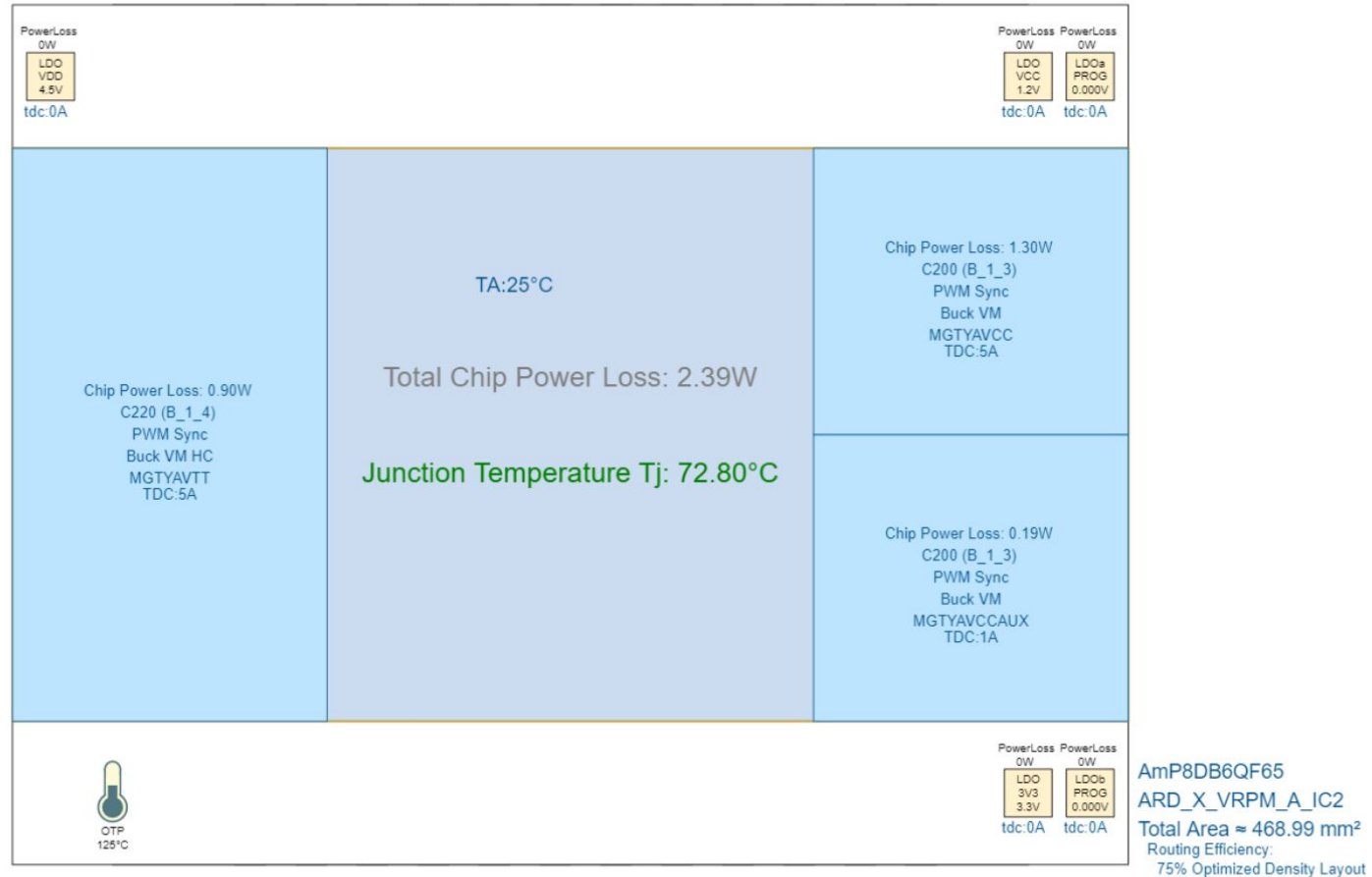Mapping (Thermal View) Design Lower Loading –IC2



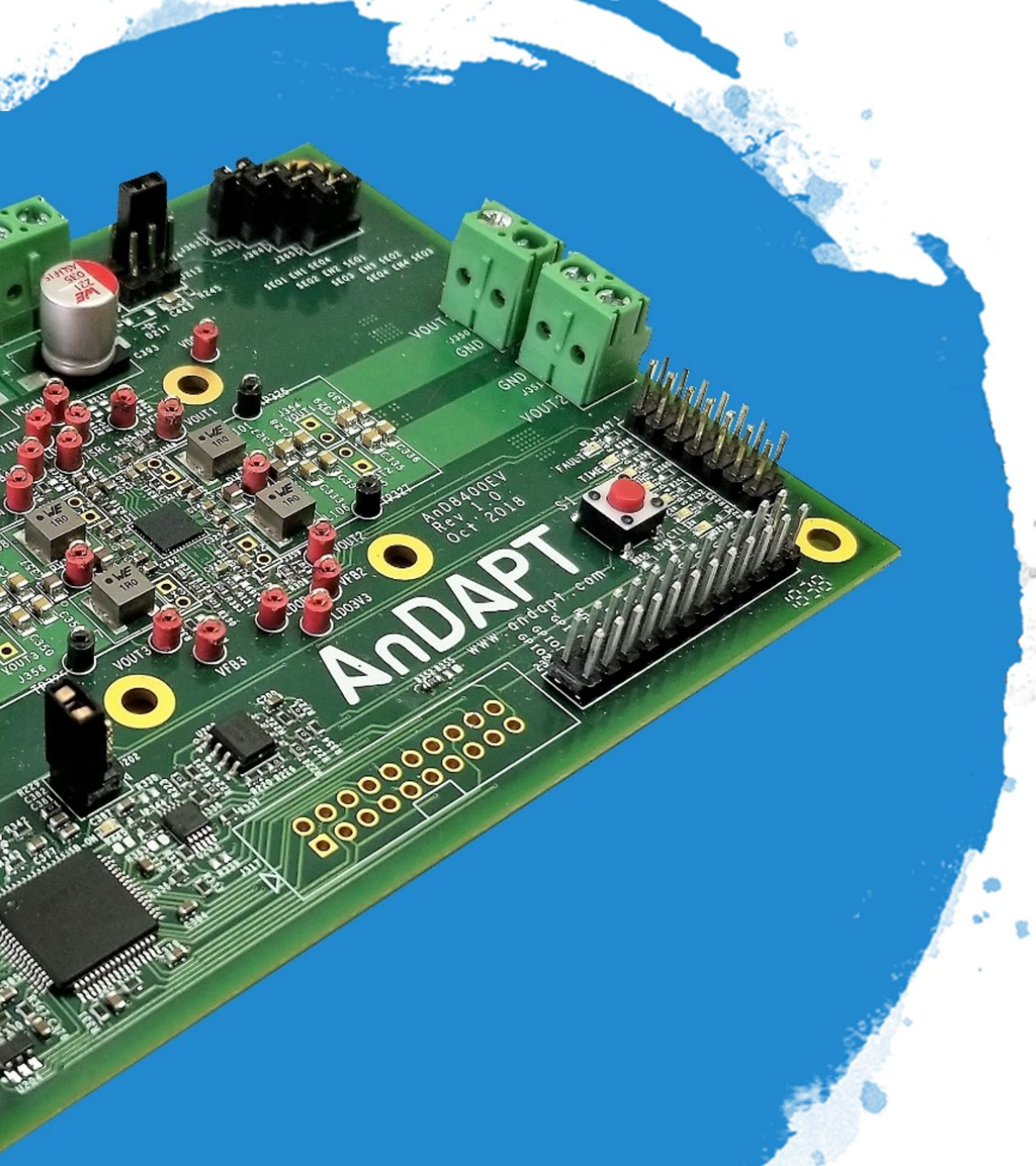

Test Data



Xilinx Versal Premium - M

VCCO_HDIO

1.8 V / 3 A


- C200 (Synchronous buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1.1 \mu\text{H}$, P/N Wurth 744314110
- $C = 3 \times 47 \mu\text{F}$

Efficiency & Transient

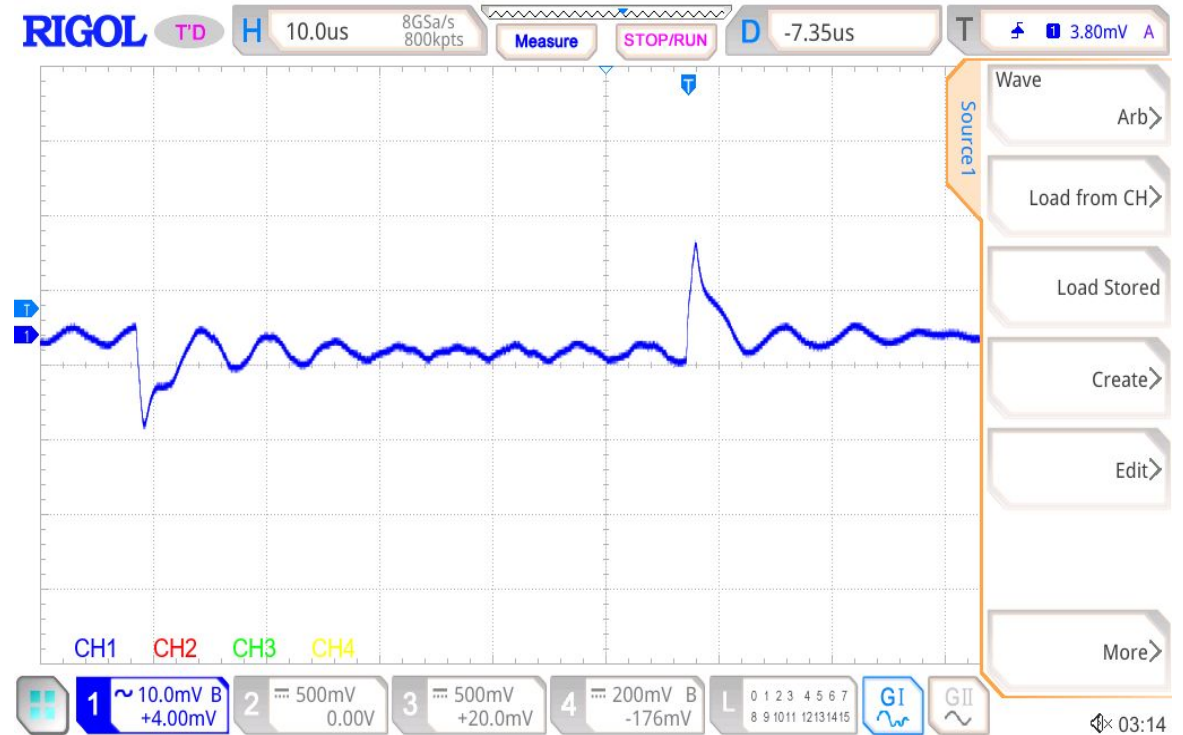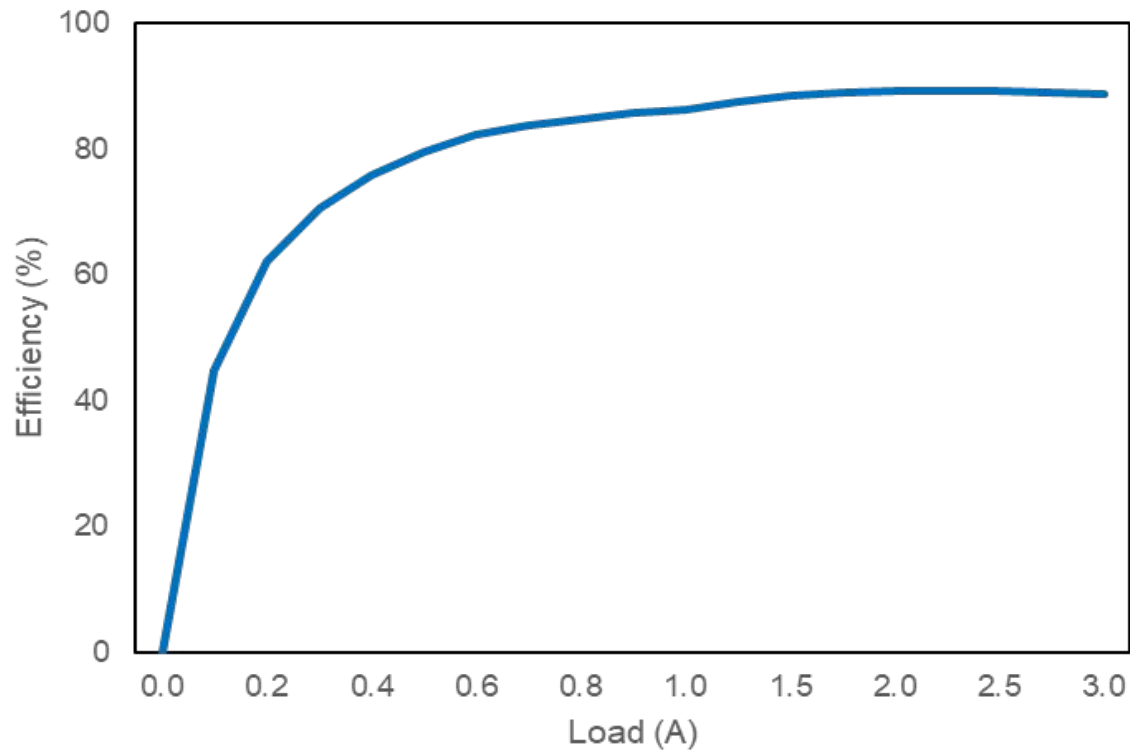


Vout = 1.8V
Transient 0A – 3 A@10 A/ μ s
 V_{PP} = 32 mV
Fsw = 0.571 MHz
L = 1.1 μ H, C = 3x47 uF

Ripple

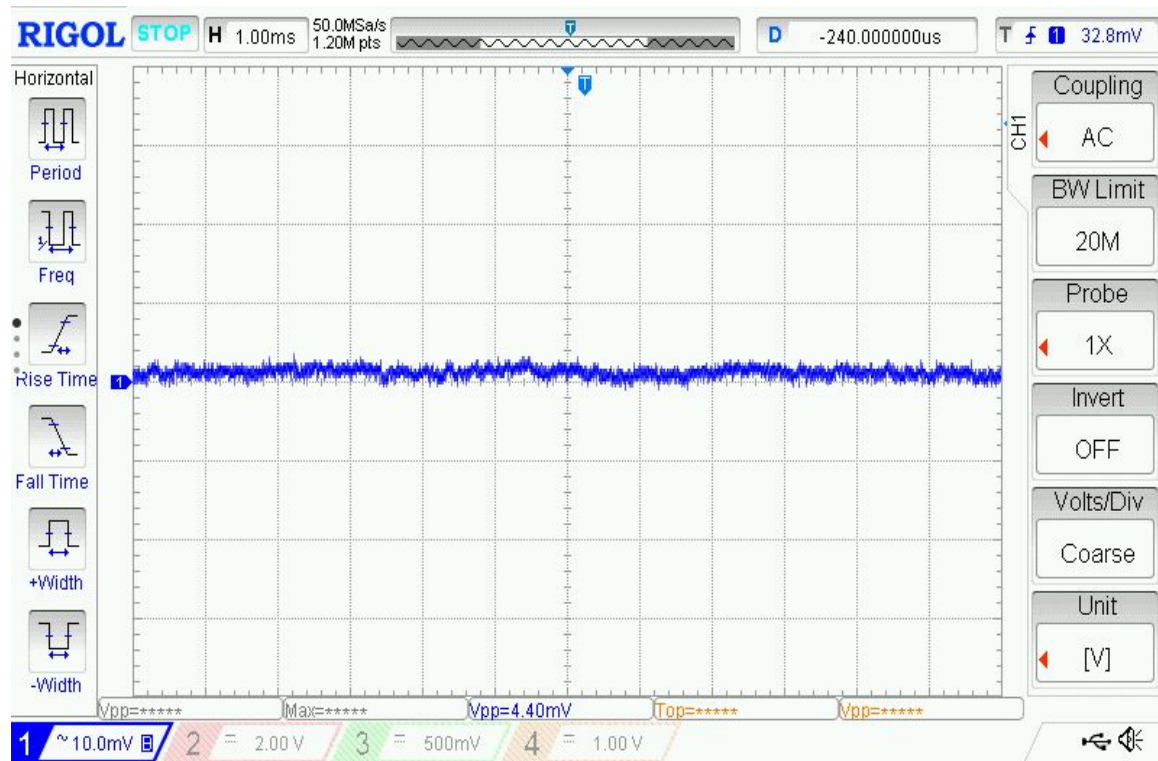

No Load
 $V_{PP} = 4.40 \text{ mV}$

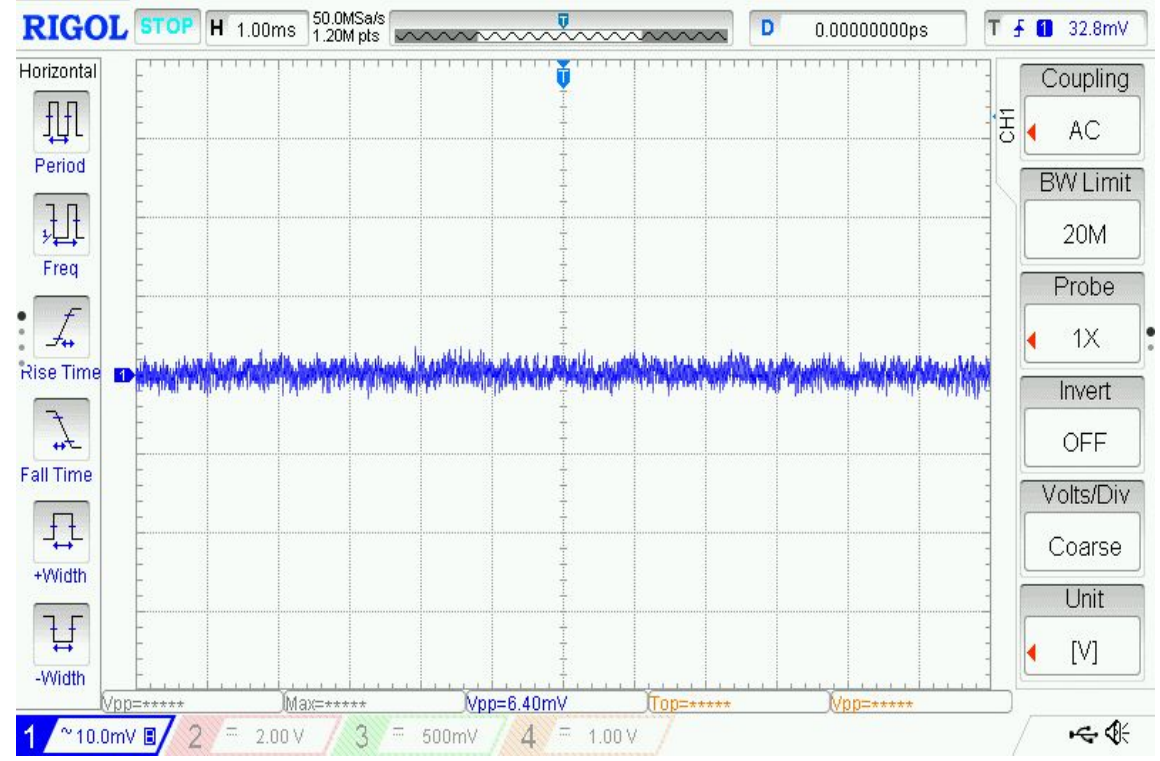

3 A Load
 $V_{PP} = 6.4 \text{ mV}$



$V_{out} = 1.8 \text{ V}$

VCCO_XPIO

1.5 V / 1 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \mu\text{F}$

Efficiency & Transient

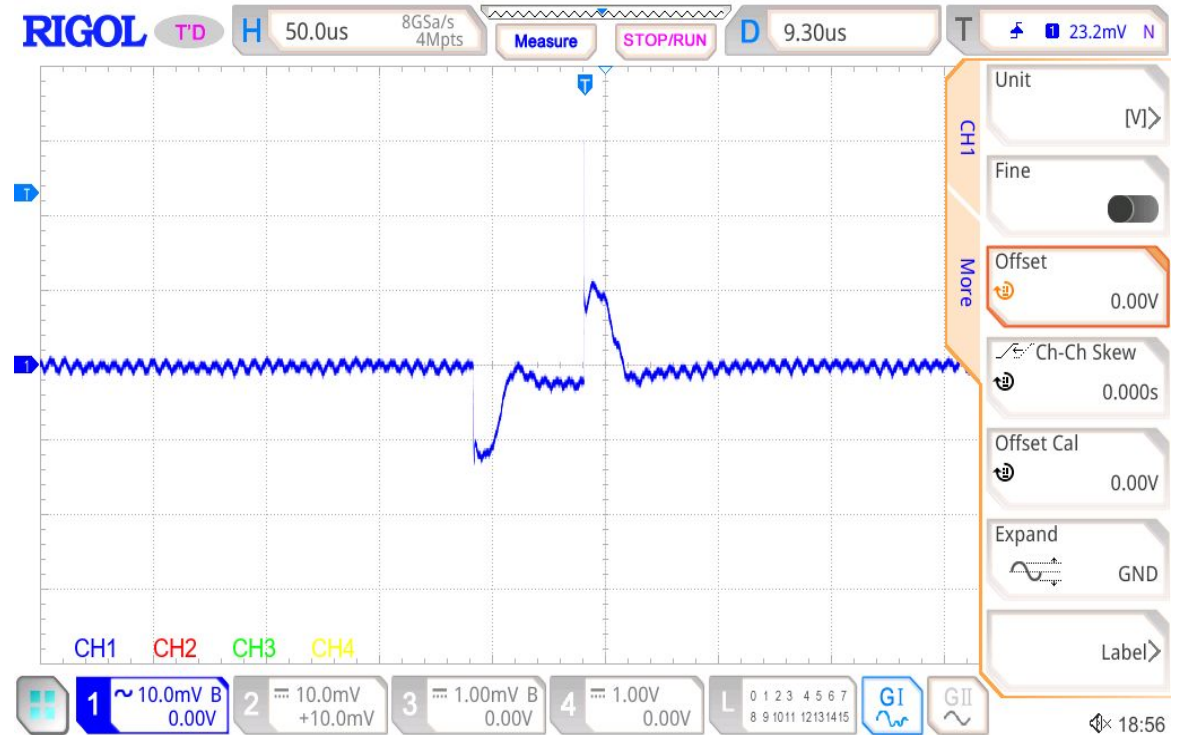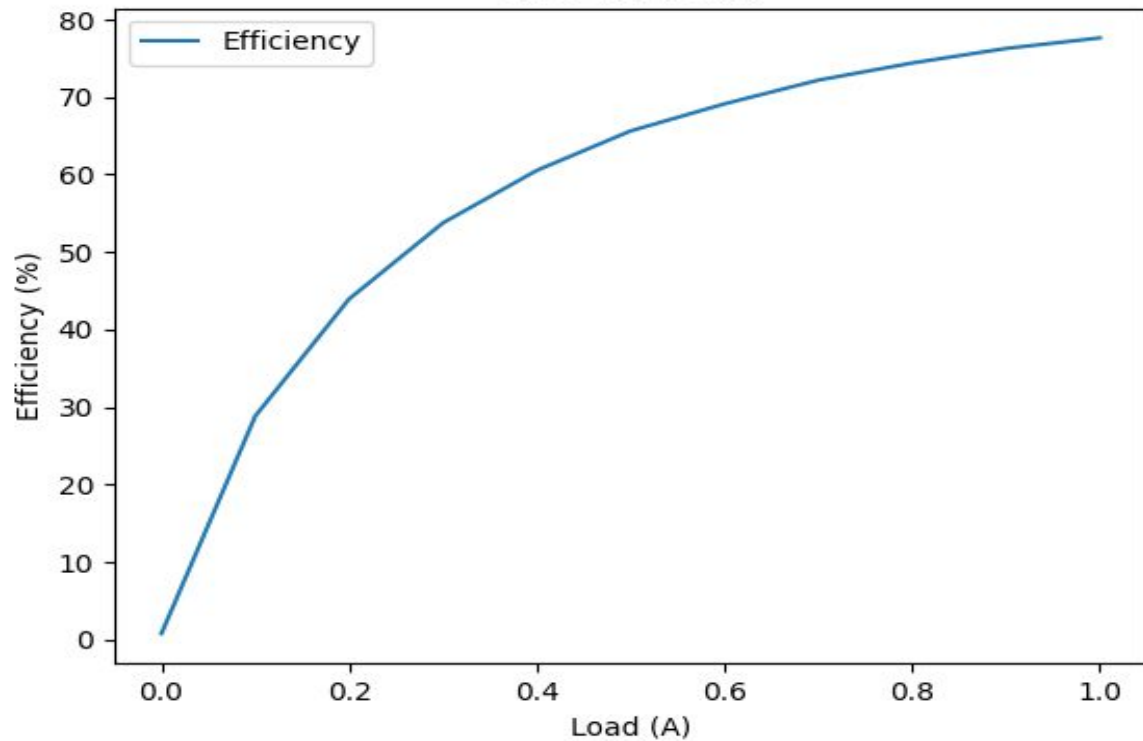


Vout = 1.5V
Transient 0.67 – 1 A@10 A/μs
V_{PP} = 24 mV
Fsw = 0.571 MHz
L = 4.7 μH, C = 1x47 uF

Ripple

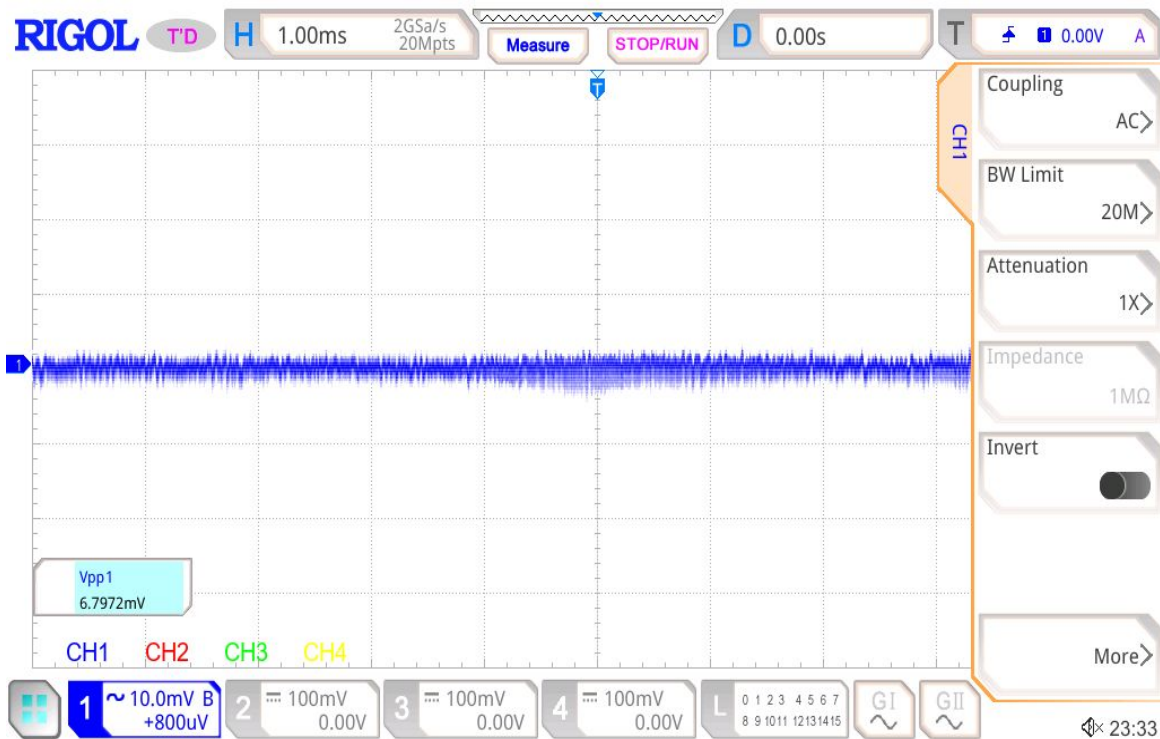

No Load
 $V_{PP} = 6.79 \text{ mV}$

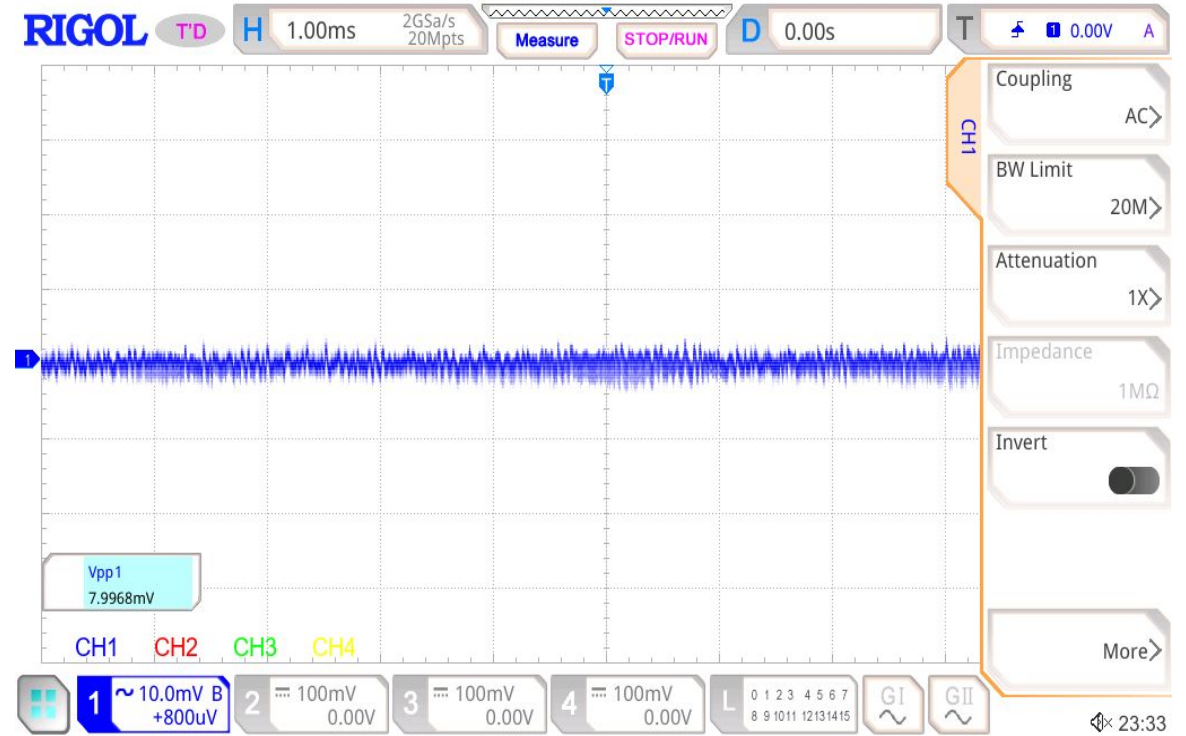

1 A Load
 $V_{PP} = 7.99 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

VCCAUX

1.5 V / 4 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \mu\text{F}$

Efficiency & Transient

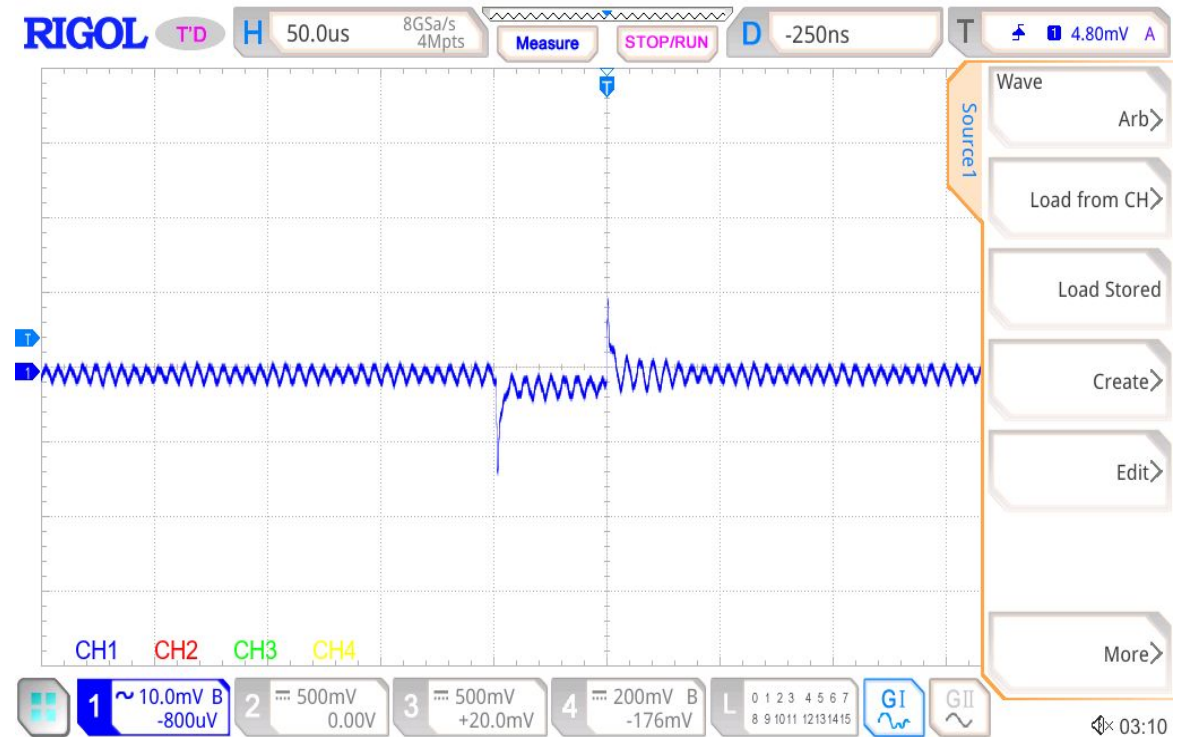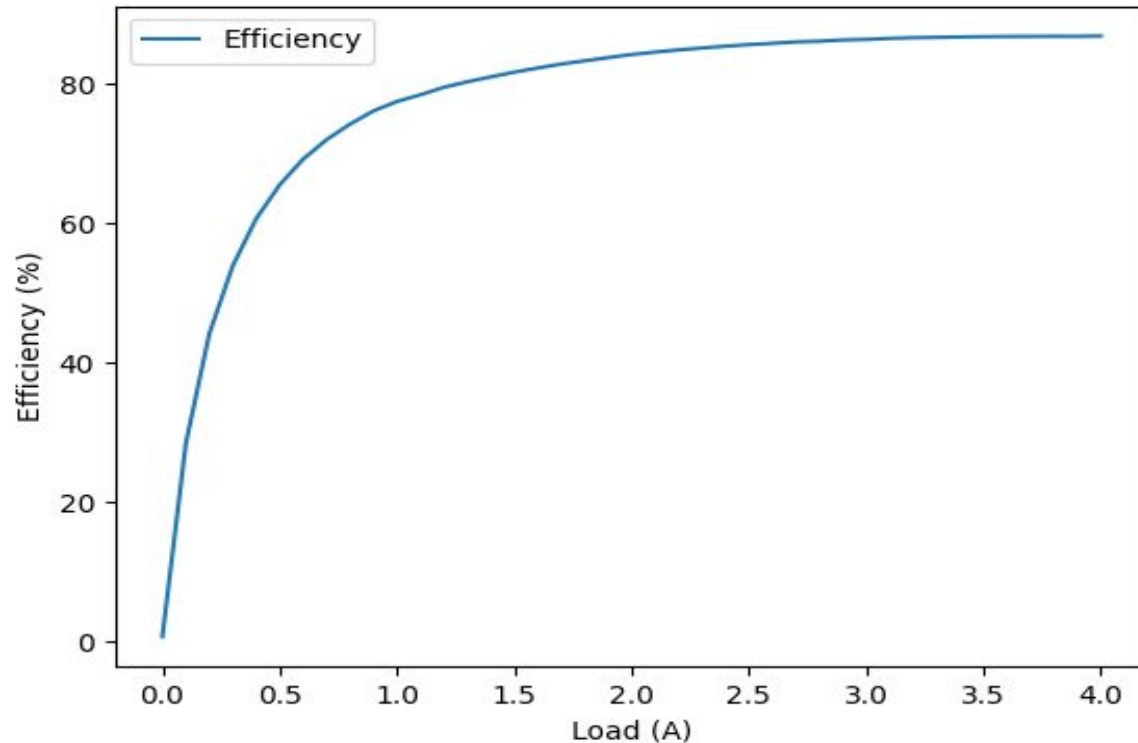


Vout = 1.5V
Transient 2.68A – 4A @ 10 A/ μ s
 V_{PP} = 25 mV
Fsw = 0.571 MHz
L = 4.7 μ H, C = 1x47 uF

Ripple

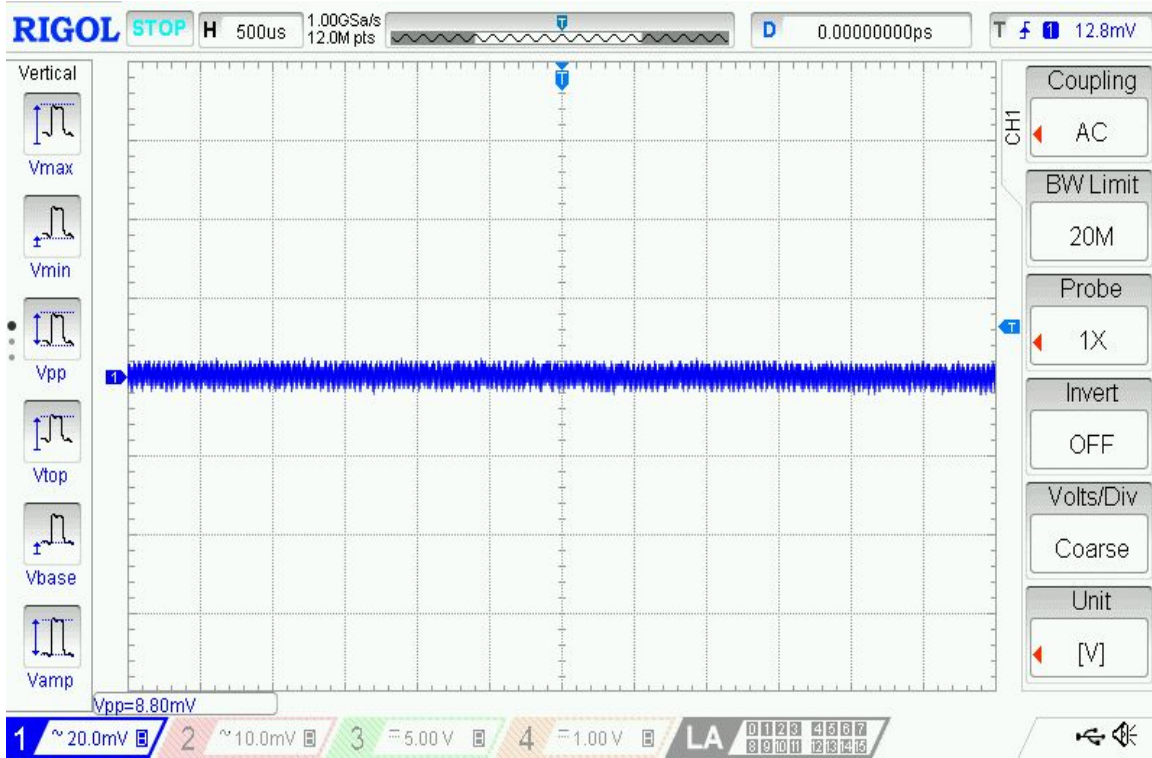

No Load
 $V_{PP} = 8.80 \text{ mV}$

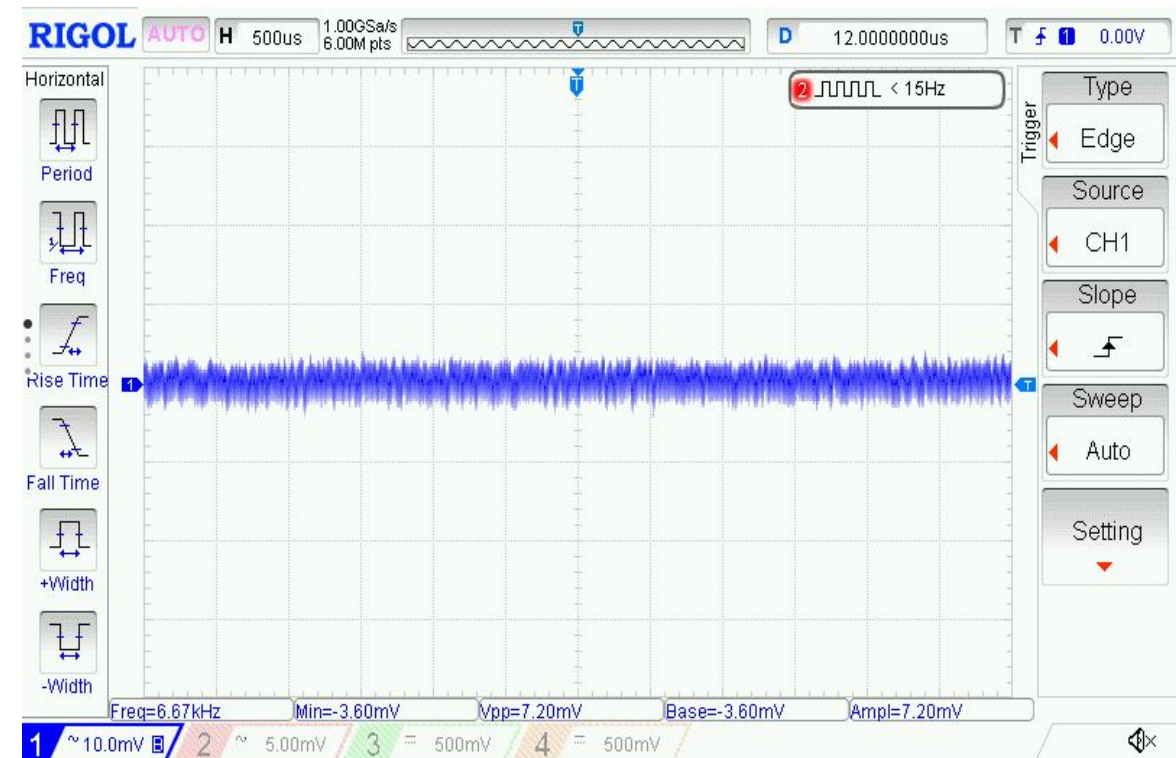

4 A Load
 $V_{PP} = 7.20 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

MGTYAVCCAUX

1.5 V / 1 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \mu\text{F}$

Efficiency & Transient

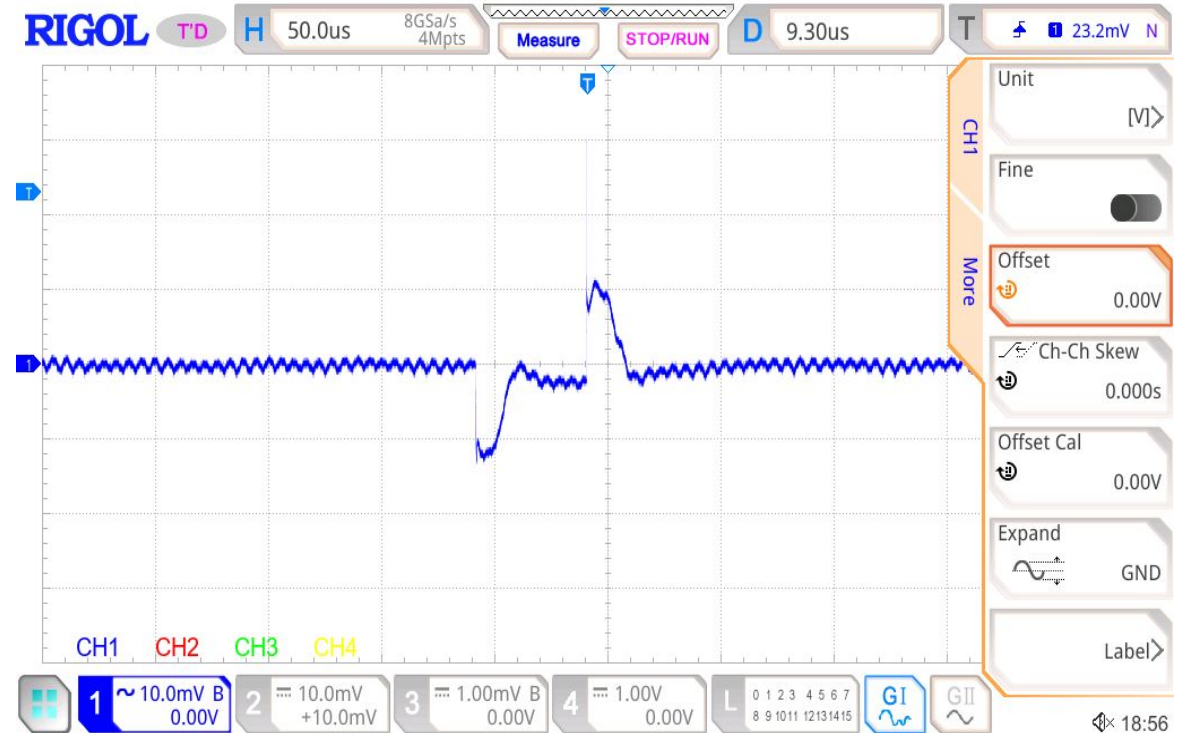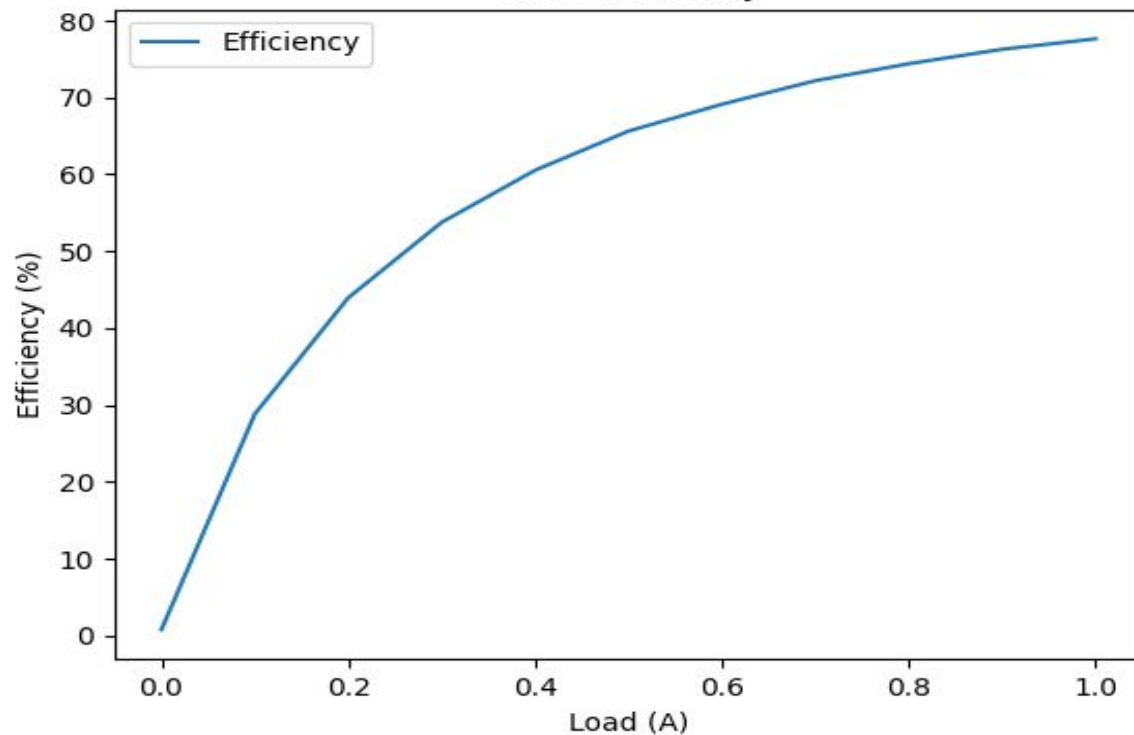


Vout = 1.5V
Transient 0.67 – 1 A@10 A/ μ s
V_{PP} = 30 mV
Fsw = 0.571 MHz
L = 4.7 μ H, C = 1x47 uF

Ripple

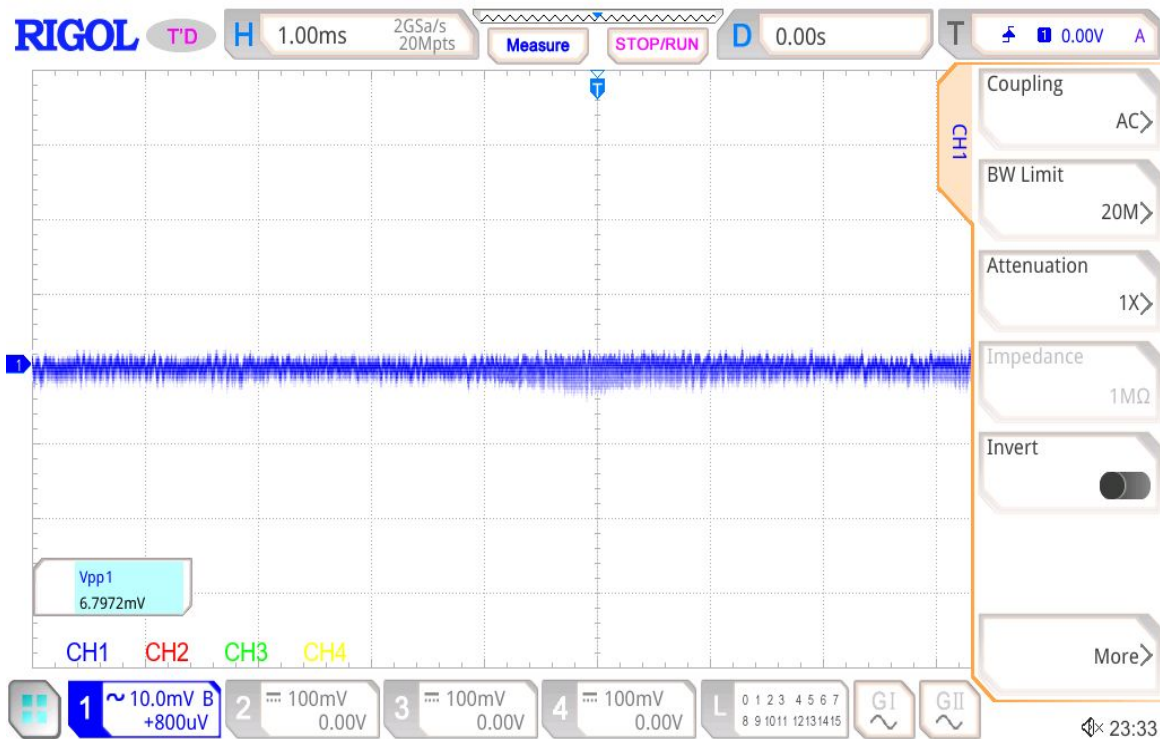

No Load
 $V_{PP} = 6.79 \text{ mV}$

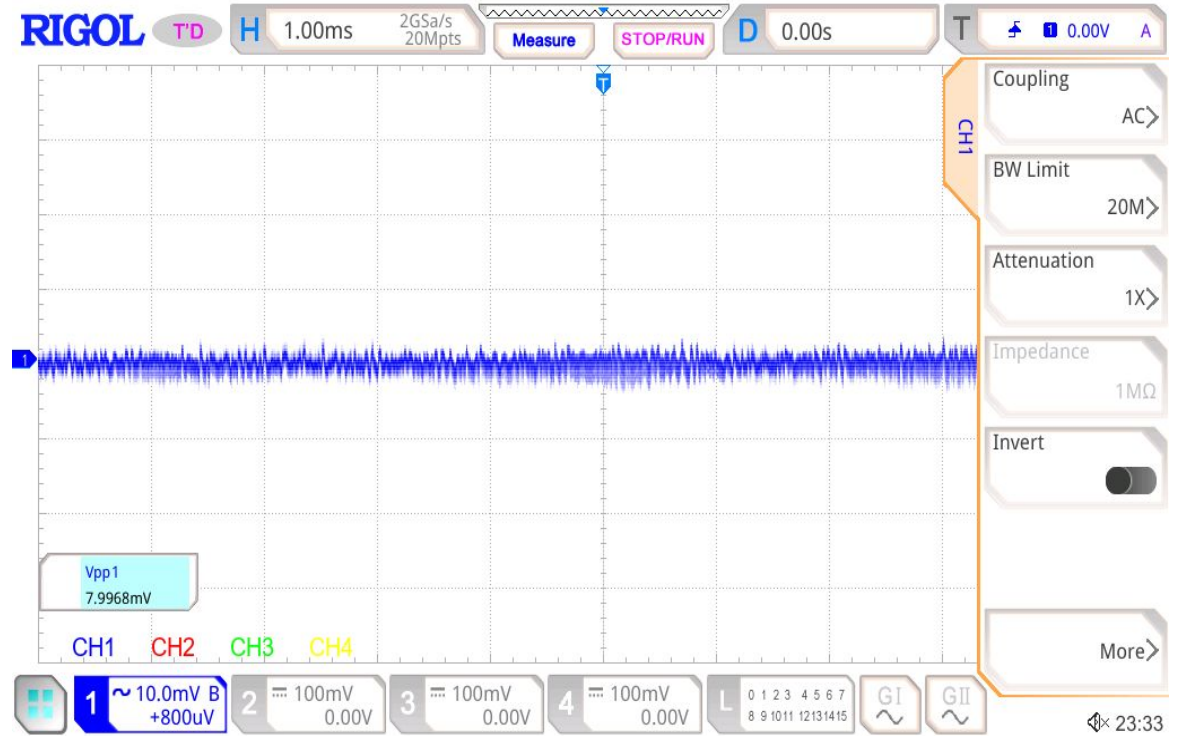

1 A Load
 $V_{PP} = 7.99 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

MGTYAVCC

0.88 V / 6 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744383560056
- $C = 6 \times 47 \mu\text{F}$

Efficiency & Transient

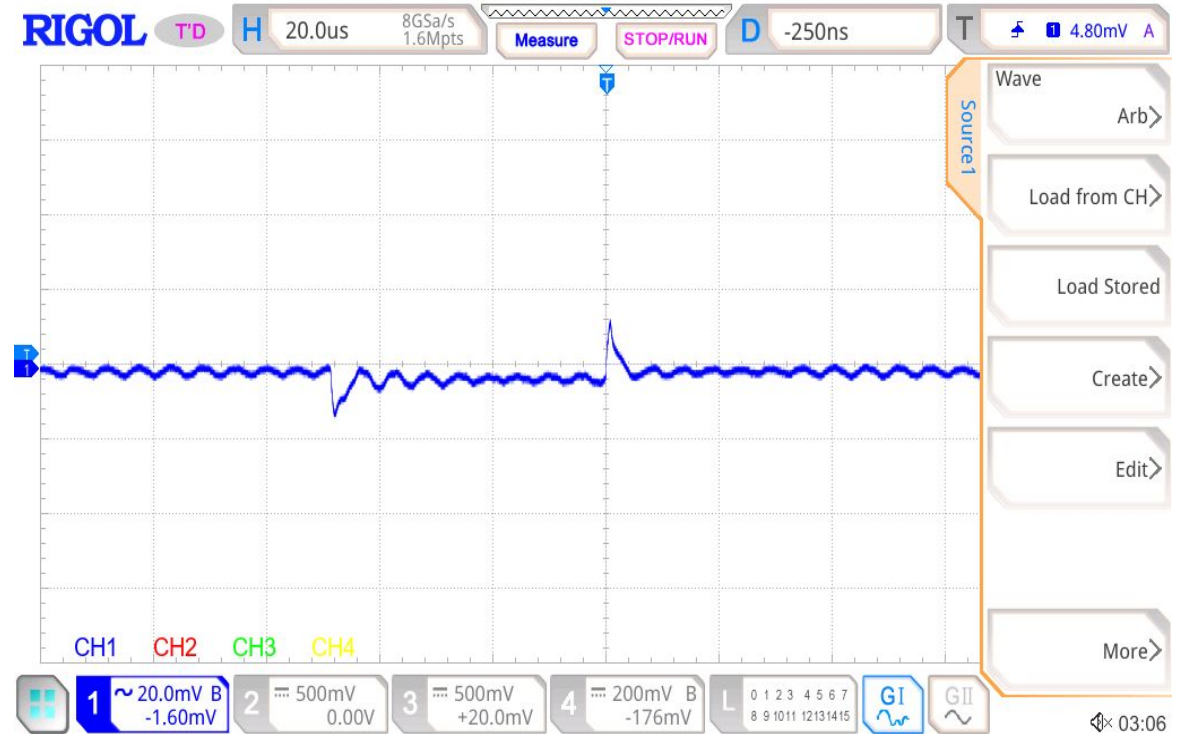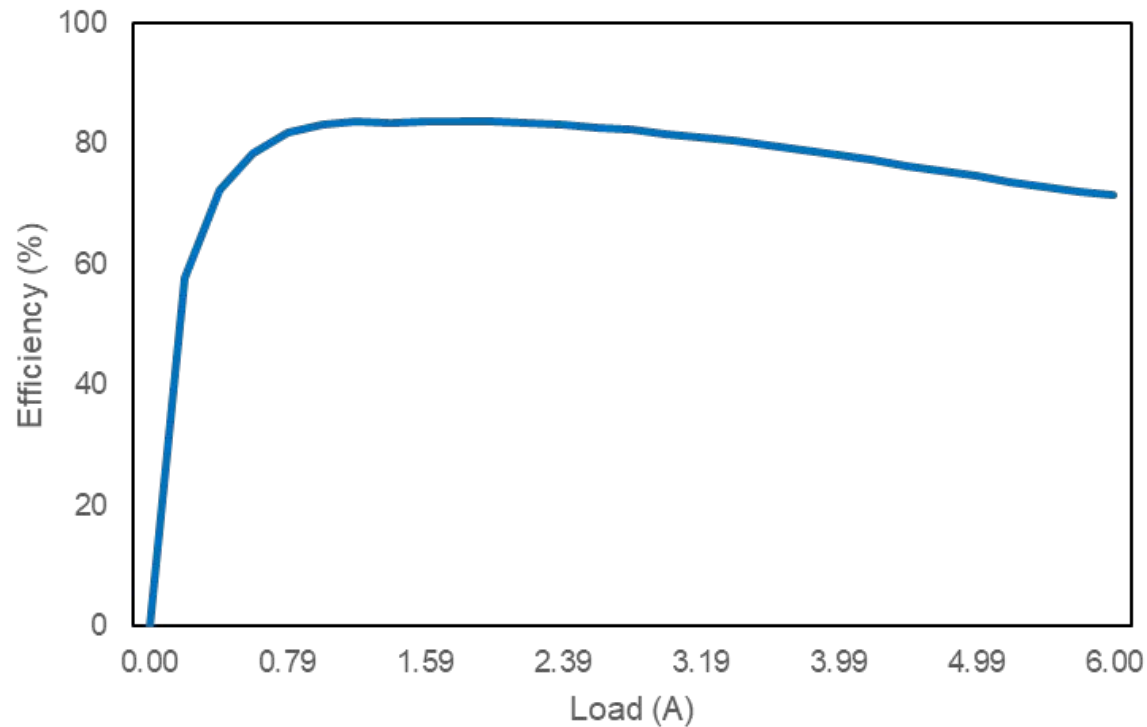


Vout = 0.88V
Transient 4.02 – 6A@10 A/ μ s
 V_{PP} = 24 mV
Fsw = 0.571 MHz
L = 0.56 μ H, C = 6x47 uF

Ripple

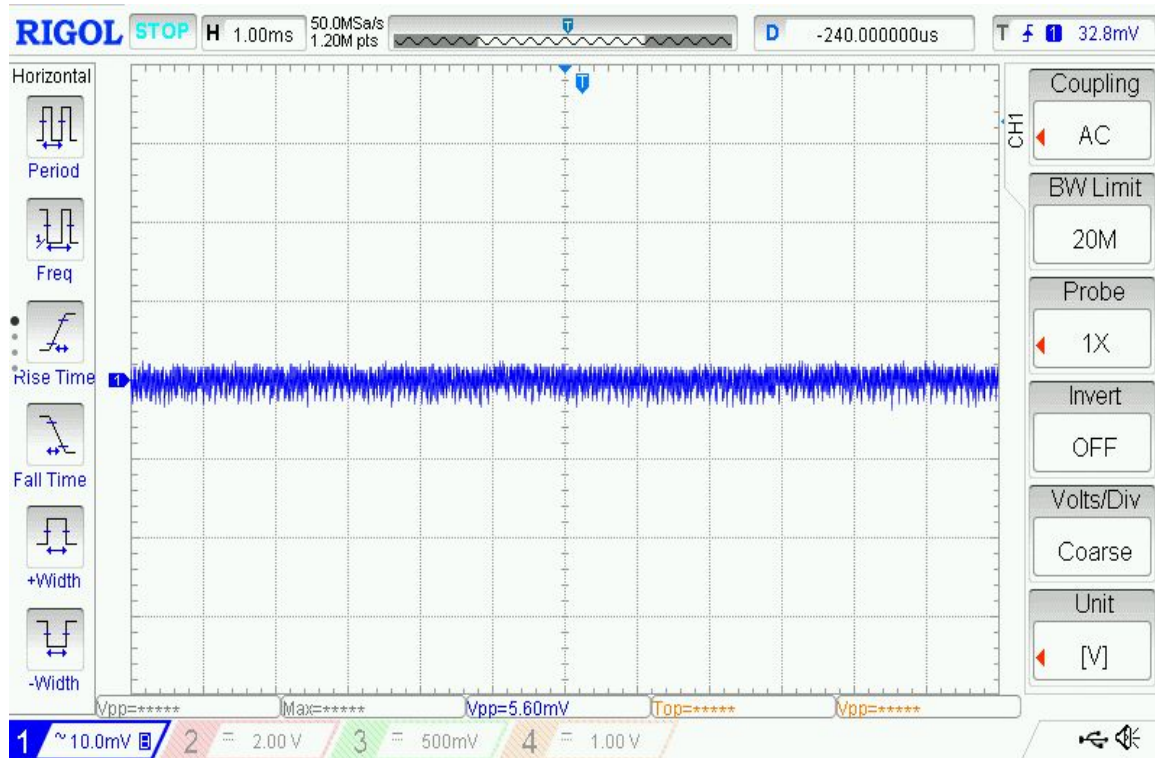

No Load
 $V_{PP} = 5.6 \text{ mV}$

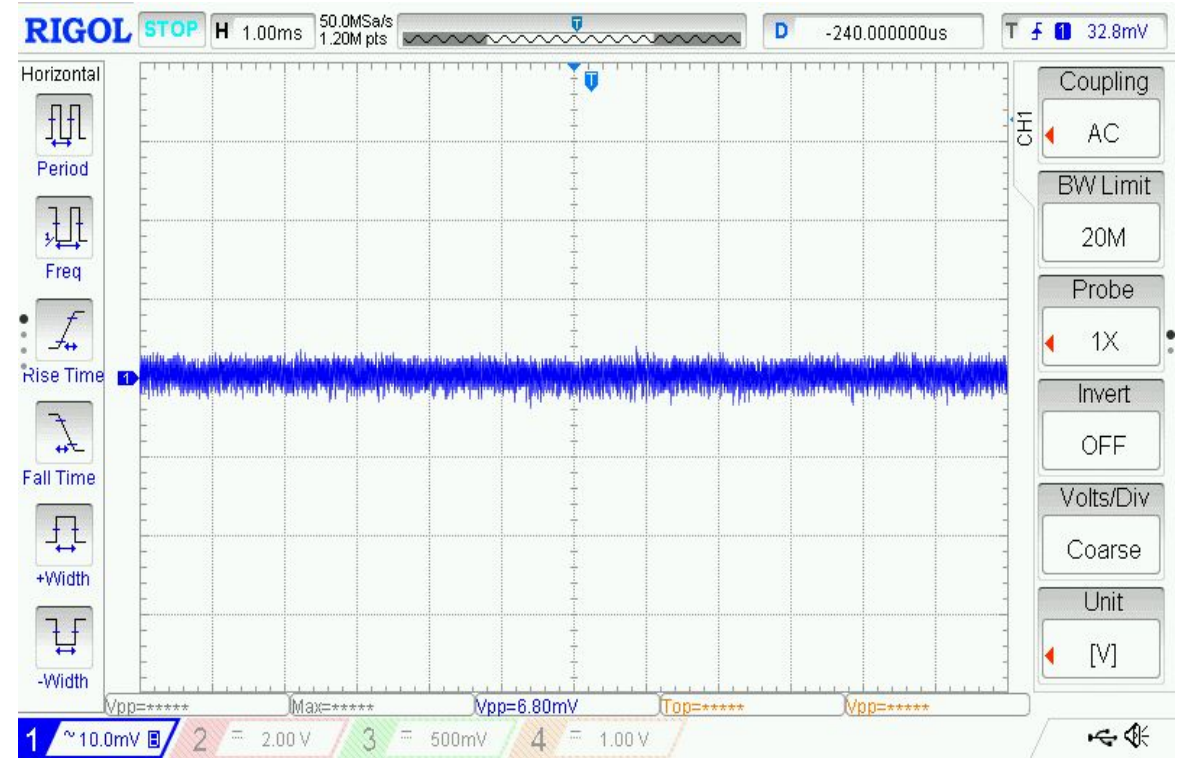

6 A Load
 $V_{PP} = 6.80 \text{ mV}$



$V_{out} = 0.88 \text{ V}$

MGTYAVTT

1.2 V / 10 A


- C220 (High Current Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 0.33 \mu\text{H}$, P/N Wurth 744308033
- $C = 7 \times 47 \mu\text{F}$

Efficiency & Transient

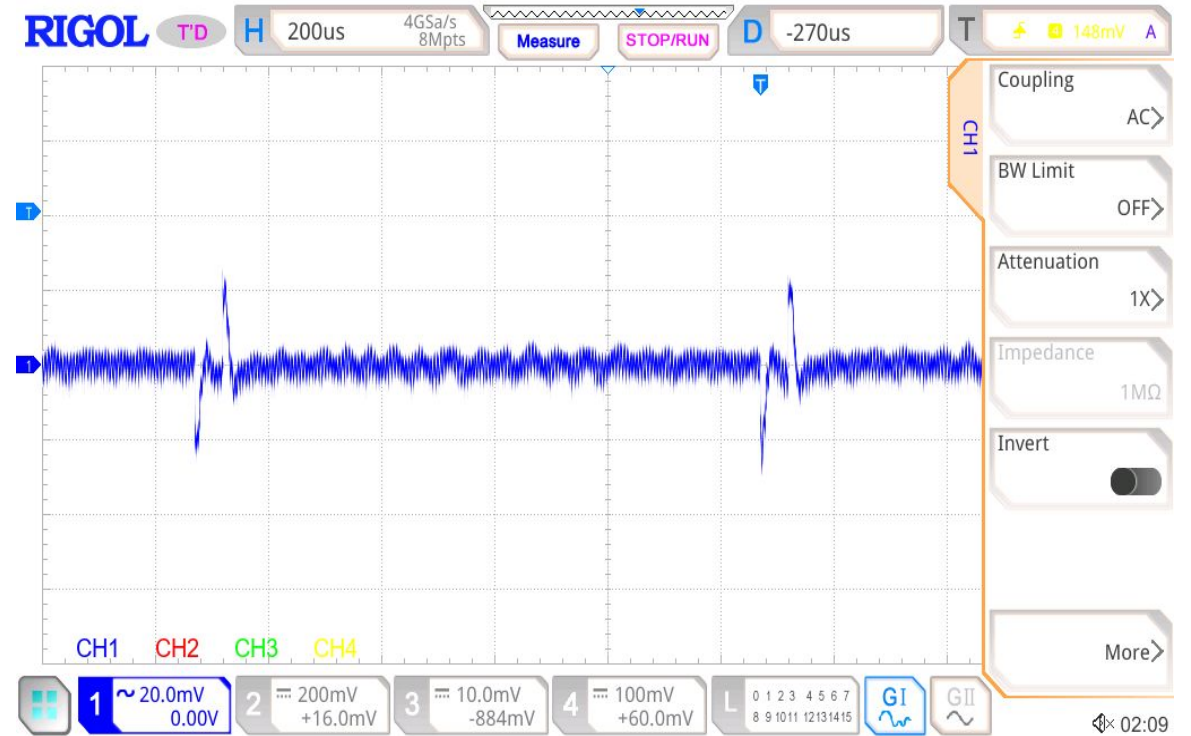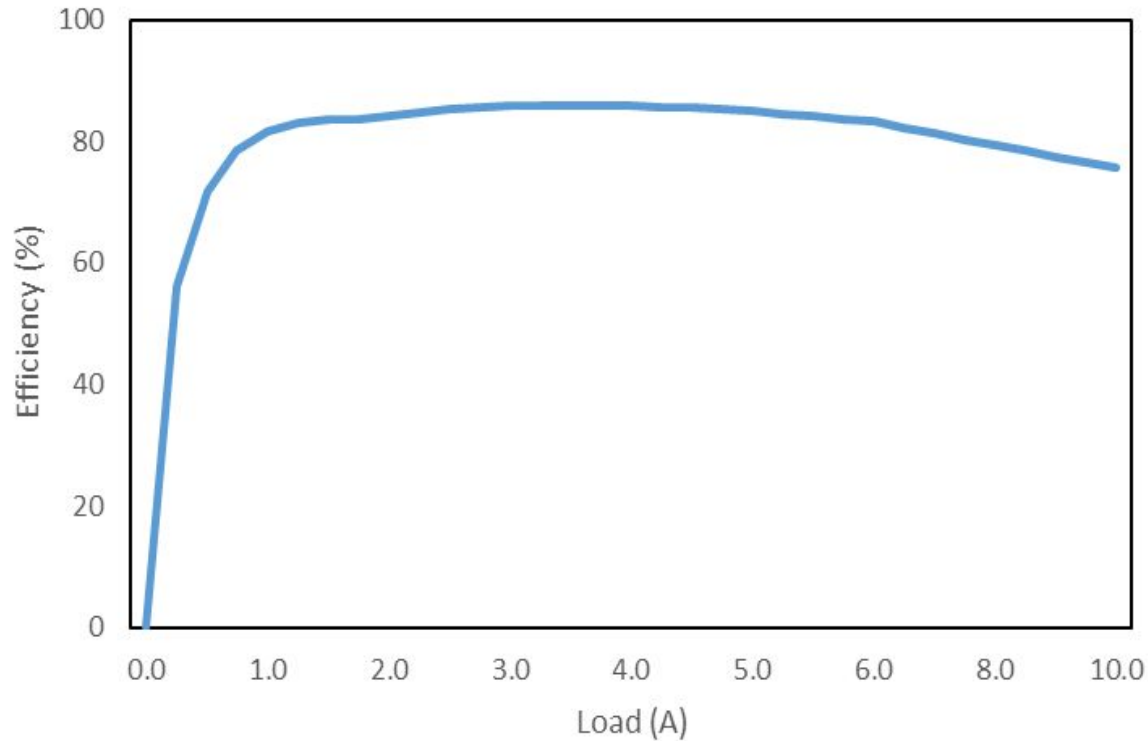


Vout = 1.2V
Transient 6.7 – 10 A@10 A/ μ s
 V_{PP} = 44 mV
Fsw = 0.571 MHz
L = 0.33 μ H, C = 7x47 uF

Ripple

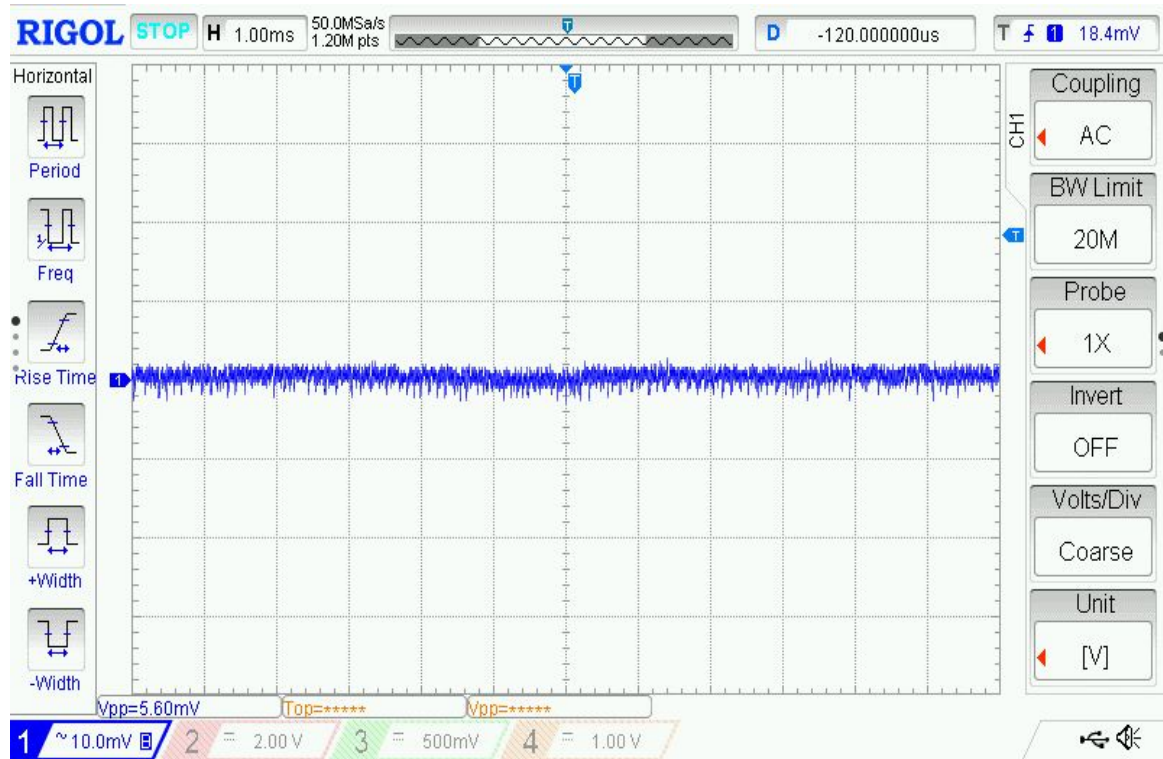


No Load
 $V_{PP} = 5.60 \text{ mV}$

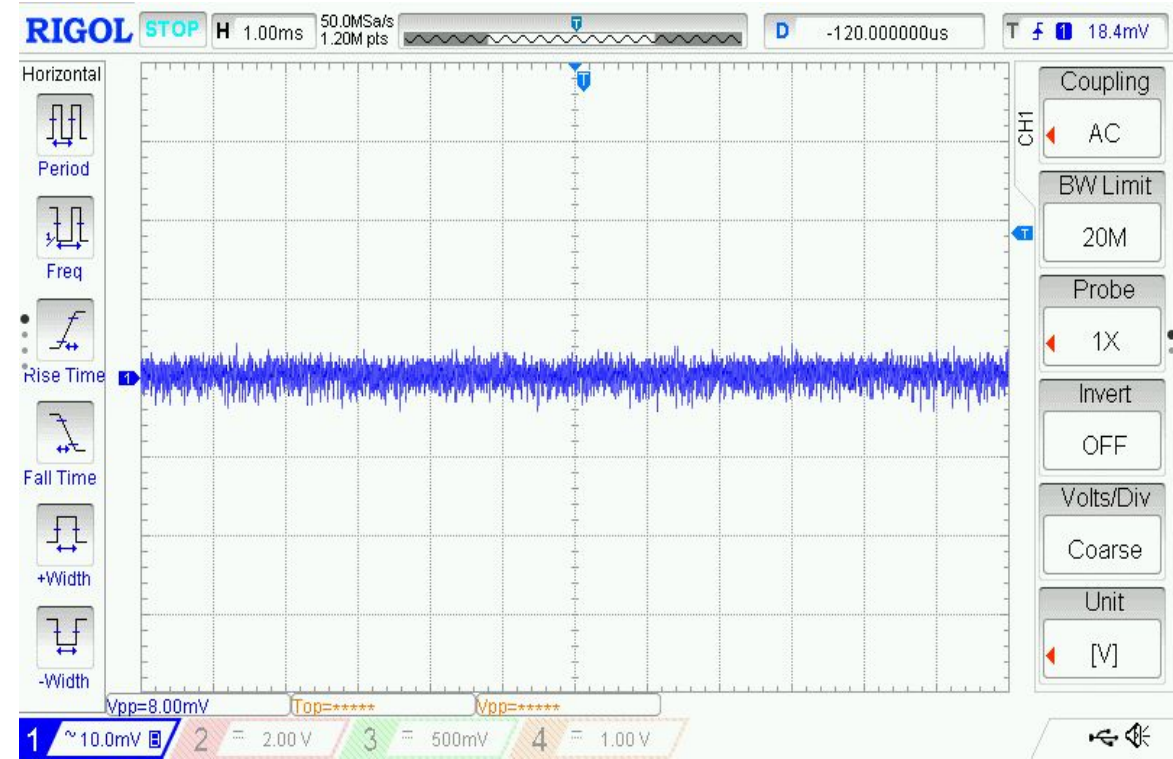

$V_{out} = 1.2 \text{ V}$

10 A Load
 $V_{PP} = 8 \text{ mV}$

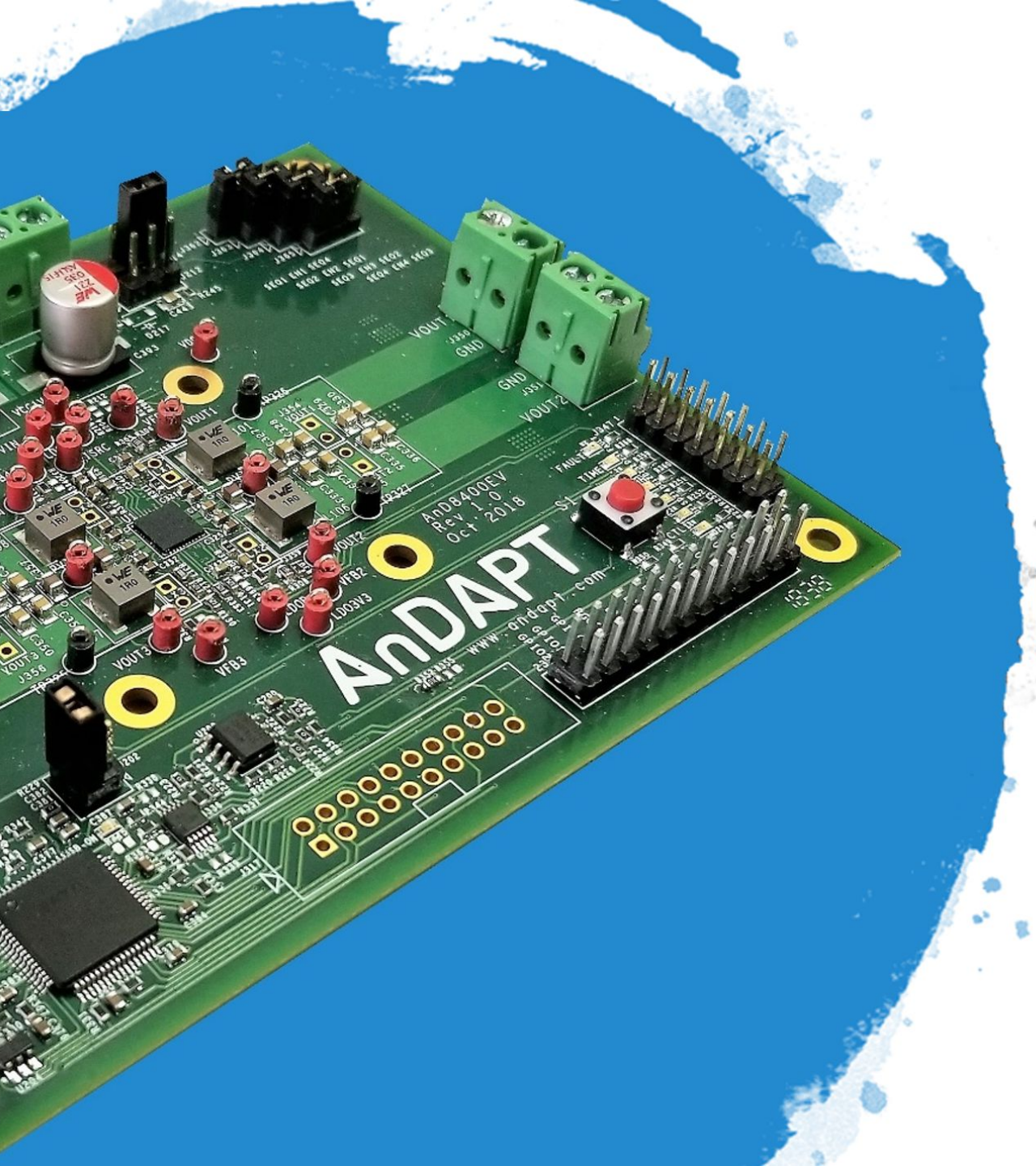

Thank You