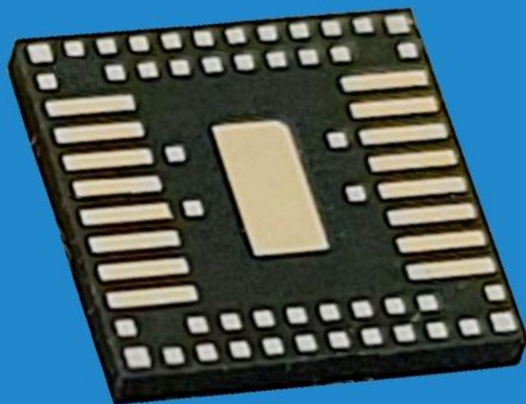




Xilinx Versal Prime (Minimum Rails, Low Voltage) Power Solution

Mapping & Test Data

AnDAPT Marketing Team


AnDAPT

Versal Prime (Minimum Rails, Low Voltage) Power Mapping Highlights

- Power tree mappings completed as per data received from Xilinx Power Management team.
- Both Typical and Upper use-cases are served by the same design.
- Data gathered and bench tested by the applications team at AnDAPT.
 - Data meets or exceeds Xilinx power and timing specifications.
- Total 10 power rails covered by 2x AmP ICs including memory and termination rails.
- Total solution area is 1625.47 mm².
- Presentation contains thermal views of both ICs.

Xilinx Versal Prime Power Tree

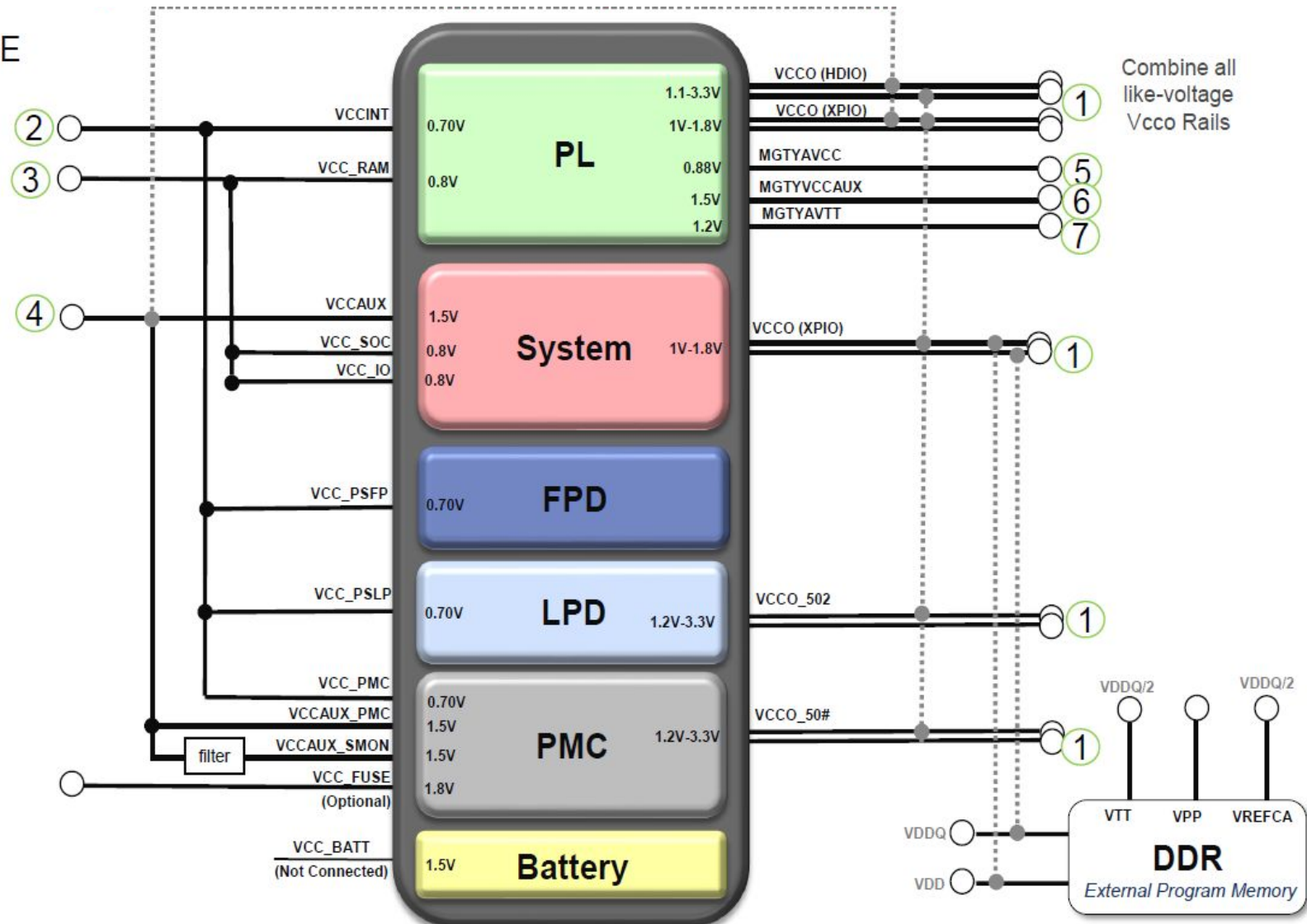Check the latest XPE on Xilinx.com for supported rail groupings and sequences



Versal Prime (Minimum Rails, Low Voltage) Power Rails: Typical and Upper

Sequence	Rail Name	Voltage (V)	Prime	
			Typical (A)	Upper (A)
Rail 1	VCCINT, VCC_PSLP, VCC_PSFP, VCC PMC	0.7V	45.45	54.54
Rail 2	VCC IO, VCCRAM, VCC SOC	0.8V	4.88	5.856
Rail 3	VCCAUX, VCCAUX_SMON, VCCAUX_PMC	1.5V	3.1	3.72
Rail 4	MGTAVCC	.88V	2.47	3.08
Rail 5	MGTAVAUX	1.5V	0.23	0.29
Rail 6	MGTAVTT	1.2V	3.85	4.81
Rail 7	VCCO[0....] (HDIO)	1.1V-3.3V, 1V-1.8V, 1.2V-3.3V	3.39	4.068
Current Total (A)			56.82	68.184

Versal Prime (Minimum Rails, Low Voltage) Power Tree Mapping


#	Rail	Seq	Power Component	Type	Upstream Rail	Vinput (V)	Vout (V)	Iout (A)	AnDAPT PMIC
1	VCCO_XPIO (VCCO_XPIO, VCCO_HDIO)	1	Sync Buck	C200	PVIN	12	1.5	3+3	ARD_X_VRP_IC1
2	VCCO_503 (VCCO_502, VCCO_50X)	1	Load Switch	C200	VCCO_XPIO	12	1.5	3	
3	VCCINT (VCCINT, VCC_PMC, VCC_PSF, VCC_PSLP)	2	Two-Phase DrMOS	C870	PVIN	12	0.7	55	
4	VCC_RAM (VCC_RAM, VCC_SOC, VCC_IO)	3	Sync Buck	C200	PVIN	12	0.8	5.8	
5	VCCAUX (VCCAUX, VCCAUX_PMC, VCCAUX_SMON)	4	Sync Buck	C200	PVIN	12	1.5	3.8 + 0.29	
6	MGTAVCC	5	Sync Buck	C200	PVIN	12	0.88	3.1	ARD_X_VRP_IC2
7	MGTYVCCAUX	6	Load Switch	C750	VCCAUX	1.5	1.5	0.29	
8	MGTAVTT	7	Async Buck	C150	PVIN	12	1.2	4.81	
9	VDDQ	8	Sync Buck	C200	PVIN	12	1.2	3 + 2	
10	VTT	9	VTT Terminator	C210	VDDQ	1.2	0.6	2	

PVIN = 12V


Total estimated solution area = 1625.47 mm²

Versal Prime (Minimum Rails, Low Voltage)


Power Tree Mapping

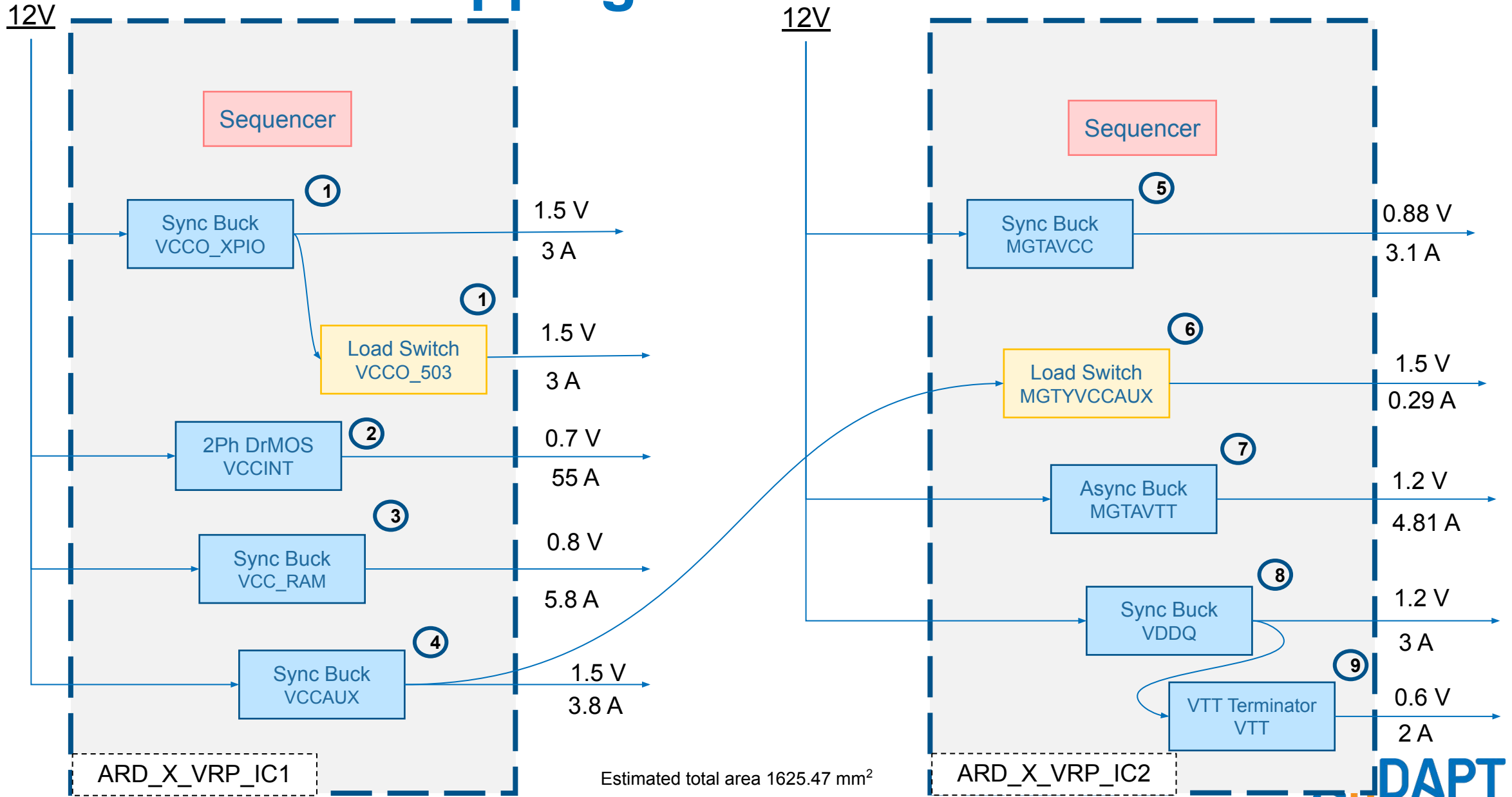

Mapping (WebAmP View) Design –IC1

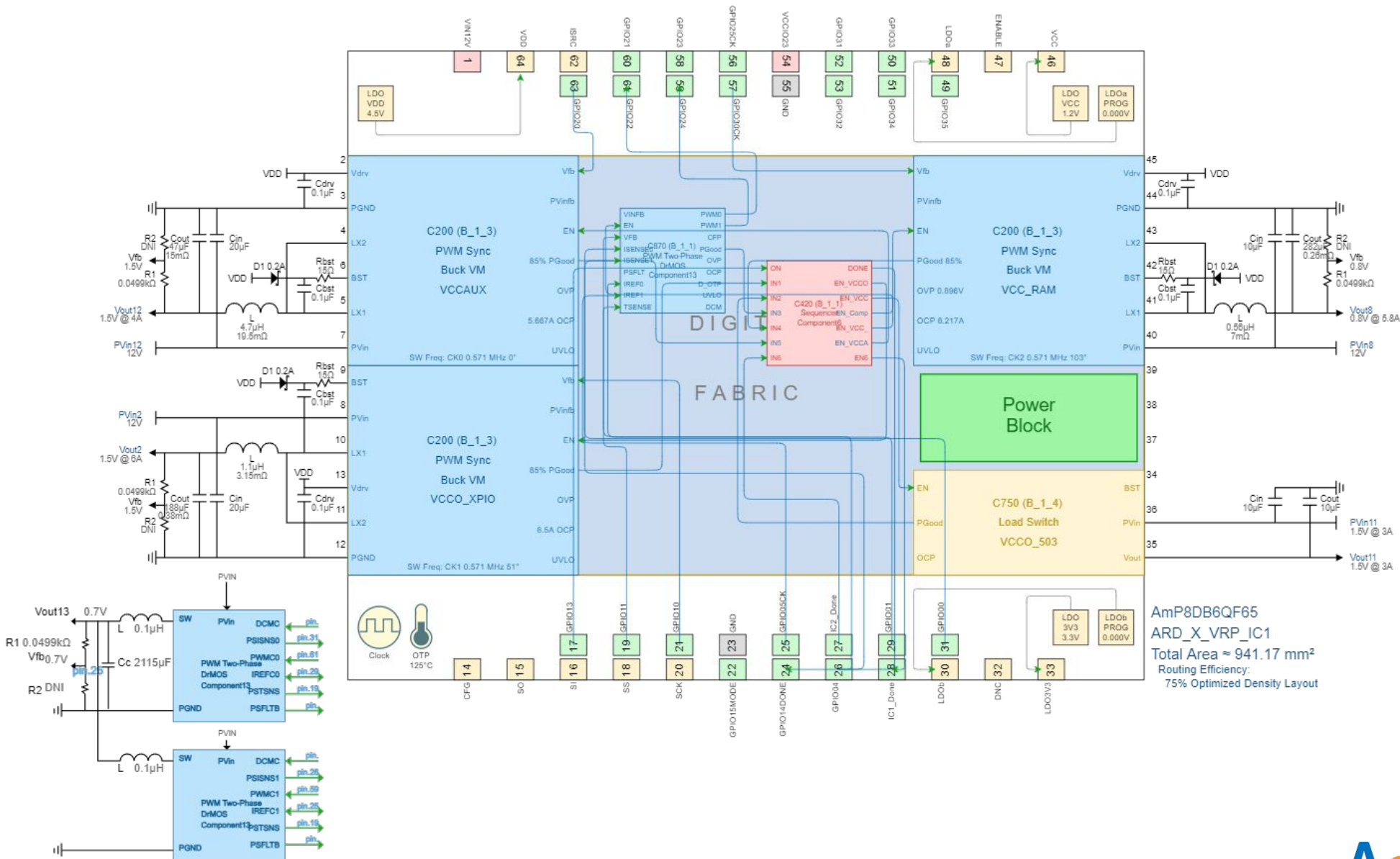


Mapping (Thermal View) –IC1

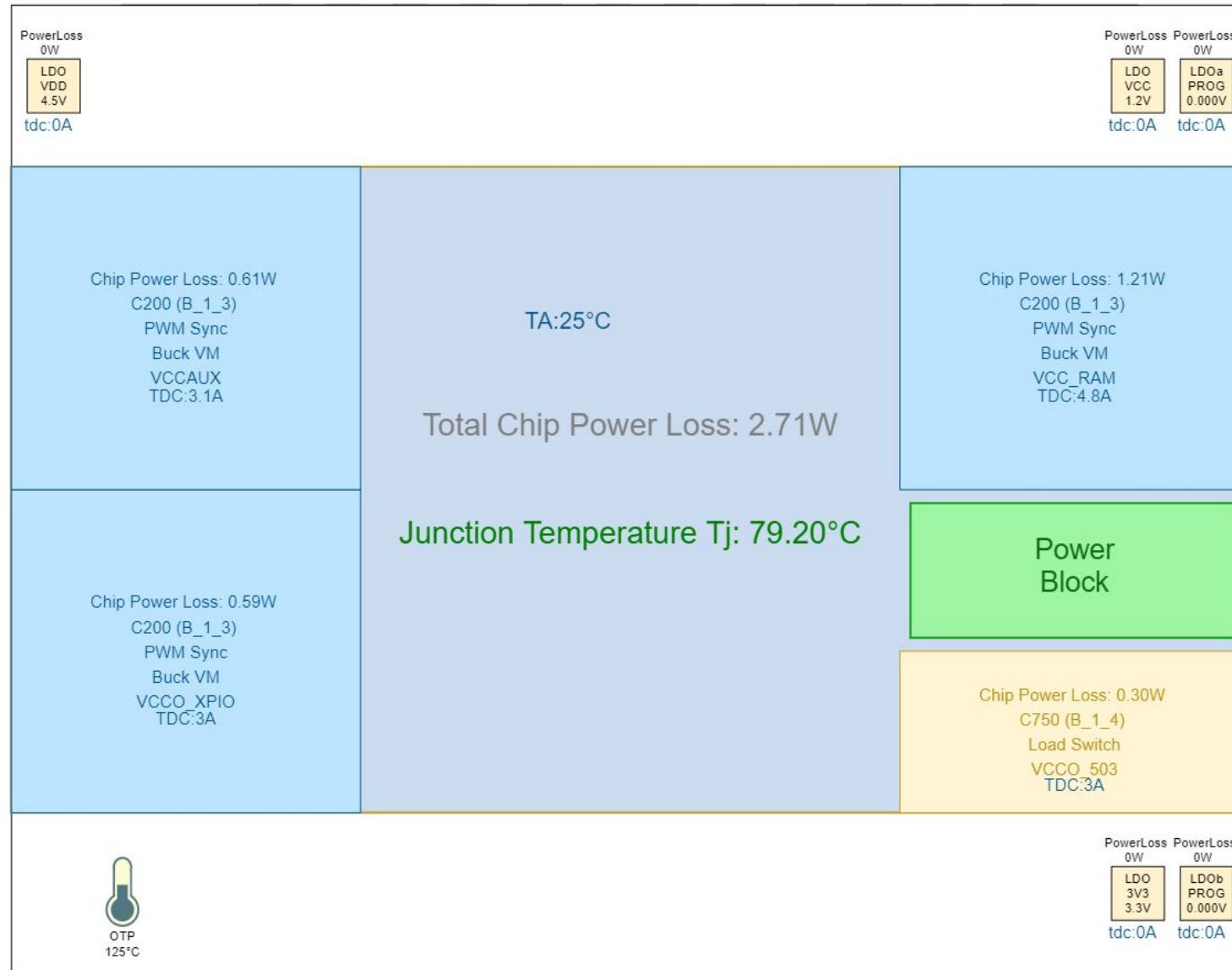


AmP8DB6QF65
ARD_X_VRP_IC1
Total Area ≈ 941.17 mm²
Routing Efficiency:
75% Optimized Density Layout


Mapping (WebAmP View) Design –IC2

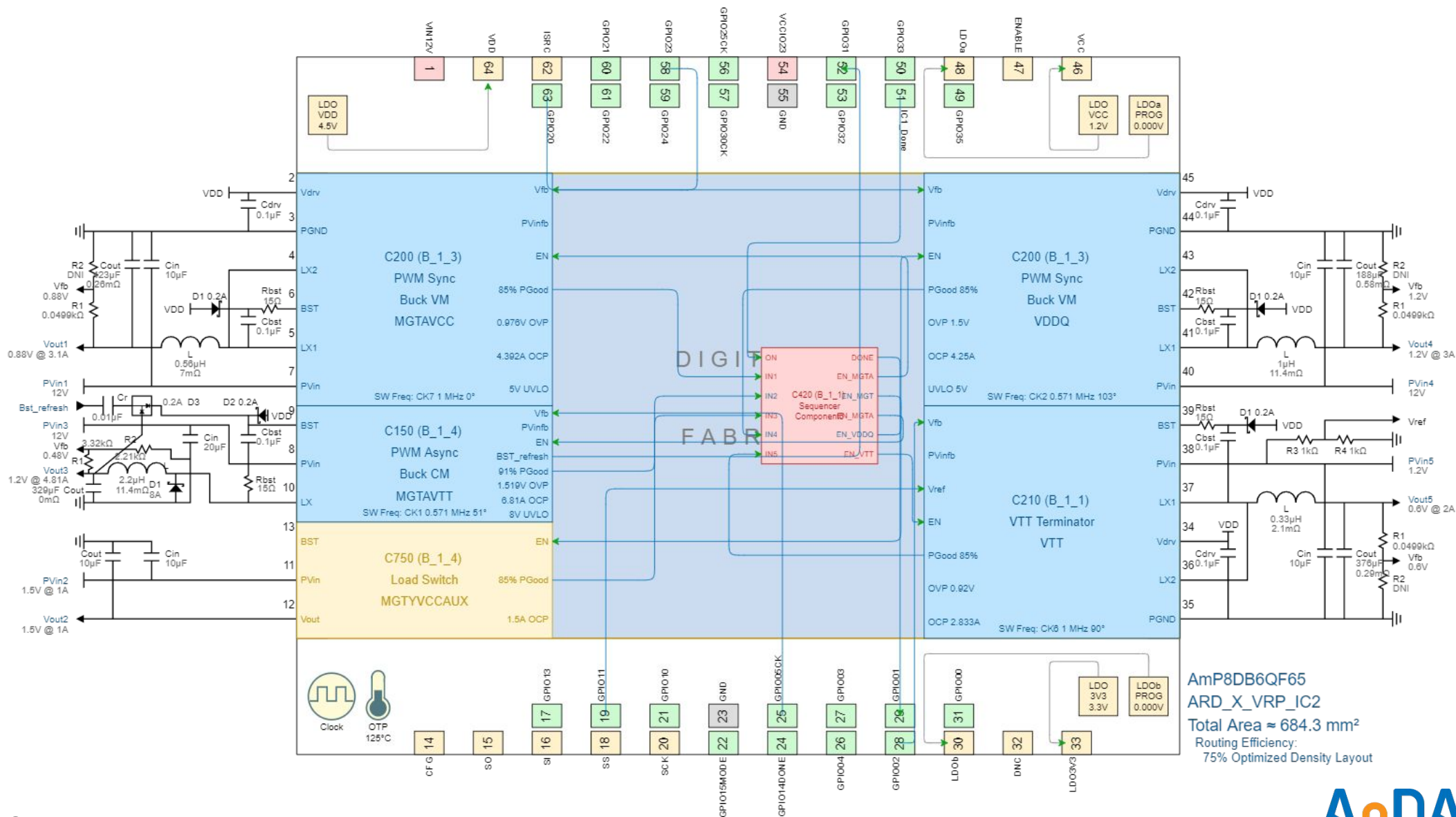

Mapping (Thermal View) –IC2

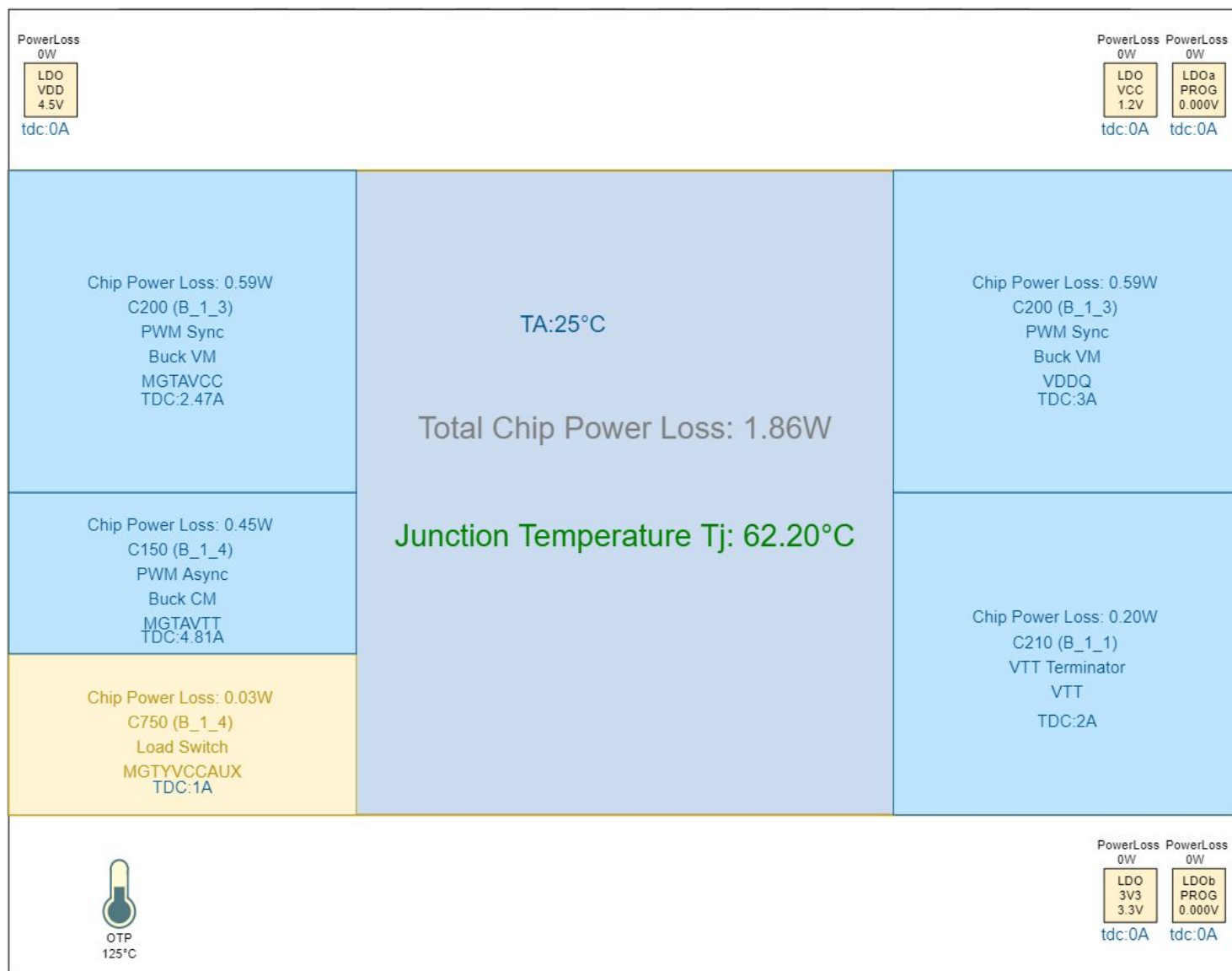

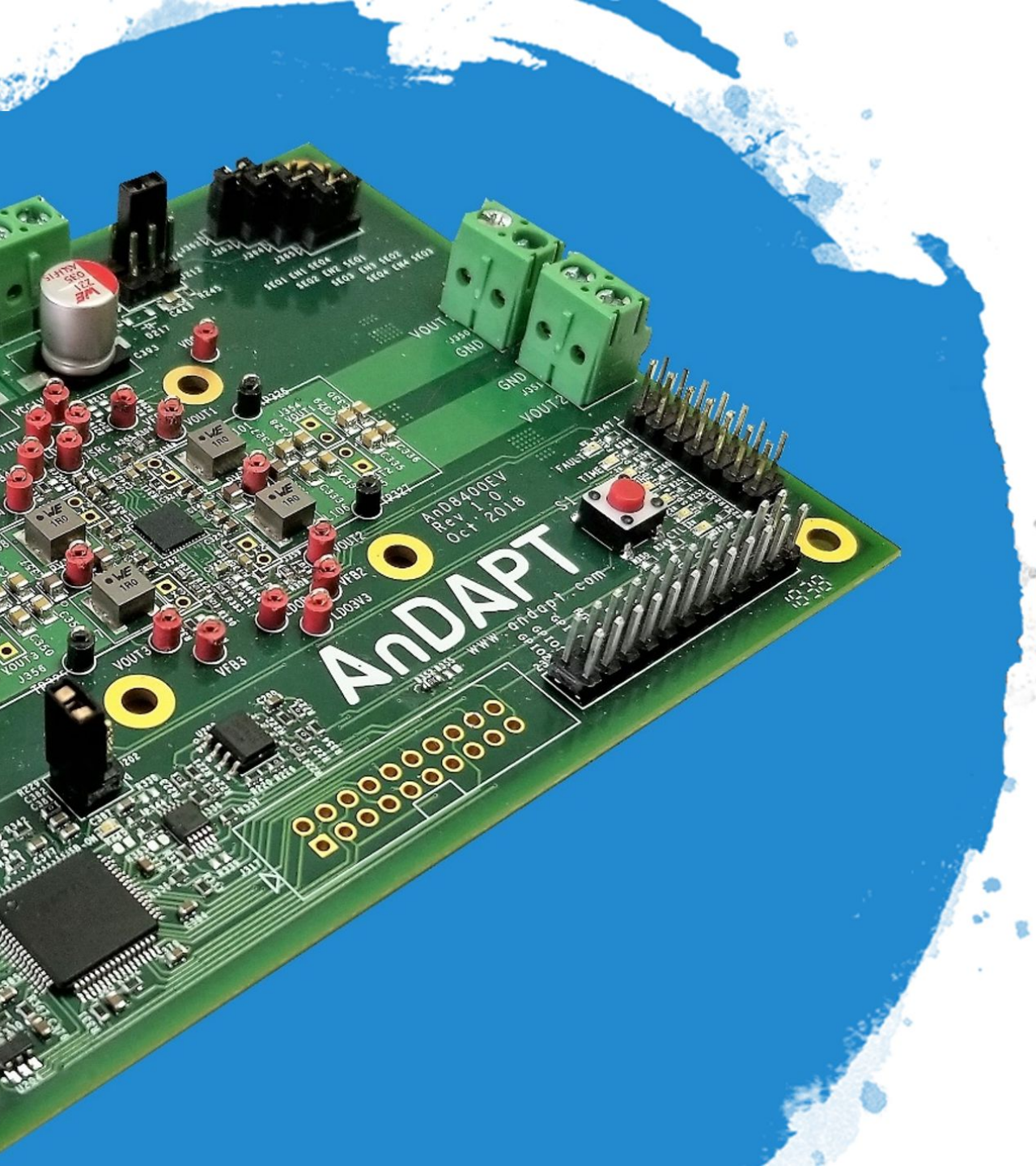AmP8DB6QF65
ARD_X_VRP_IC2
Total Area $\approx 684.3 \text{ mm}^2$
Routing Efficiency:
75% Optimized Density Layout



Test Data



**Versal Prime (Minimum
Rails, Low Voltage)**

VCCO_XPIO

1.5 V / 6 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1.1 \text{ } \mu\text{H}$, P/N Wurth 744314110
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

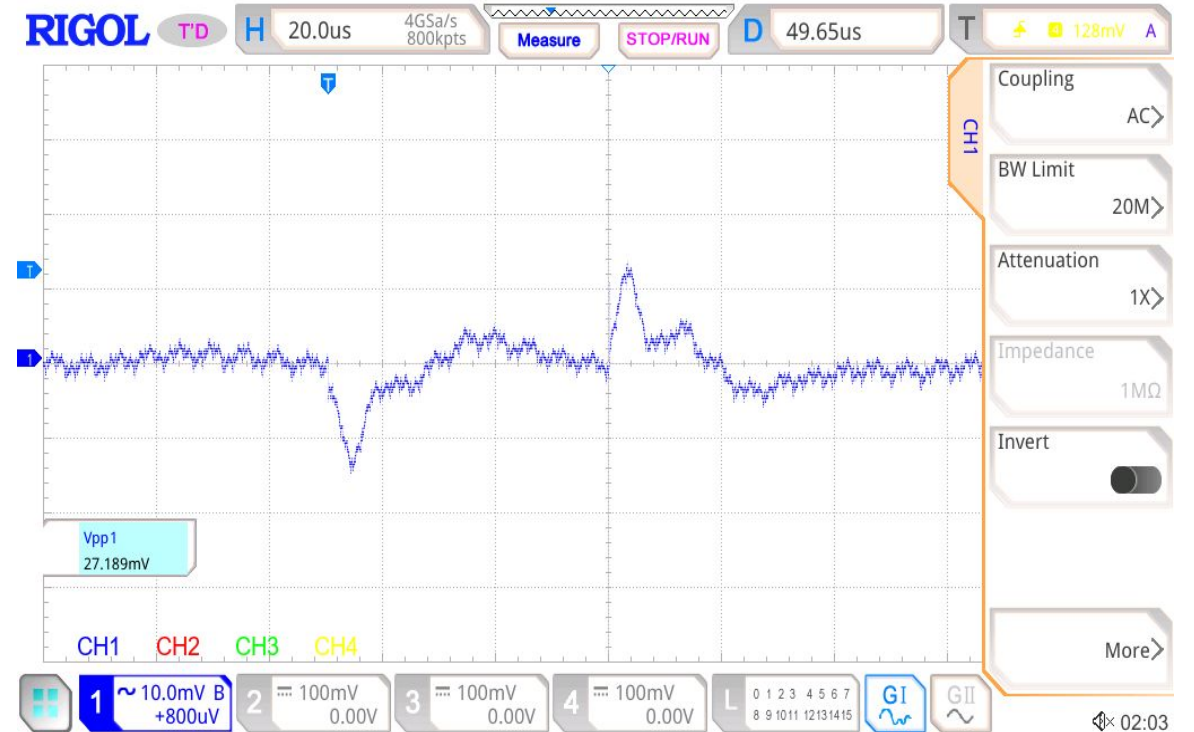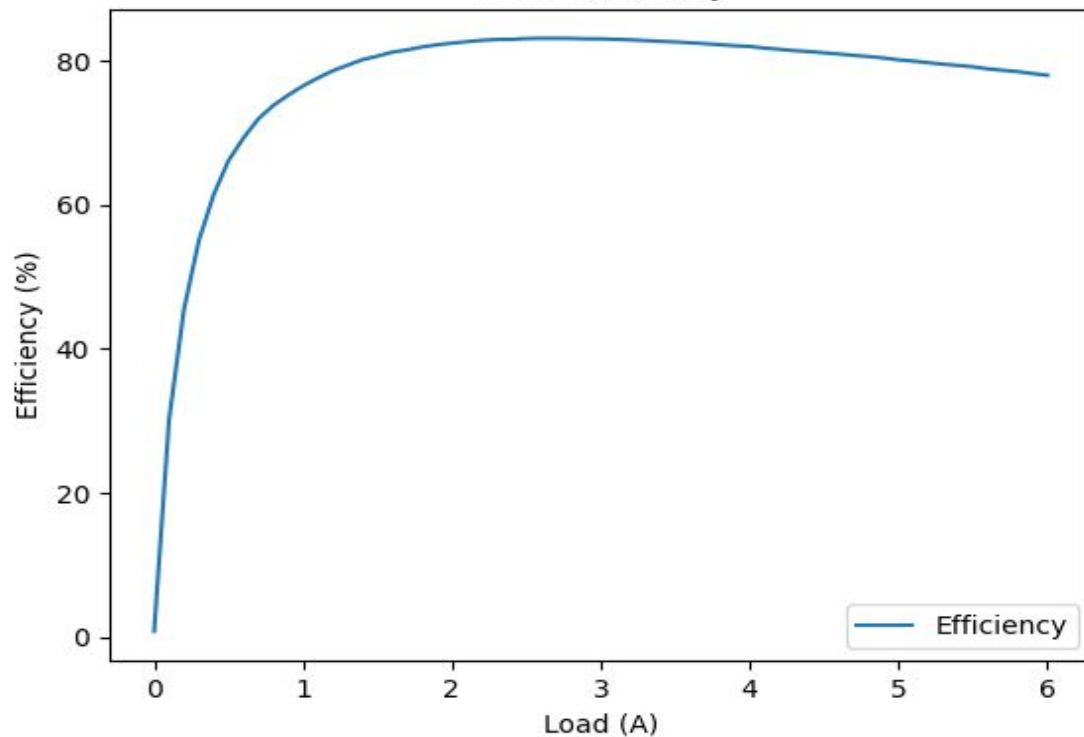


Vout = 1.5V
Transient 4.5 – 6 A@10 A/μs
 $V_{PP} = 27.18 \text{ mV}$
Fsw = 0.571 MHz
L = 1.1 μH, C = 4x47 uF

Ripple

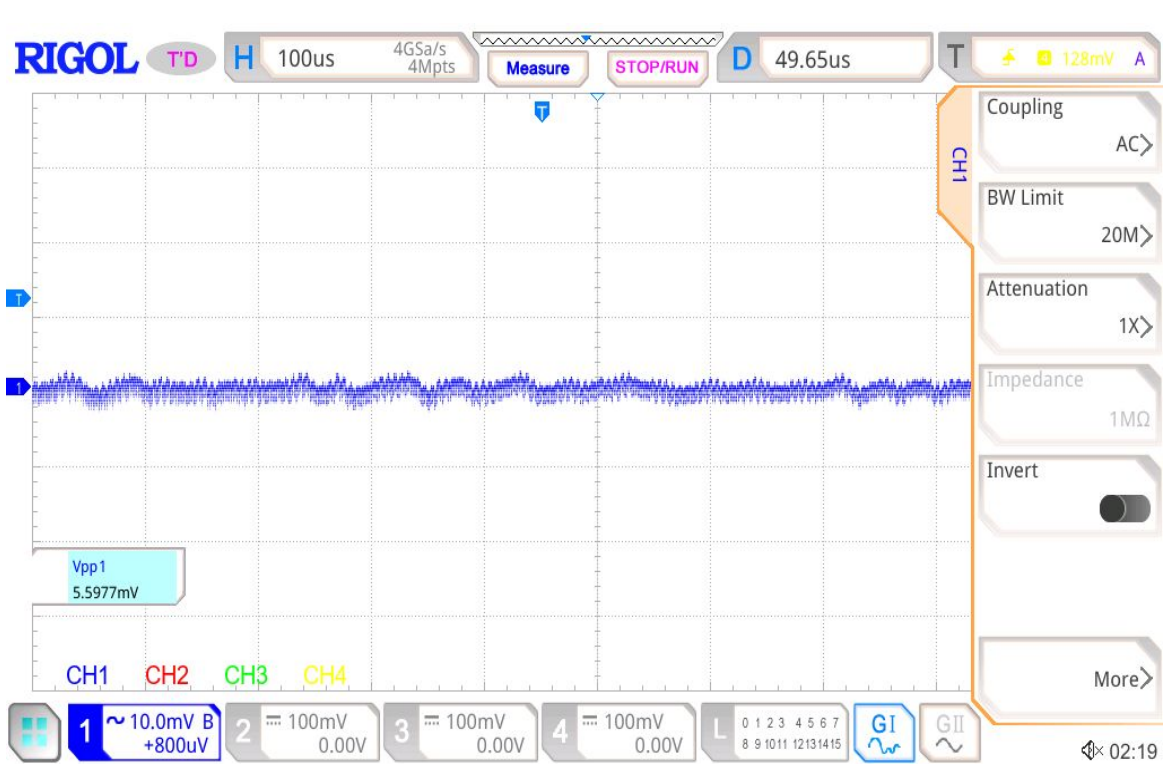

No Load
 $V_{PP} = 5.59 \text{ mV}$

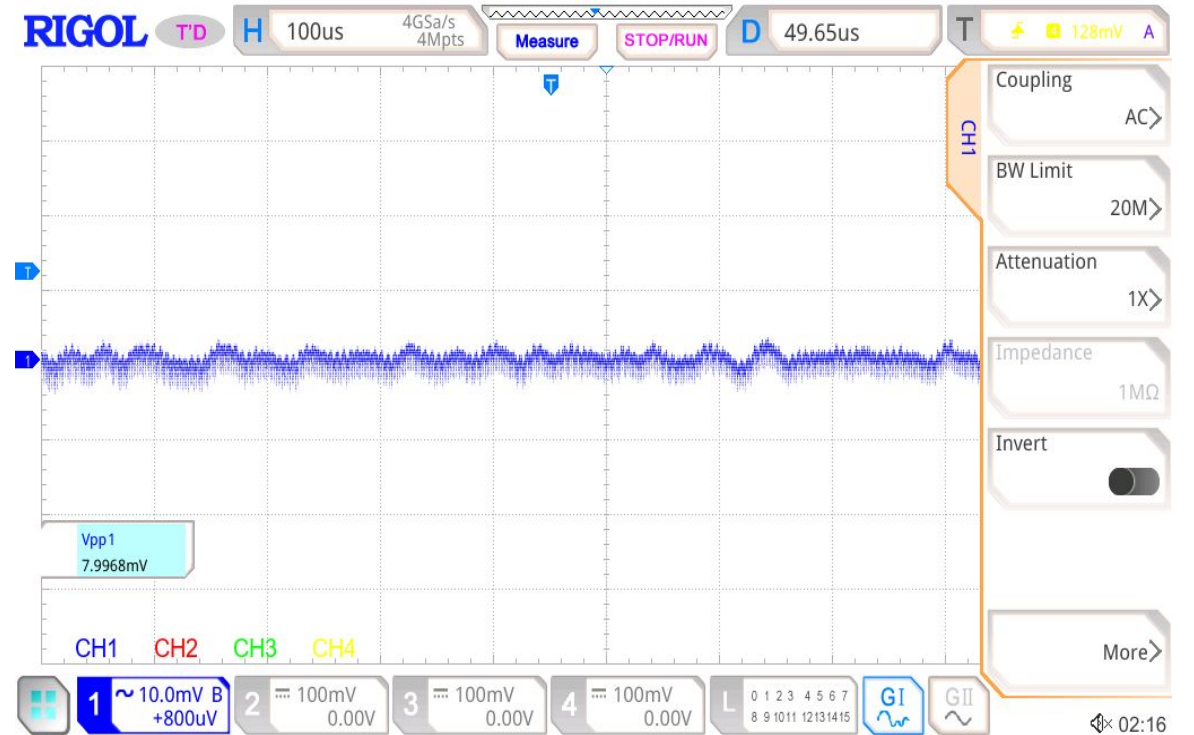

6 A Load
 $V_{PP} = 7.99 \text{ mV}$

$V_{out} = 1.5 \text{ V}$

VCCO_503

1.5 V / 3 A



- C750 (Load switch)

VCCINT

0.7 V / 55 A


- C870 (Two Phase DrMOS)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.1 \text{ } \mu\text{H}$, P/N Wurth 7443081010
- $C = 45 \times 47 \text{ } \mu\text{F} + 4 \times 470 \text{ } \mu\text{F}$

Efficiency & Transient

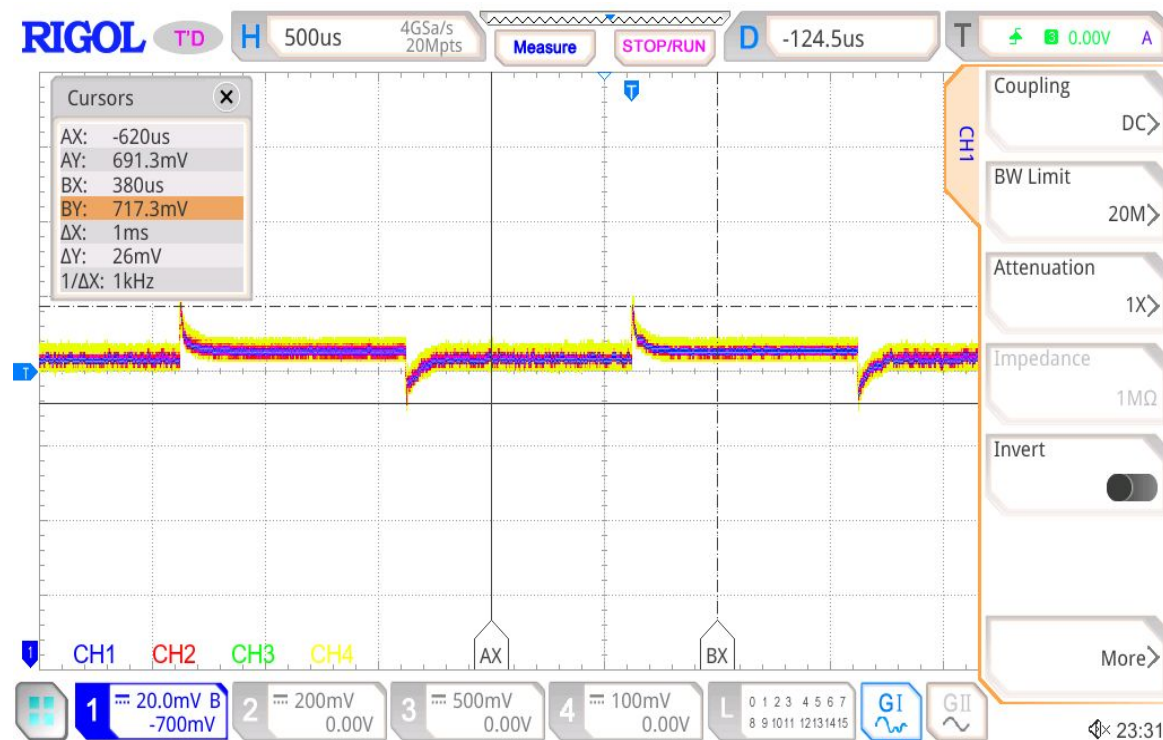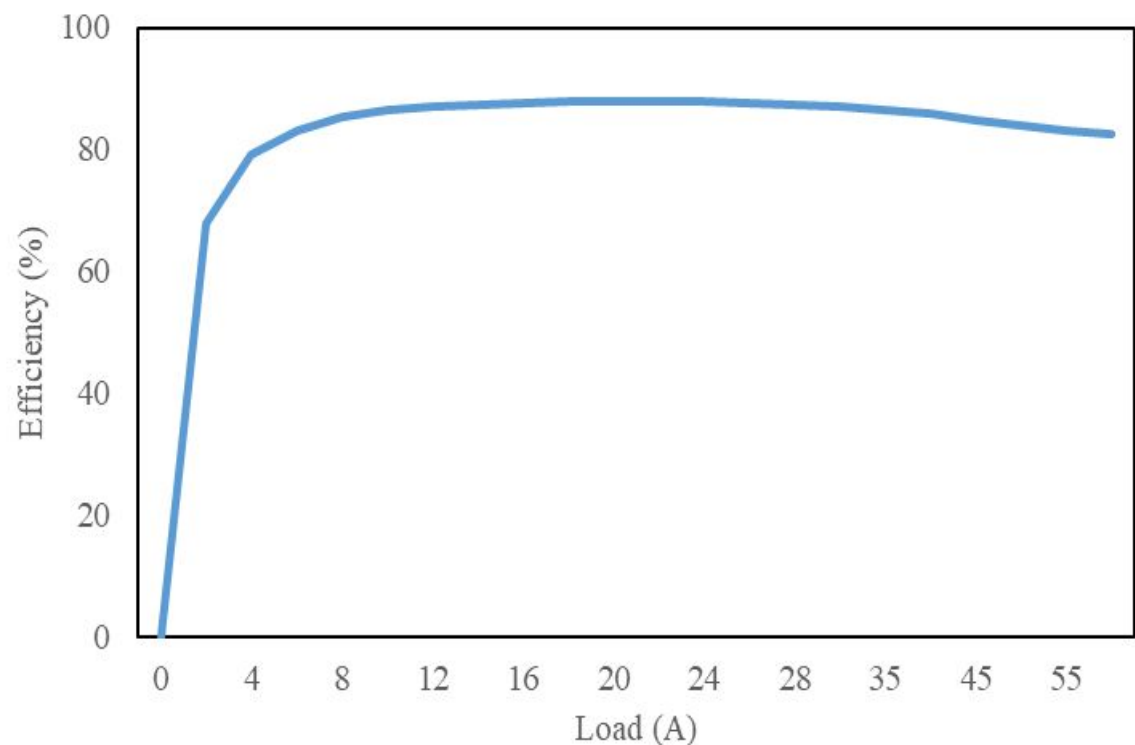


Vout = 0.7V
Transient 22A – 55A @ 100 A/μs
 $V_{PP} = 26 \text{ mV}$
Fsw = 1 MHz
L = 0.1 μH, C = 45x47 μF + 4x470 μF

Ripple

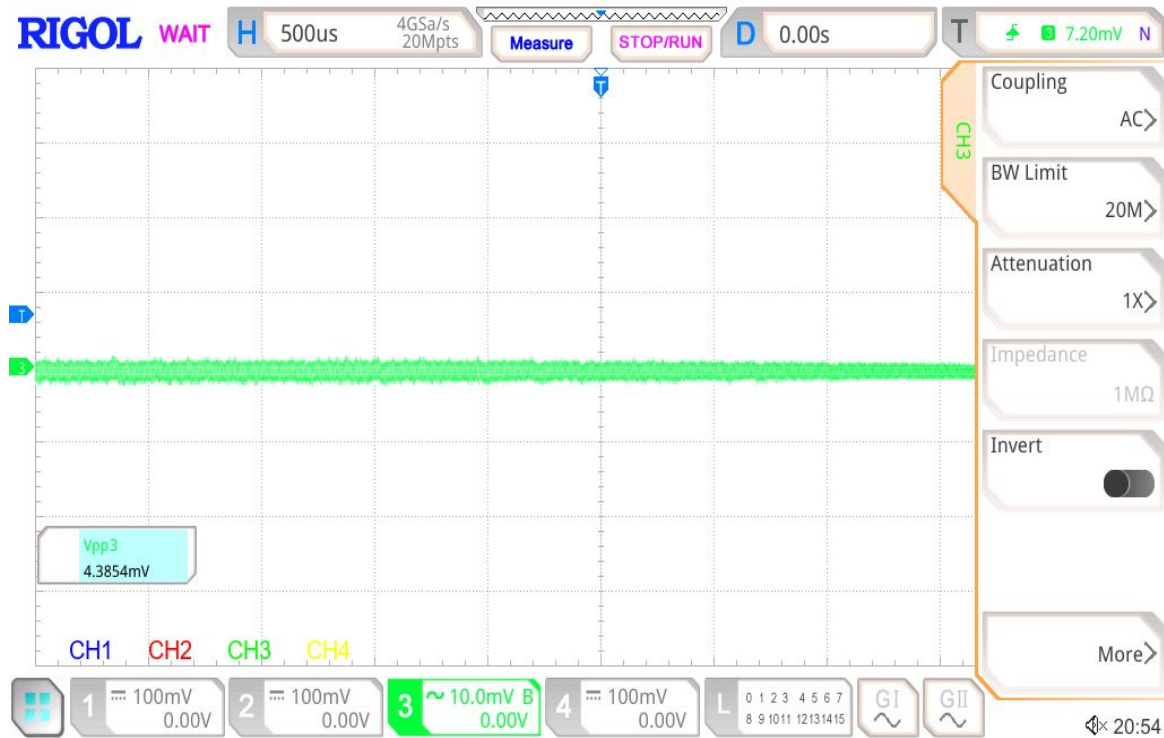

No Load
 $V_{PP} = 4.38 \text{ mV}$

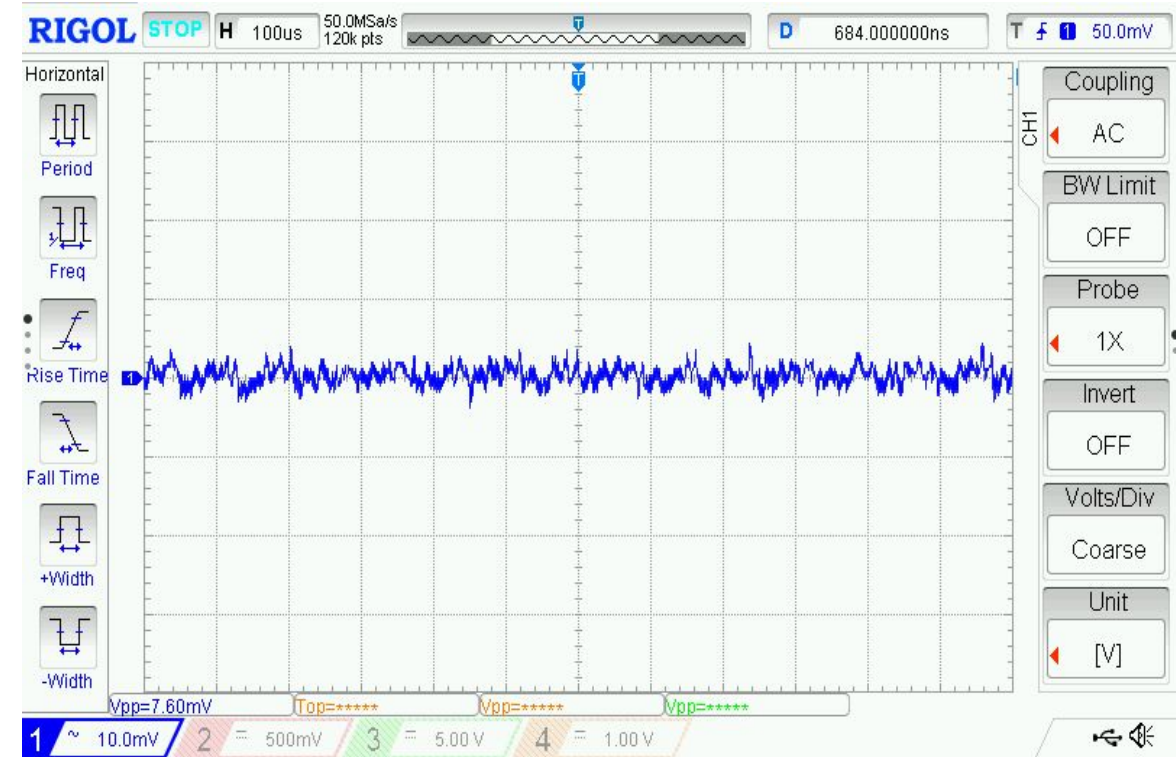

$V_{out} = 0.7 \text{ V}$



55 A Load
 $V_{PP} = 7.60 \text{ mV}$

VCC_RAM

0.8 V / 5.8 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744383560056
- $C = 6 \times 47 \mu\text{F}$

Efficiency & Transient

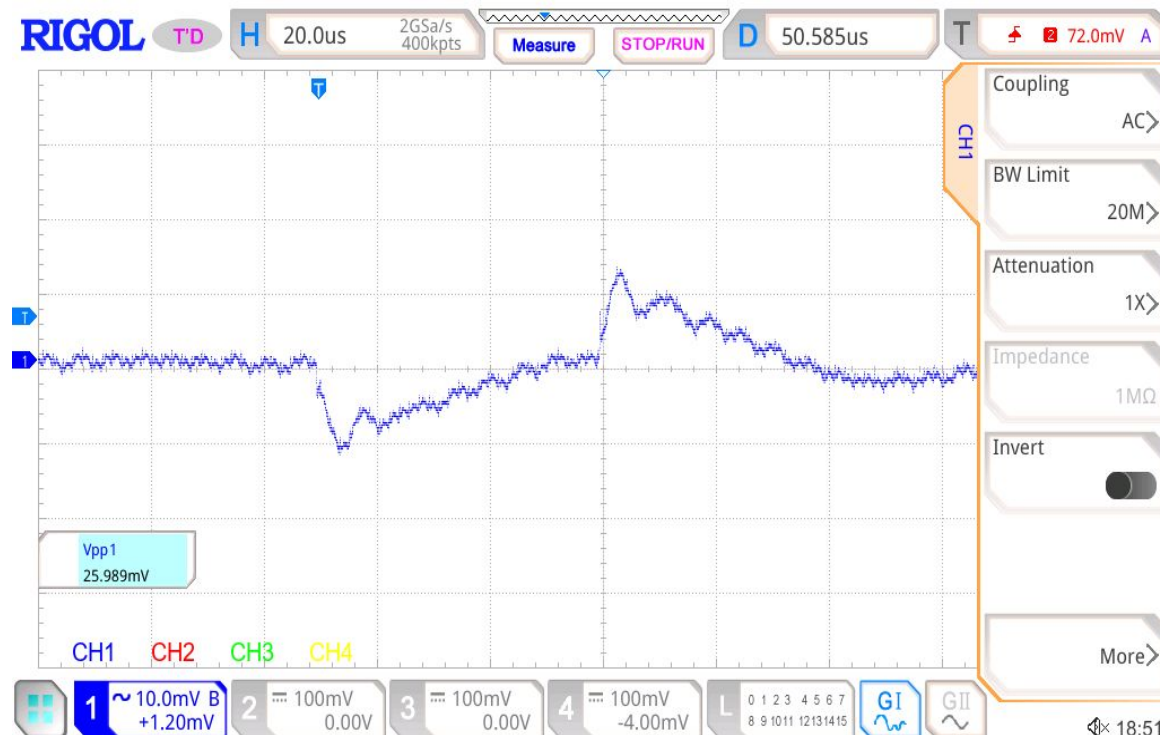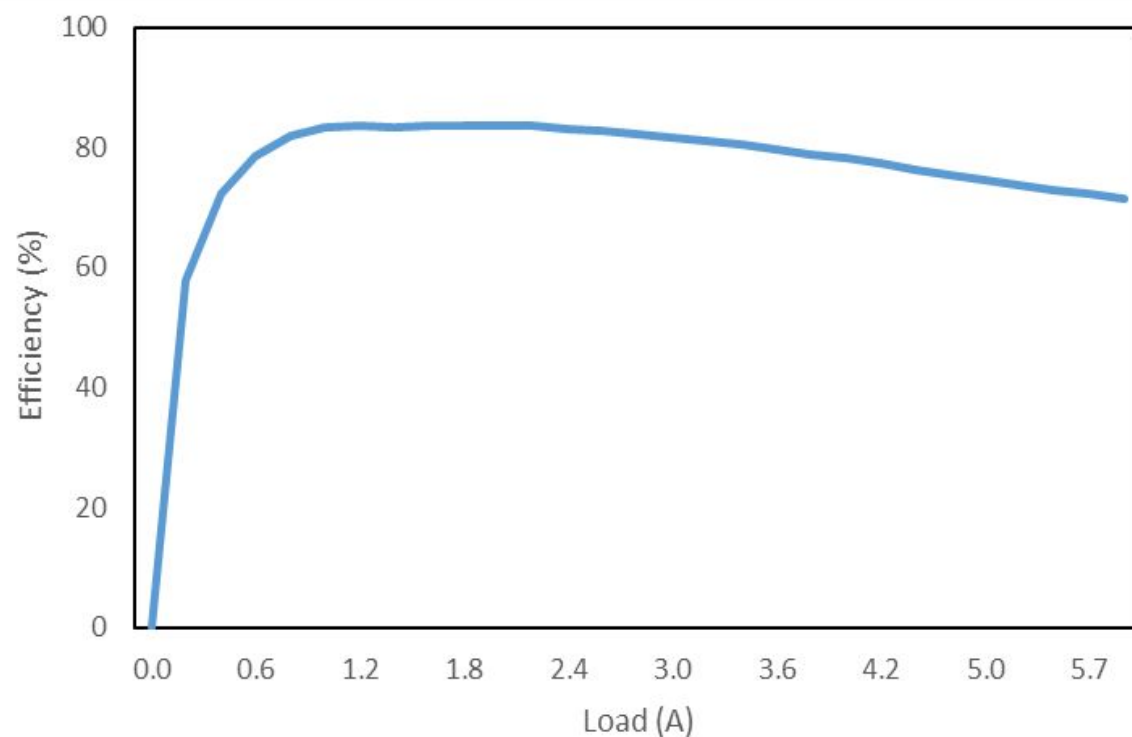


Vout = 0.8V
Transient 3.48A – 5.8A @ 10 A/μs
 $V_{PP} = 25.98 \text{ mV}$
Fsw = 0.571 MHz
L = 0.56 μH, C = 6x47 uF

Ripple

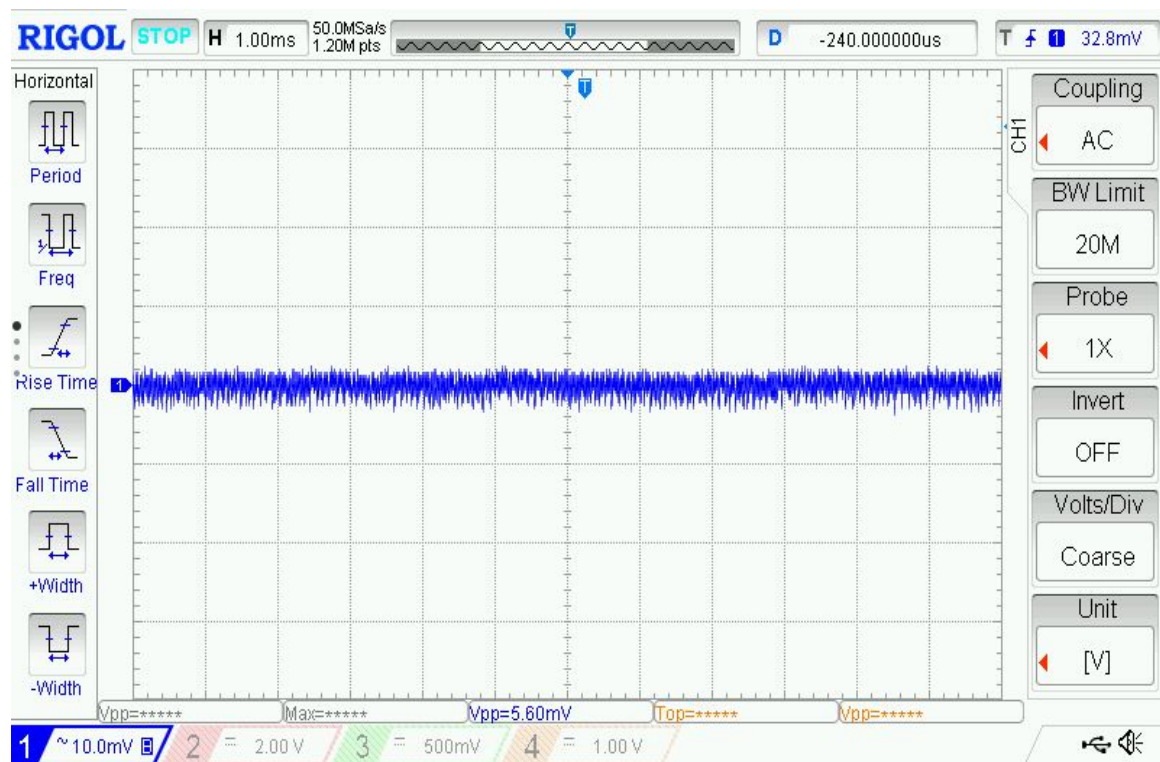

No Load
 $V_{PP} = 5.60 \text{ mV}$

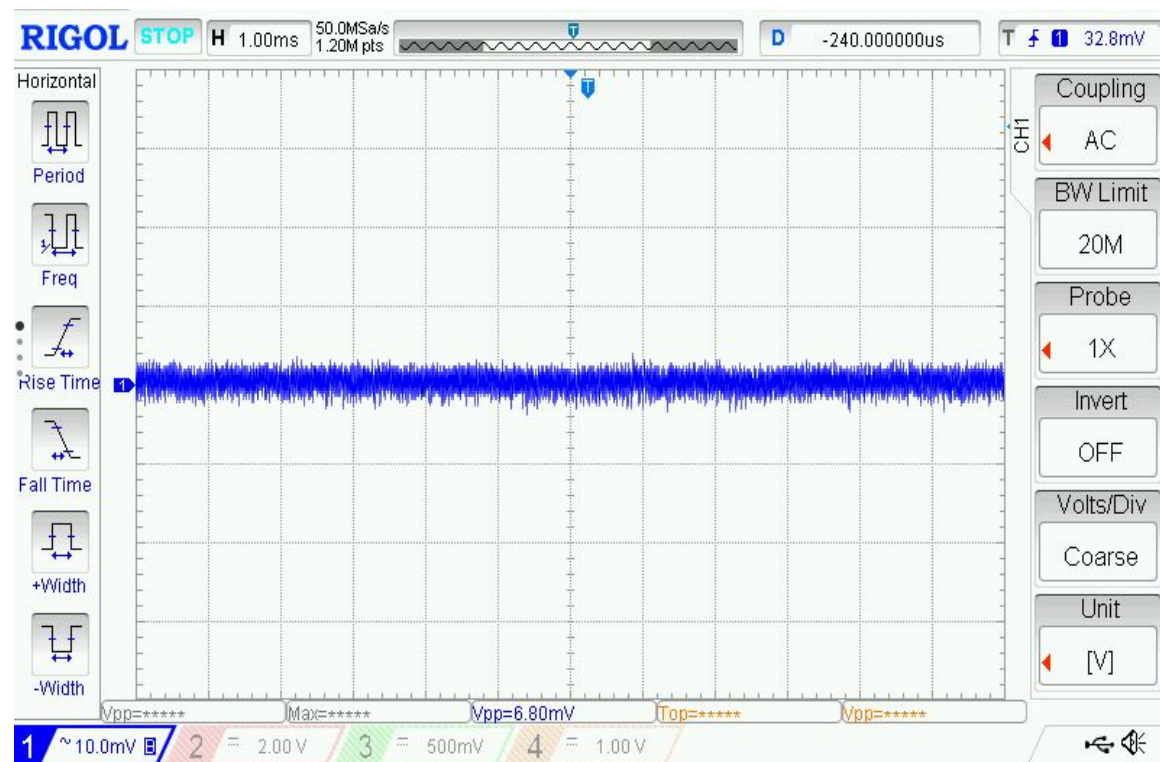

5.8 A Load
 $V_{PP} = 6.80 \text{ mV}$



$V_{out} = 0.8 \text{ V}$

VCCAUX

1.5 V / 4 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 4.7 \text{ } \mu\text{H}$, P/N Wurth 744311470
- $C = 1 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

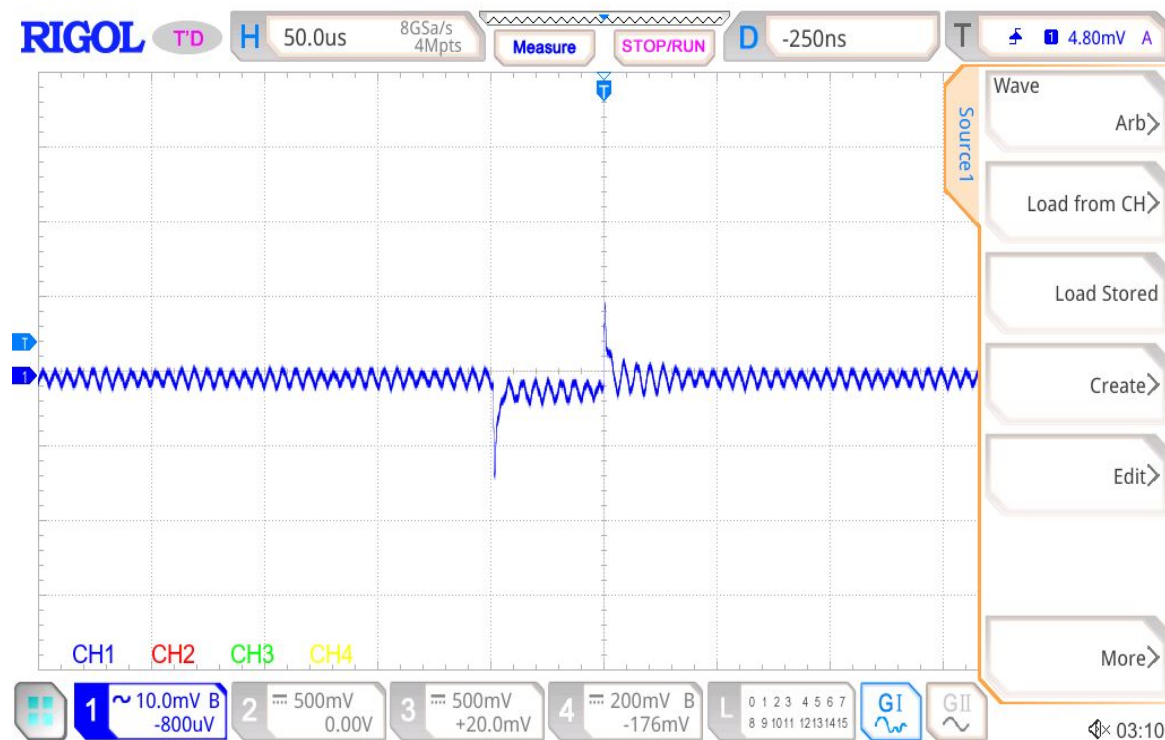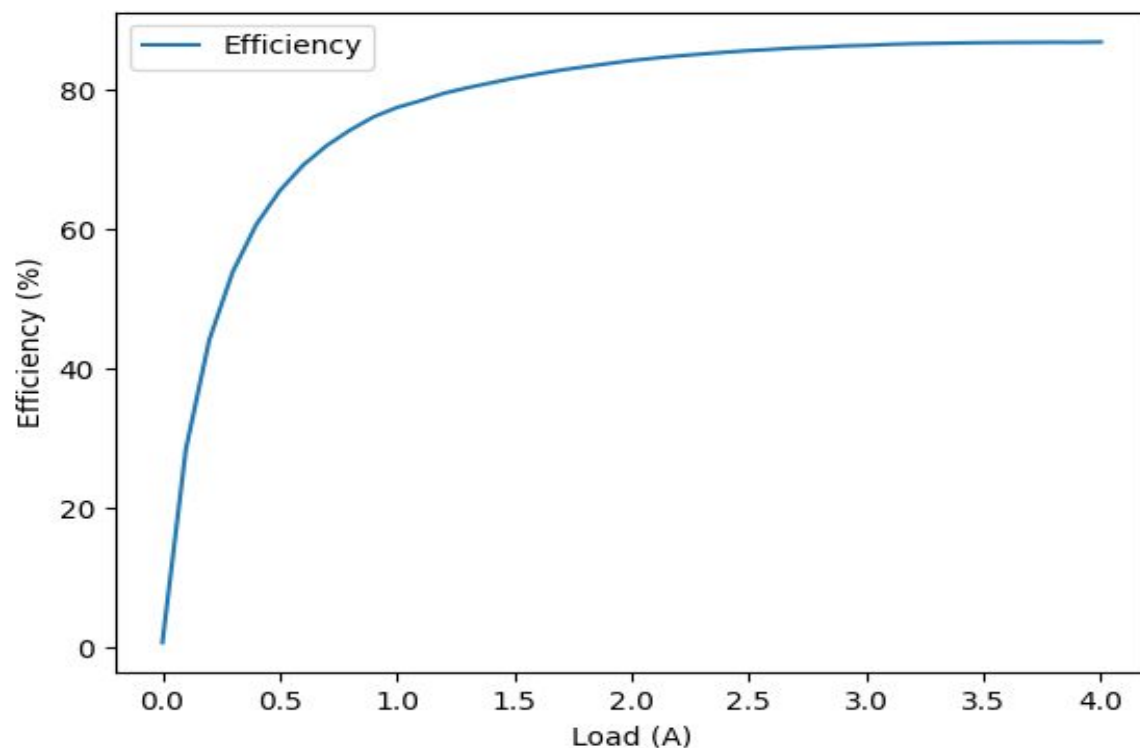


V_{out} = 1.5V
Transient 2.68A – 4A @ 10 A/μs
V_{pp} = 25 mV
F_{sw} = 0.571 MHz
L = 4.7 μH, C = 1x47 uF

Ripple

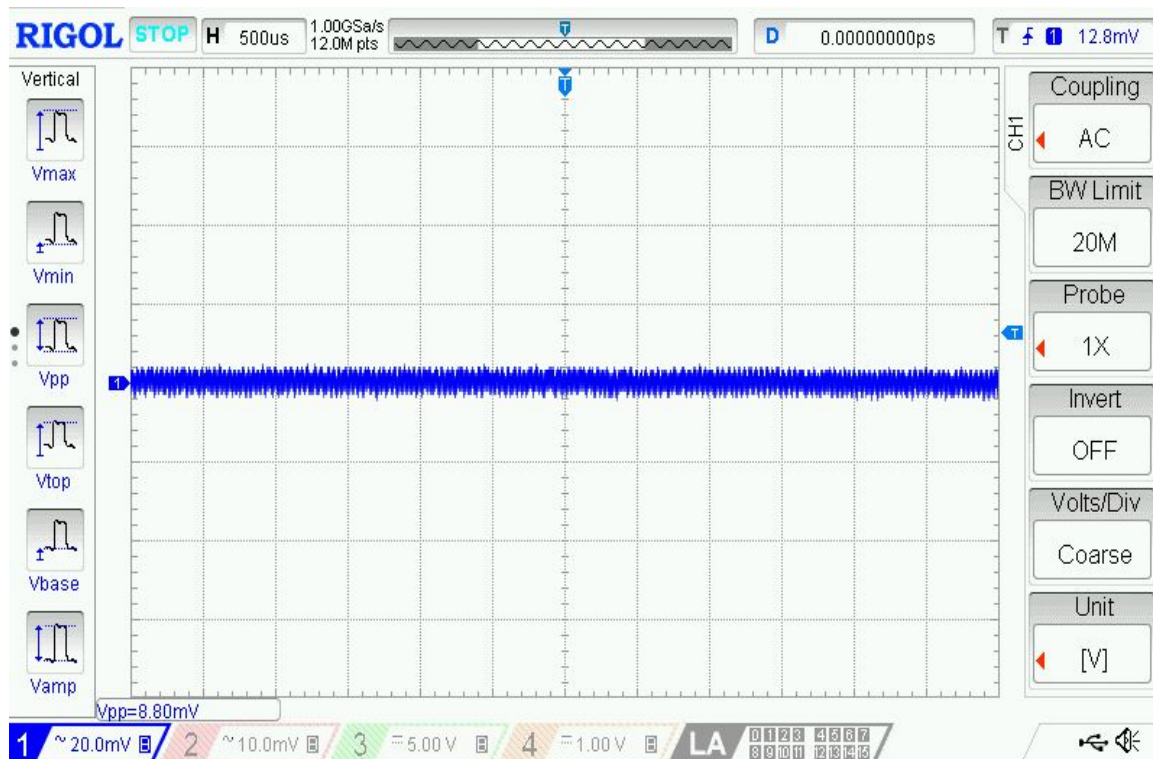

No Load
 $V_{PP} = 8.80 \text{ mV}$

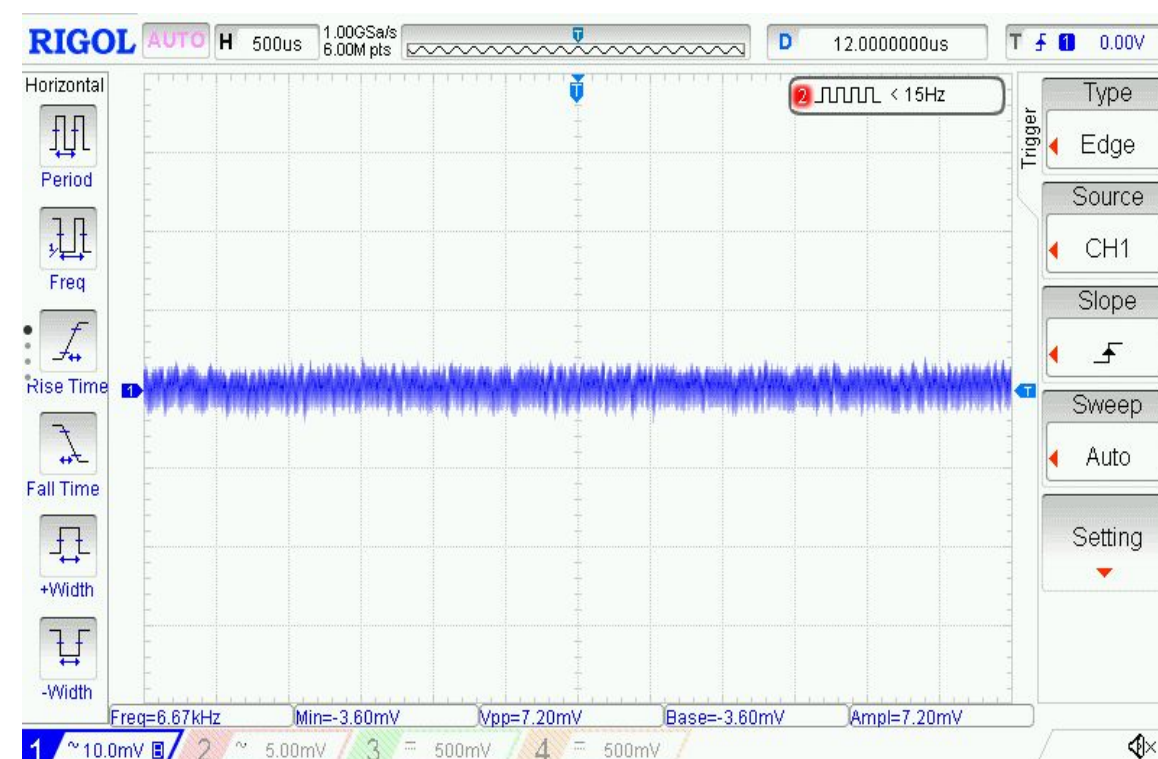

4 A Load
 $V_{PP} = 7.20 \text{ mV}$



$V_{out} = 1.5 \text{ V}$

MGTAVCC

0.88 V / 3.1 A


- C200 (Synchronous Buck)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744383560056
- $C = 9 \times 47 \mu\text{F}$

Efficiency & Transient

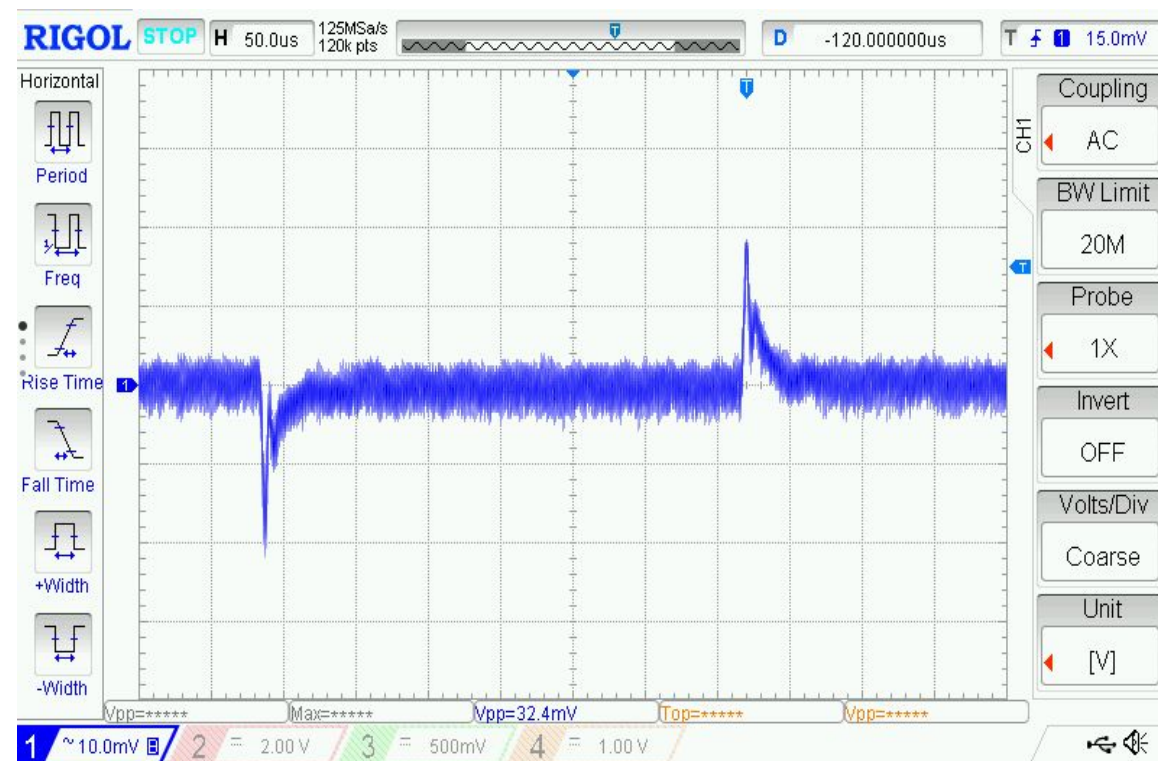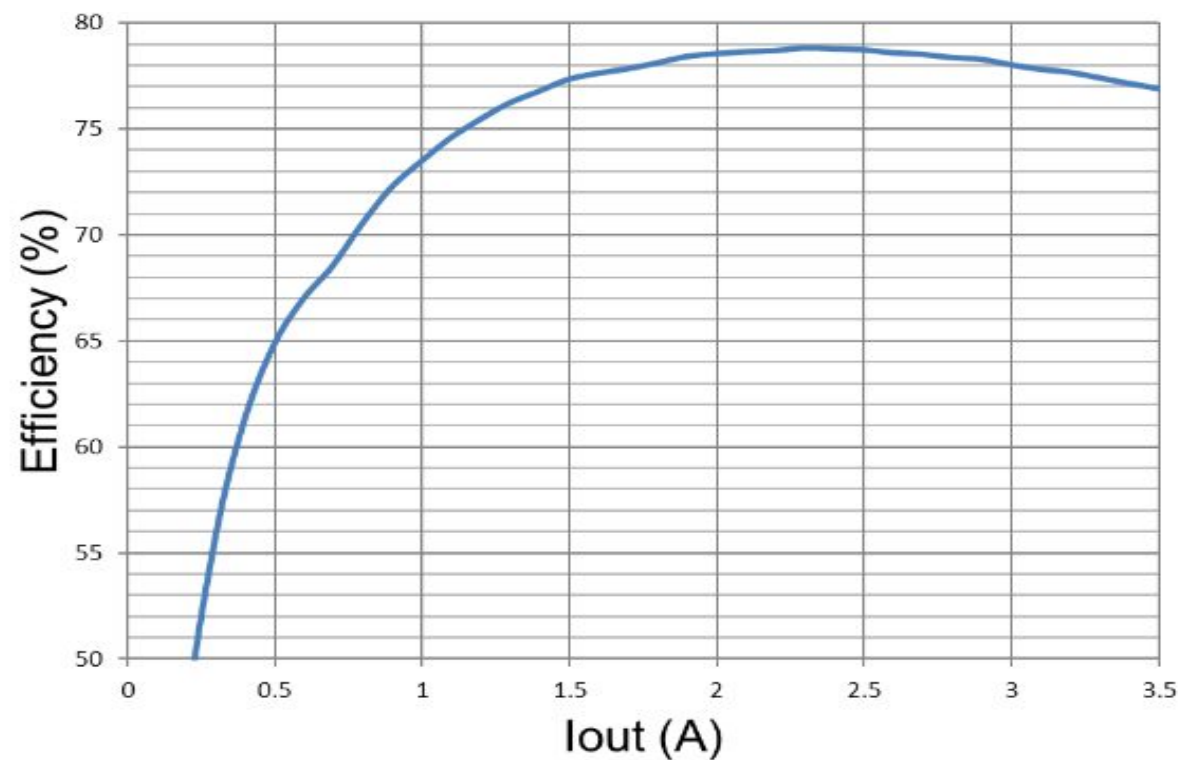


$V_{out} = 0.88V$
Transient 2.625A – 3.5A @ 10 A/ μ s
 $V_{pp} = 32.4\text{ mV}$
 $F_{sw} = 0.571\text{ MHz}$
 $L = 0.56\text{ }\mu\text{H}$, $C = 9x47\text{ }\mu\text{F}$

Ripple

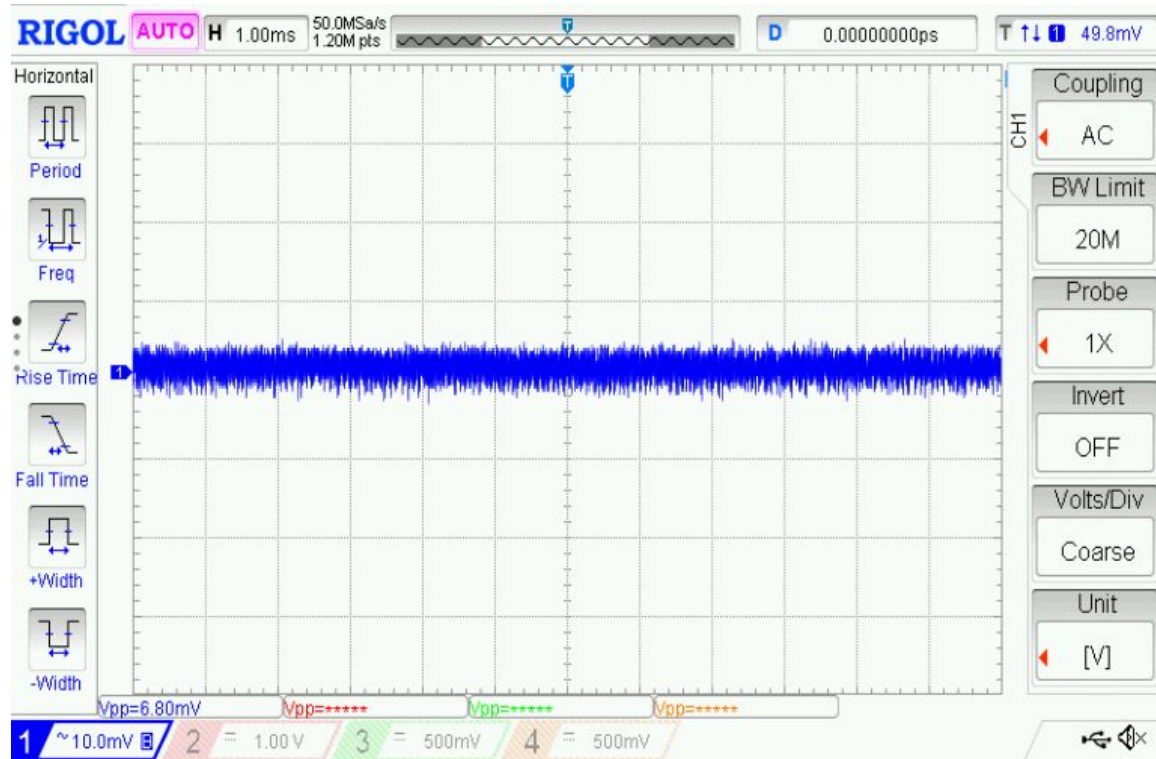

No Load
 $V_{PP} = 6.80 \text{ mV}$

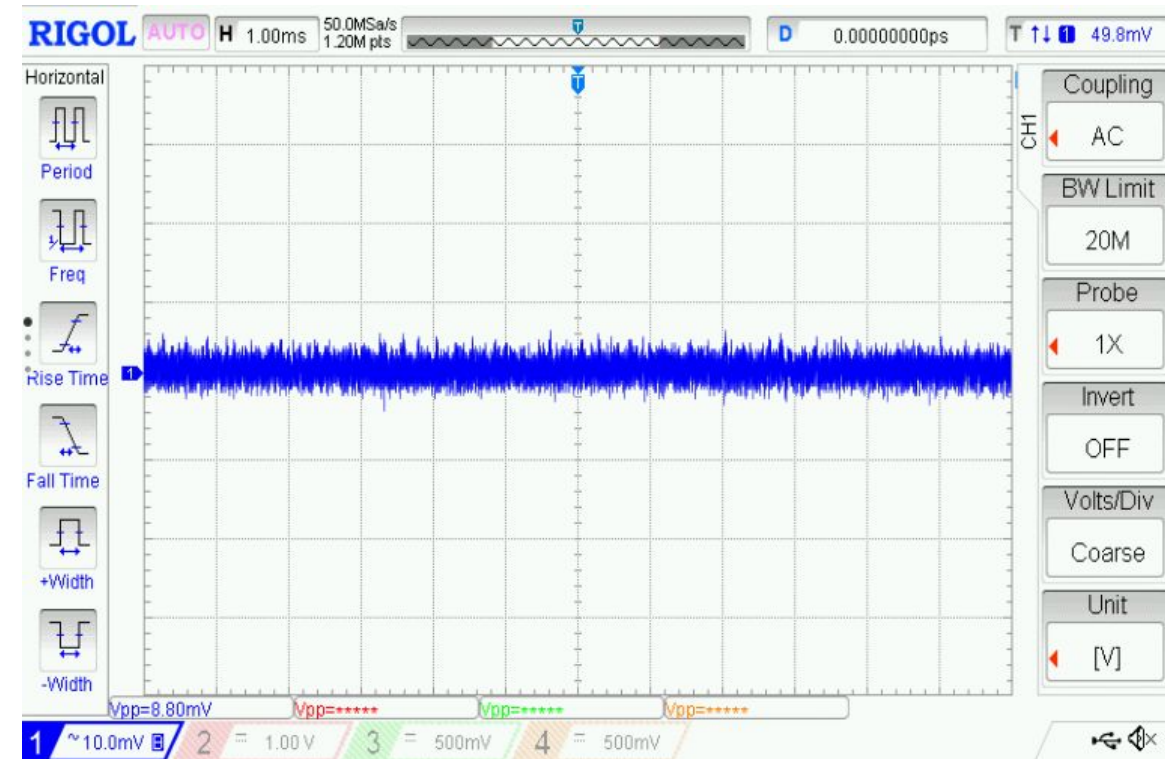

3.1 A Load
 $V_{PP} = 8.80 \text{ mV}$

$V_{out} = 0.88 \text{ V}$

MGTYVCCAUX

1.5 V / 0.29 A



- C750 (Load switch)

MGTAVTT

1.2 V / 4.81 A


- C150 (Asynchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 2.2 \mu\text{H}$, P/N Wurth 744311220
- $C = 7 \times 47 \mu\text{F}$

Efficiency & Transient

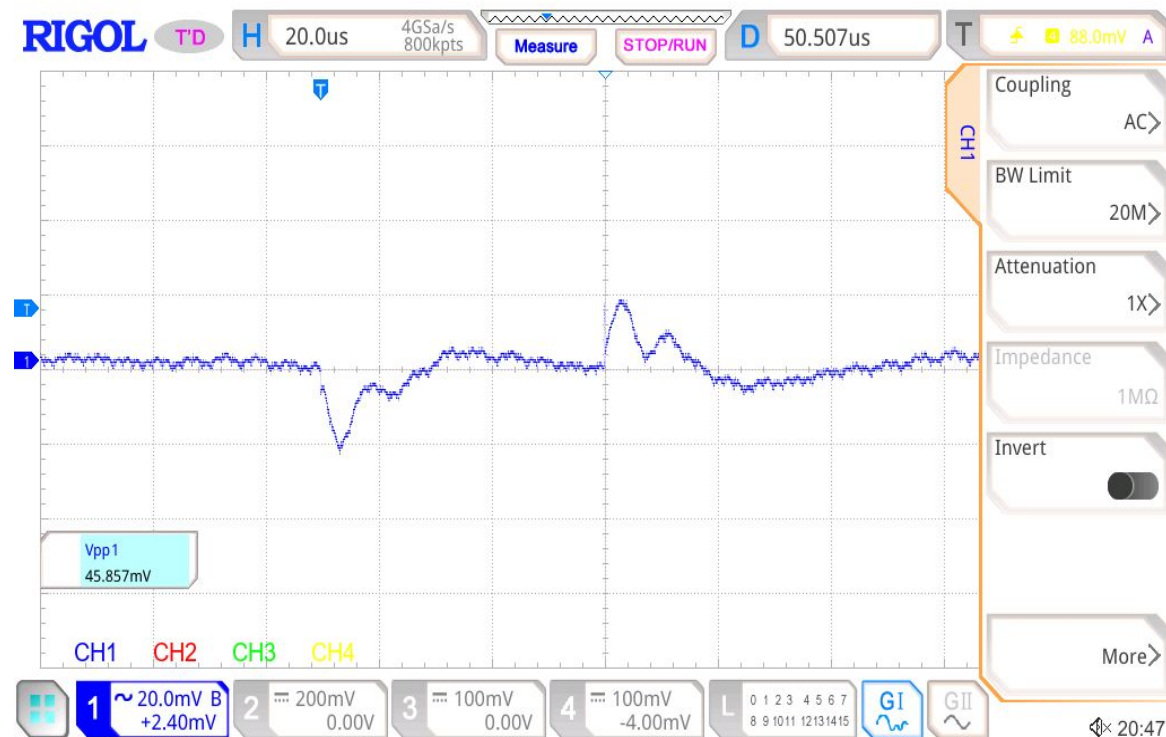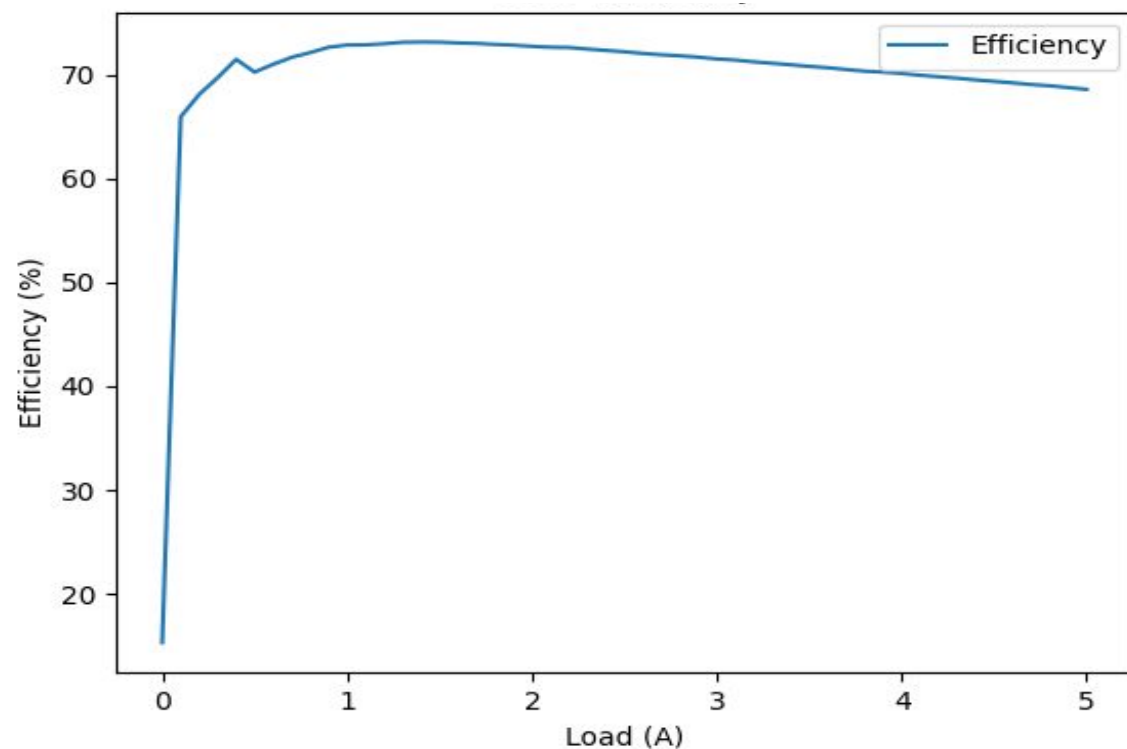


$V_{out} = 1.2V$
 Transient 3.61 – 4.81A @ 10 A/ μ s
 $V_{PP} = 45.85 \text{ mV}$
 $F_{sw} = 0.571 \text{ MHz}$
 $L = 2.2 \text{ }\mu\text{H}$, $C = 7 \times 47 \text{ }\mu\text{F}$

Ripple

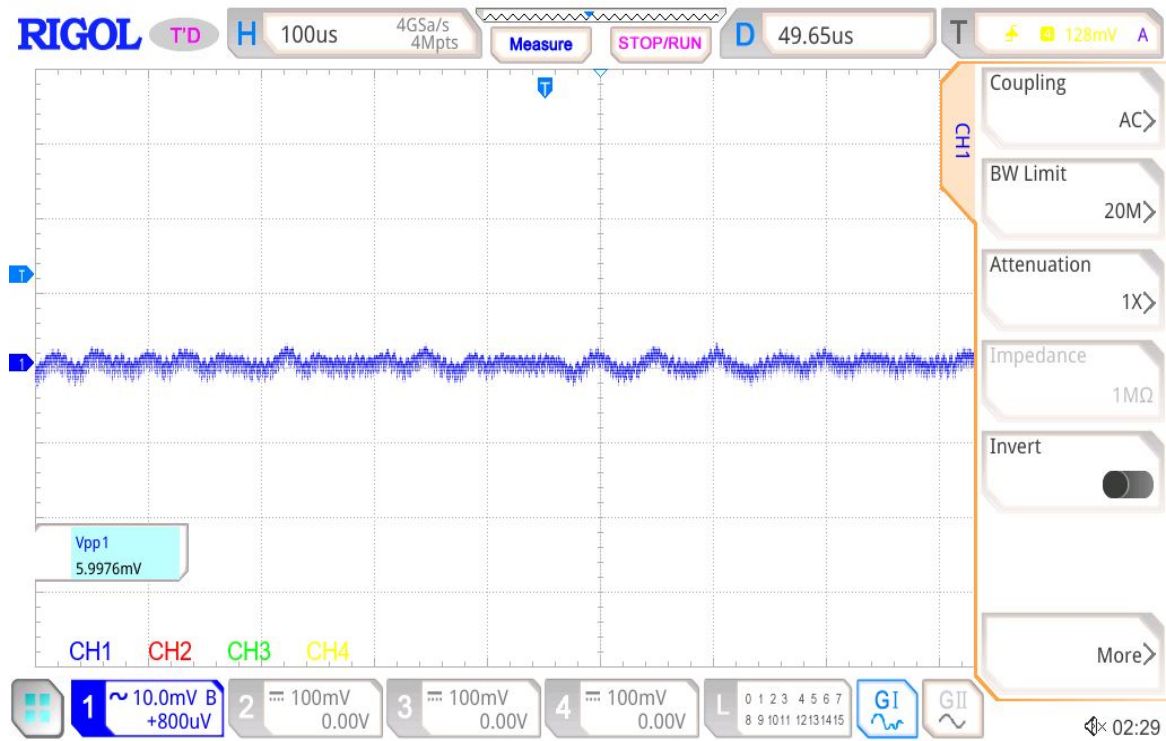

No Load
 $V_{PP} = 5.99 \text{ mV}$

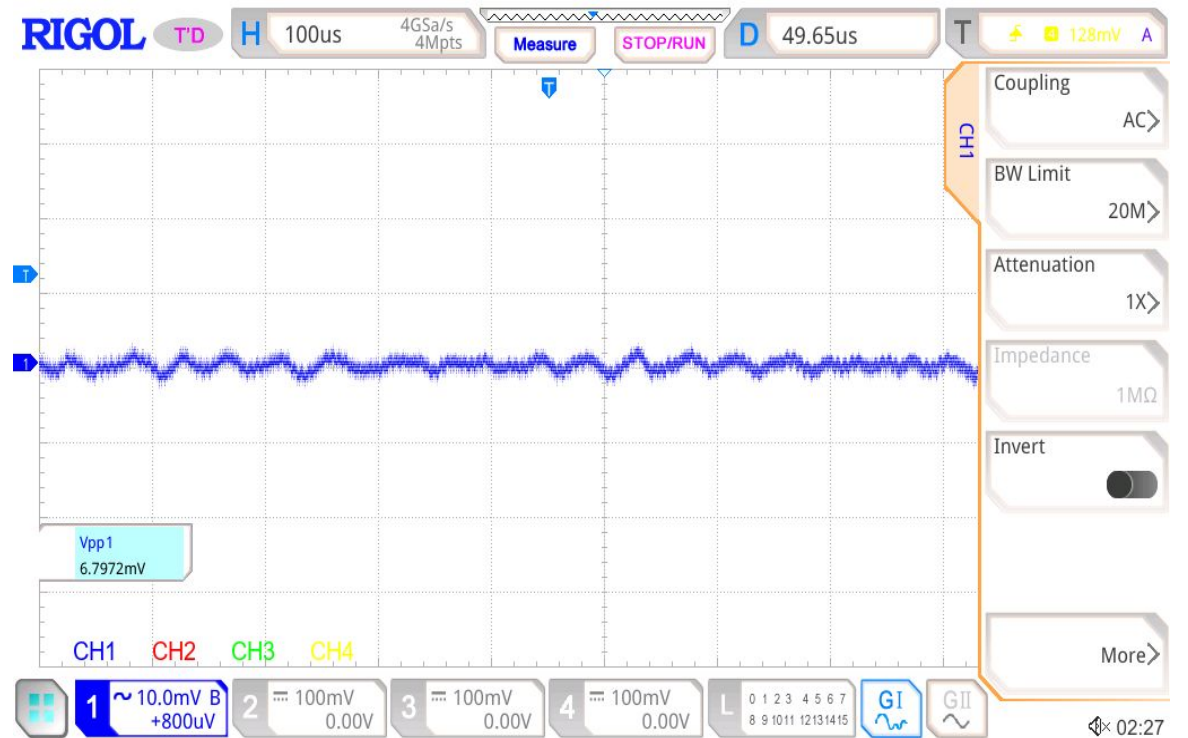

4.81 A Load
 $V_{PP} = 6.79 \text{ mV}$



$V_{out} = 1.2 \text{ V}$

VDDQ

1.2 V / 3 A


- C200 (Synchronous Buck)
- $F_{sw} = 0.571 \text{ MHz}$
- $L = 1 \text{ } \mu\text{H}$, P/N Wurth 74438366010
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

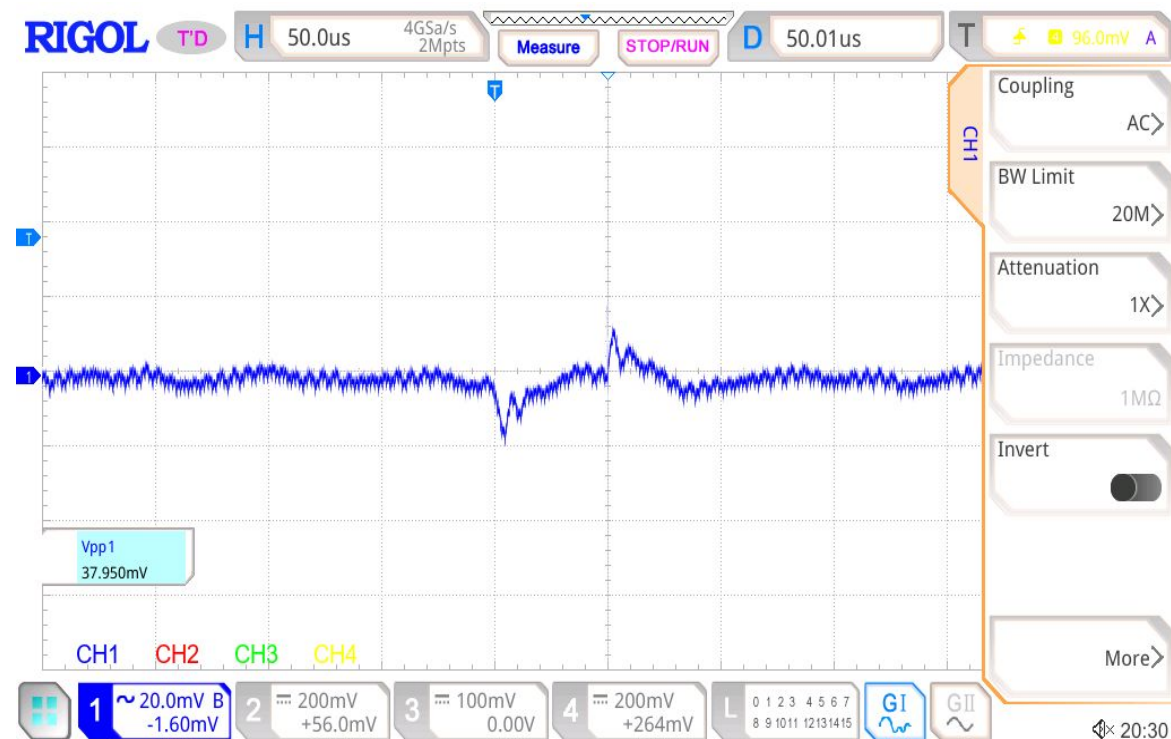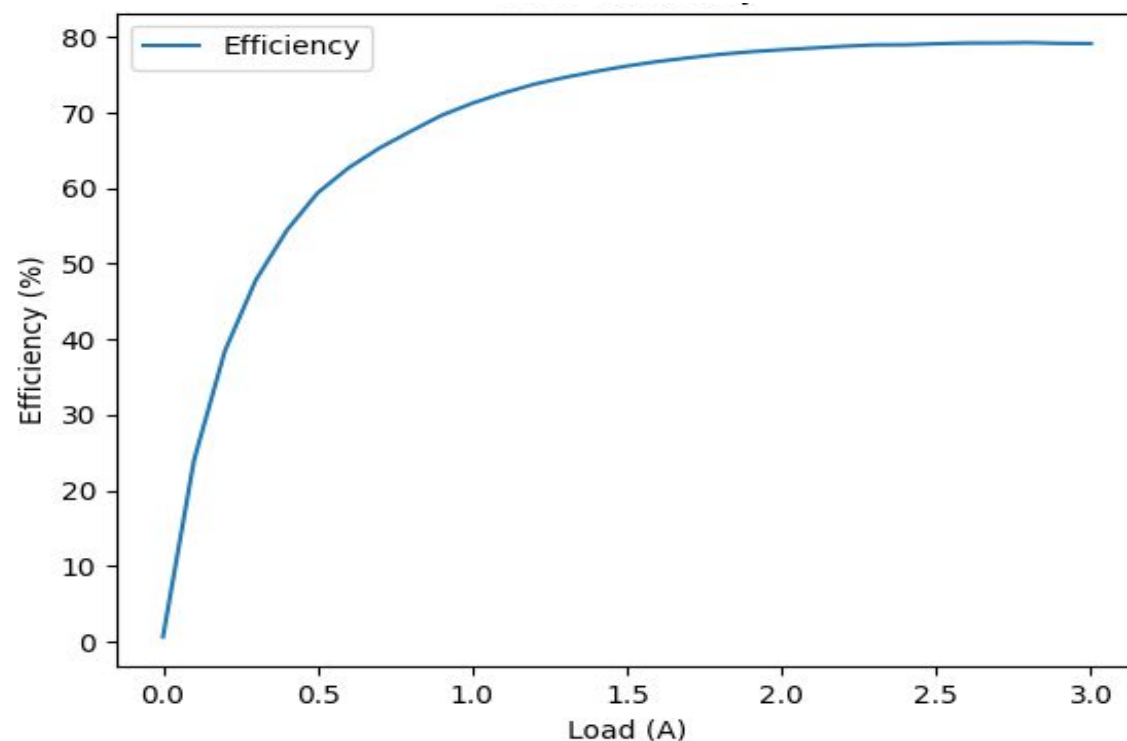


Vout = 1.2V
Transient 0.3 – 3A @ 10 A/ μ s
 V_{PP} = 37.95 mV
Fsw = 0.571 MHz
L = 1 μ H, C = 4x47 μ F

Ripple

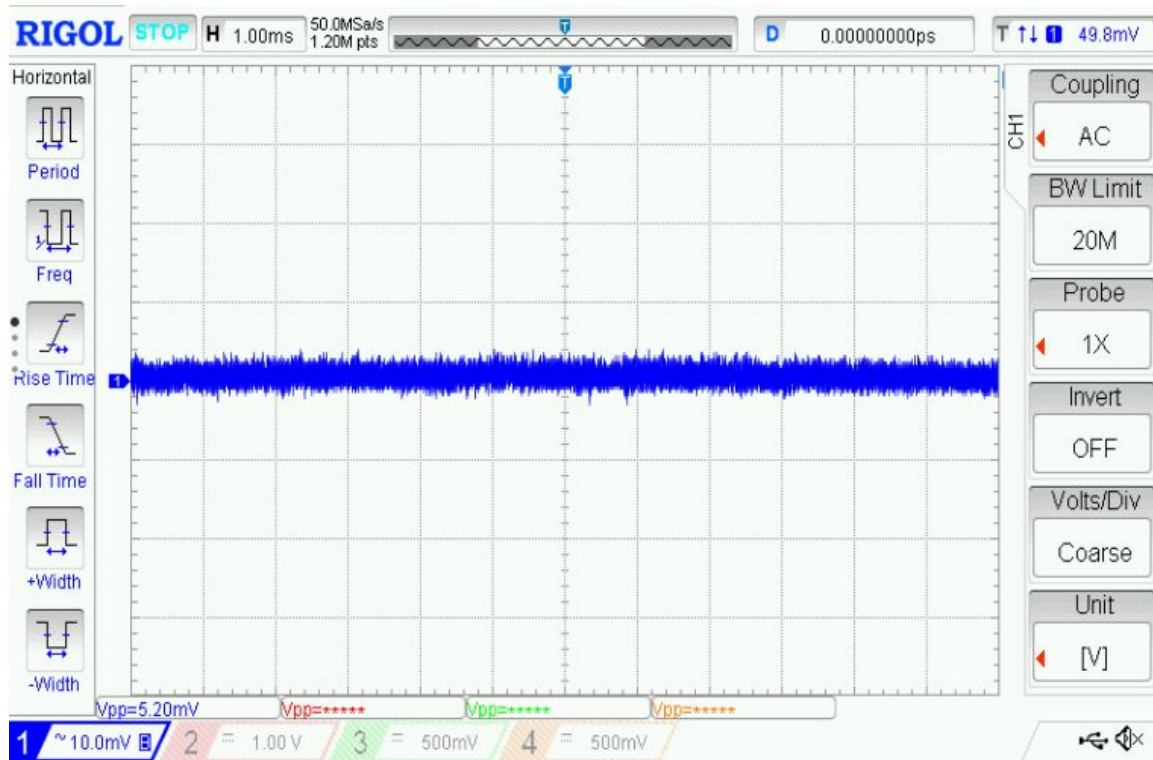

No Load
 $V_{PP} = 5.20 \text{ mV}$

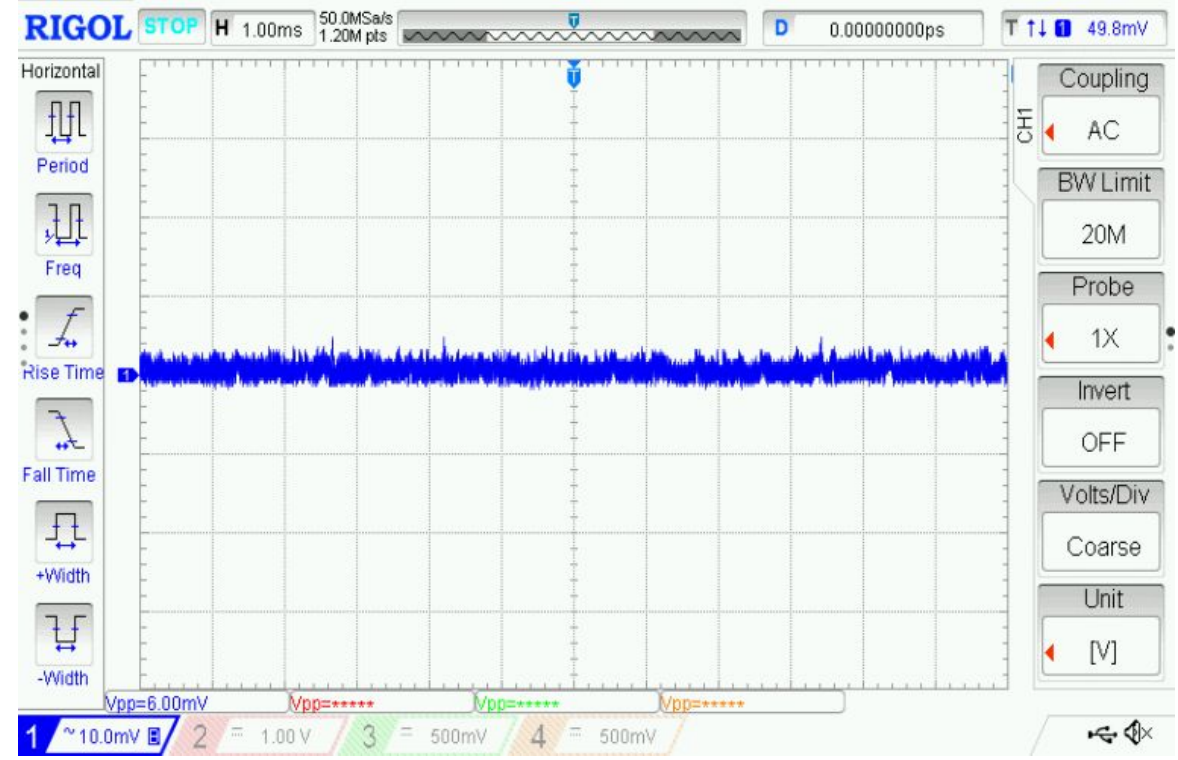

3 A Load
 $V_{PP} = 6.00 \text{ mV}$


$V_{out} = 1.2 \text{ V}$

VTT


0.6 V / 2 A

- C210 (VTT Terminator)
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.33 \text{ } \mu\text{H}$, P/N Wurth 744393440033
- $C = 8 \times 47 \text{ } \mu\text{F}$


Efficiency & Transient

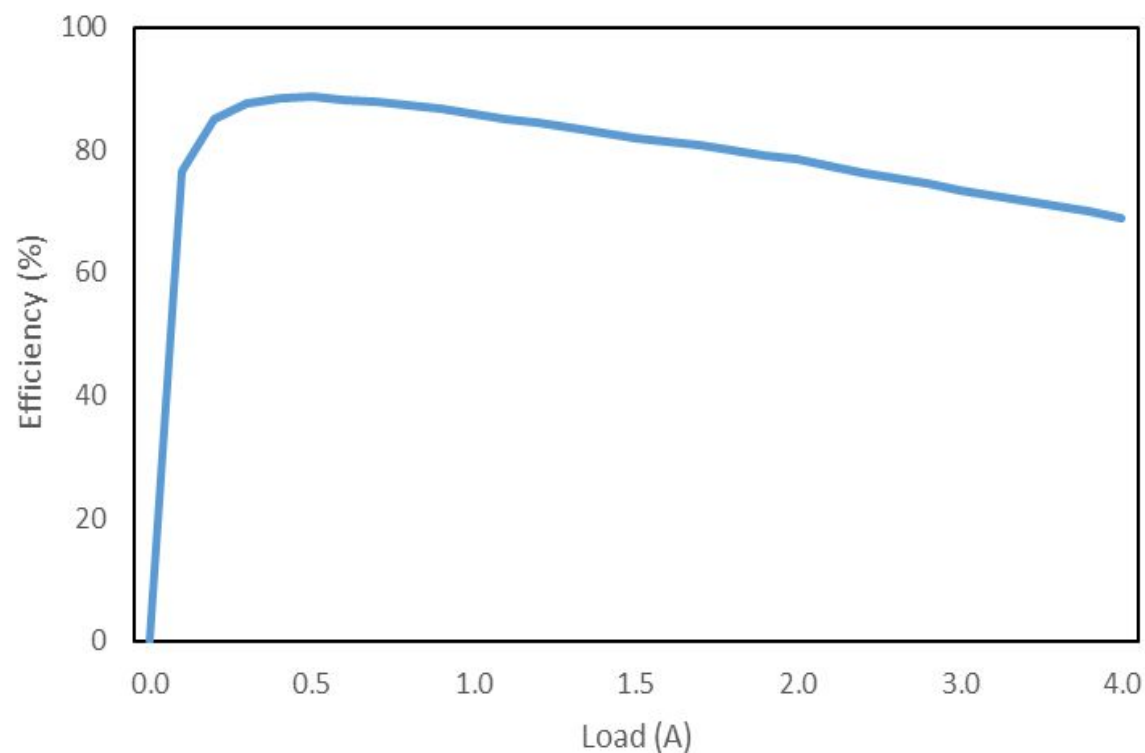

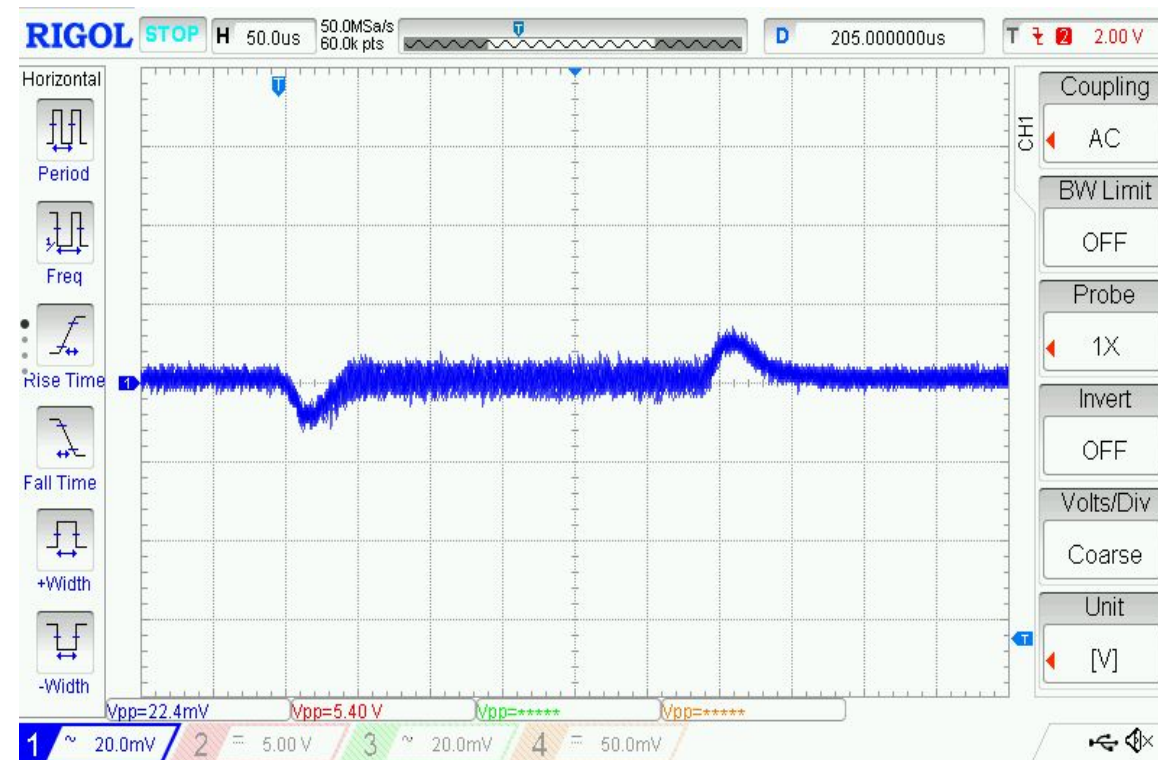
Vout = 0.6V
Transient 3 – 4A @ 10 A/ μ s
 $V_{PP} = 22.4$ mV
Fsw = 1 MHz
L = 0.33 μ H, C = 8x47 μ F



Ripple

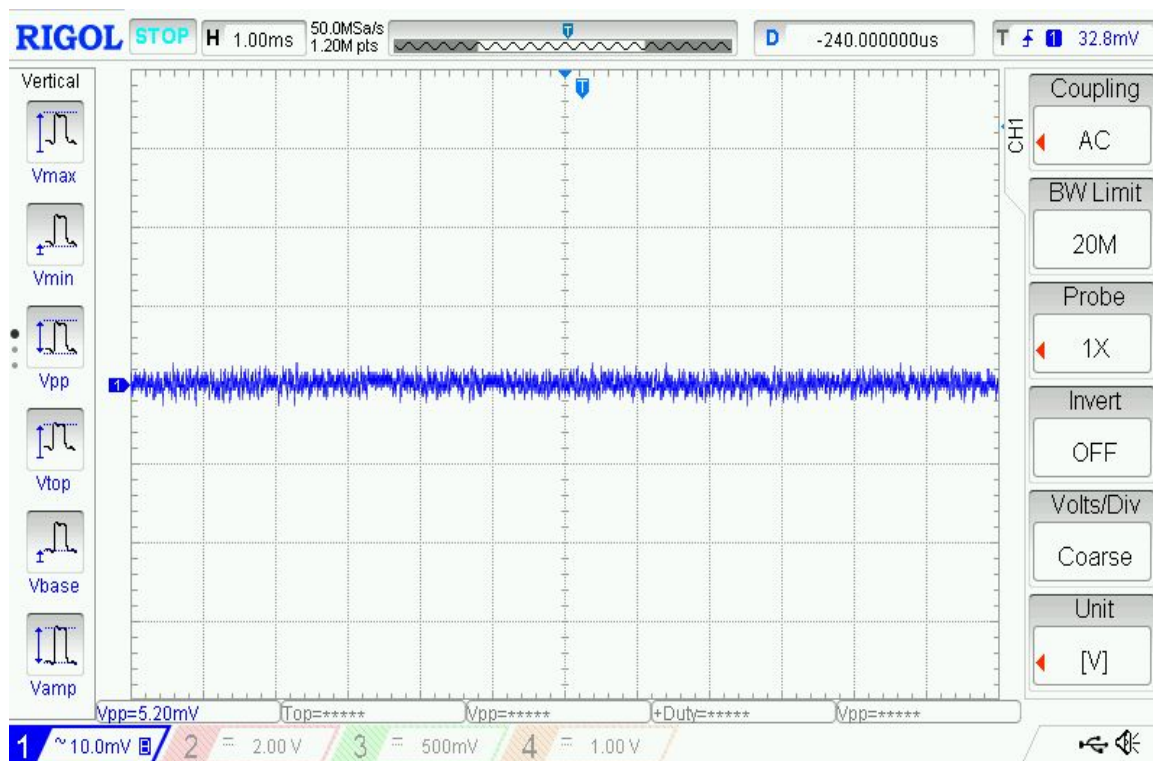


No Load
 $V_{PP} = 5.20 \text{ mV}$

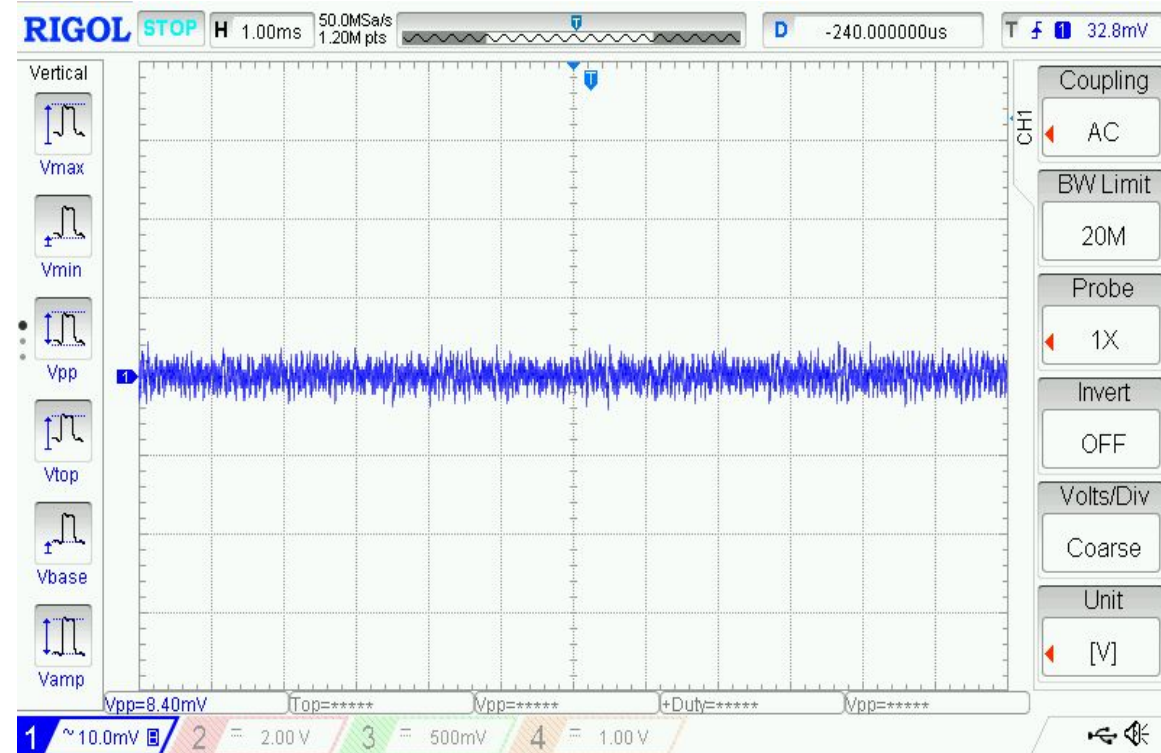

4 A Load
 $V_{PP} = 8.40 \text{ mV}$

$V_{out} = 0.6 \text{ V}$

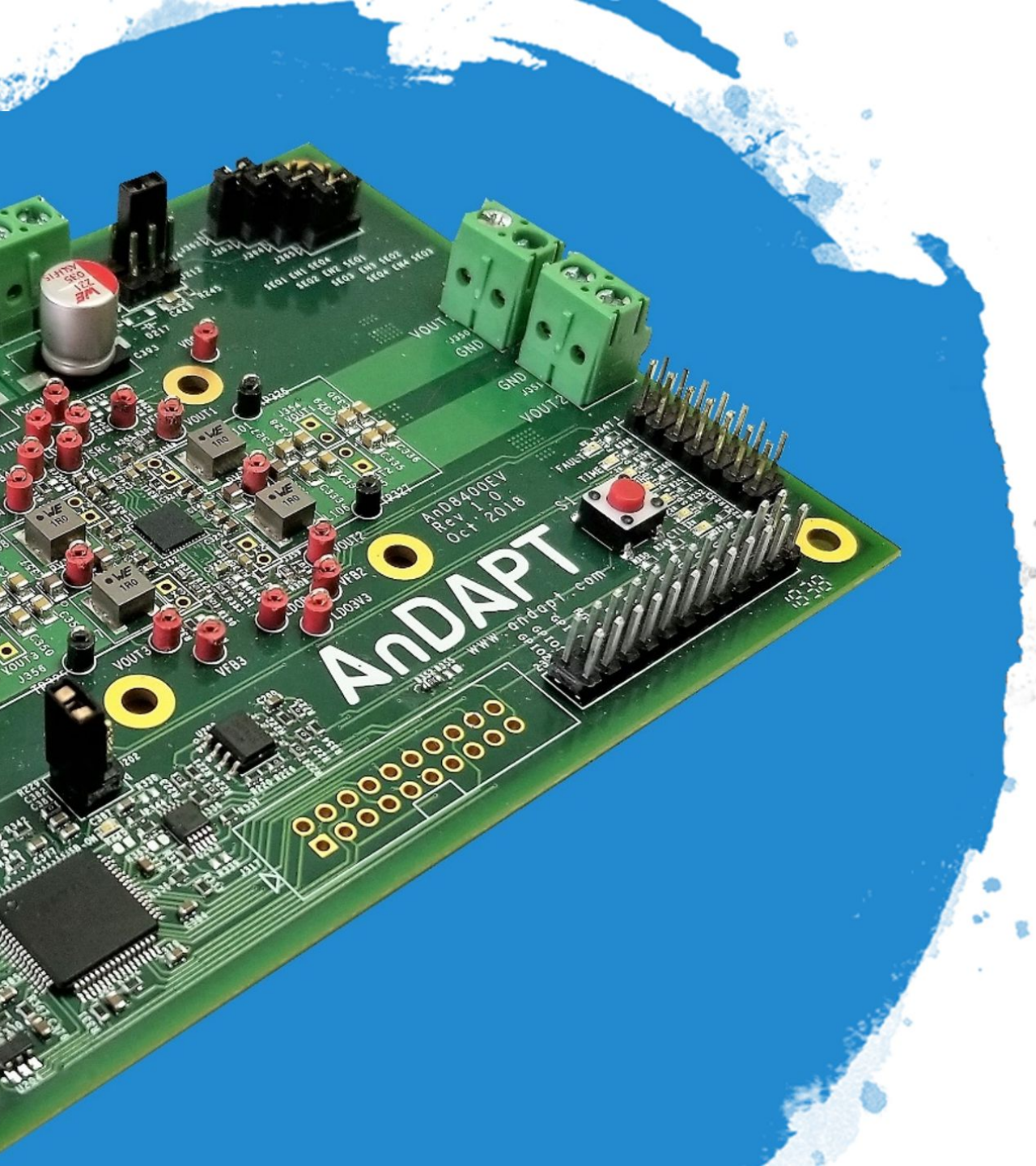

Thank You