 


Zynq UltraScale+ (Minimum Rails) Cost-optimized Portfolio

Mapping & Test Data



Contents

- Xilinx Zynq UltraScale+ (ZU+) family of devices SKUs (minimum rails/rail consolidation) in cost-optimized portfolio
- Zynq US+ power maps
- AnDAPT integrated power supply design
- Bench data including efficiency, transients, ripple for each power rail
- AnDAPT PMICs meet or exceed all power performance specs provided by Xilinx for ZU+ family FPGAs

*Xilinx document: https://www.xilinx.com/support/documentation/user_guides/ug583-ultrascale-pcb-design.pdf

Zynq UltraScale+ (ZU+) Device SKUs Covered- Minimum Rails

Supported SKUs
XCZU1
XCZU2
XCZU3

List may not be exhaustive. Please contact AnDAPT for further details

AnDAPT Confidential

Zynq UltraScale+ (Minimum Rails)

 


Image courtesy Xilinx: https://www.xilinx.com/support/documentation/user_guides/ug583-ultrascale-pcb-design.pdf

Power Tree: Zynq UltraScale+ (Minimum Rails)

PVIN = 12V

#	Rail	Seq	Vout (V)	Iout (A)	Comment
1	VCCINT, VCCBRAM, VCCINT_IO, VCC_PSINTLP, VCC_PSINTFP, VCC_PSINTFP_DDR	1	0.72/0.85	2-4.2	
2	VCCAUX, VCCAUX_IO, VCCADC, VCC_PSAUX, VCC_PSADC, VCC_PSDDR_PLL	2	1.8	0.5-1	
3	VCC_PSPLL	3	1.2	0.1	
4	VCCO_PSDDR, DDR_VDDQ/VDD	4	1.1-1.5	3	
5	VCCO_PSIO	5	1.8-3.3	0.5	
6	VTT	6	VCCO_PSDD R/2	2	


Power Tree Mapping: Zynq UltraScale+ (Minimum Rails)

PVIN = 12V


#	Rail	Seq	Power Component	Type	Upstream Rail	Vinput (V)	Vout (V)	Iout (A)	AnDAPT PMIC
1	VCCINT (VCCINT, VCCBRAM, VCCINT_IO, VCC_PSINTLP, VCC_PSINTFP, VCC_PSINTFP_DDR)	1	C200	Sync Buck	PVIN	12	0.72	4.2	ARD_X_ZUM_A1_IC1
2	VCCAUX (VCCAUX, VCCAUX_IO, VCCADC, VCC_PSAUX, VCC_PSADC, VCC_PSDDR_PLL)	2	C150	Async Buck	PVIN	12	1.8	1 + 0.5 + 0.1	ARD_X_ZUM_A1_IC1
3	VCC_PSPLL	3	C710	LDO	VCCAUX	1.8	1.2	0.1	ARD_X_ZUM_A1_IC1
4	VCCO_PSDDR (VCCO_PSDDR, DDR_VDDQ/VDD)	4	C150	Async Buck	PVIN	12	1.2	3	ARD_X_ZUM_A1_IC1
5	VCCO_PSIO	5	C750	Load Switch	VCCAUX	1.8	1.8	0.5	ARD_X_ZUM_A1_IC1
6	VTT	6	C210	VTT Term.	VCCO_PSDDR	1.2	0.6	1.5	ARD_X_ZUM_A1_IC1

Estimated total area estimated = 355 mm²


Power Tree Mapping

 


Mapping (WebAmP View)

 

Mapping (Thermal View)

 

 
AmP8DB6QF65
ARD_X_ZUM_A1_IC1
Total Area $\approx 713.5 \text{ mm}^2$
Routing Efficiency:
75% Optimized Density Layout



Bench Data

Zynq UltraScale+
(Minimum Rails)



Integrated Sequencer Graphic (Turn ON)

 

VCCINT (VCCINT, VCCBRAM, VCCINT_IO, VCC_PSINTLP, VCC_PSINTFP, VCC_PSINTFP_DDR) 0.72 V / 4.2 A

- C200 Sync Buck
- $F_{sw} = 1 \text{ MHz}$
- $L = 0.56 \mu\text{H}$, P/N Wurth 744393440056
- $C = 9 \times 47 \mu\text{F}$

Efficiency & Transient

  

$V_{out} = 0.72\text{ V}$


Transient 3.15A – 4.2A @ 100 A/ μ s

$V_{pp} = 25.6\text{ mV}$


$F_{sw} = 1\text{ MHz}$

$L_{out} = 0.56\text{ }\mu\text{H}$, $C_{out} = 9 \times 47\text{ }\mu\text{F}$

Ripple

 

No Load
 $V_{PP} = 5.6 \text{ mV}$

 



$V_{out} = 0.72 \text{ V}$

4.2A Load
 $V_{PP} = 6.4 \text{ mV}$

VCCAUX (VCCAUX, VCCAUX_IO, VCCADC, VCC_PSAUX, VCC_PSADC, VCC_PSDDR_PLL) 1.8 V / 1.6 A

- C150 Async Buck
- $F_{sw} = 571 \text{ kHz}$
- $L = 2.2 \mu\text{H}$, P/N Wurth 744311220
- $C = 2 \times 47 \mu\text{F}$

Efficiency & Transient

  

$V_{out} = 1.8 \text{ V}$


Transient 0.16 A – 1.6 A @ 2.5 A/ μ s

$V_{pp} = 57.6 \text{ mV}$


$F_{sw} = 571 \text{ kHz}$

$L_{out} = 2.2 \text{ }\mu\text{H}$, $C_{out} = 2 \times 47 \text{ }\mu\text{F}$

Ripple

 

No Load
 $V_{PP} = 11.6 \text{ mV}$

 

$V_{out} = 1.8 \text{ V}$


1.6A Load
 $V_{PP} = 8.0 \text{ mV}$

VCC_PSPLL

1.2 V / 0.1 A

- C710 LDO
- C = 10 μ F

Transient

 


$V_{out} = 1.2 \text{ V}$

Transient 0 A – 0.1 A @ 2.5 A/ μ s


$V_{PP} = 6.8 \text{ mV}$

$C = 10 \text{ }\mu\text{F}$

Ripple

 

No Load
 $V_{PP} = 4.8 \text{ mV}$

 



$V_{out} = 1.2 \text{ V}$

0.1 A Load
 $V_{PP} = 8.8 \text{ mV}$

VCCO_PSDDR (VCCO_PSDDR, DDR_VDDQ/VDD) 1.2 V / 3 A

- C150 Async Buck
- $F_{sw} = 571 \text{ kHz}$
- $L = 1 \text{ } \mu\text{H}$, P/N Wurth 74438356010
- $C = 4 \times 47 \text{ } \mu\text{F}$

Efficiency & Transient

  

Vout = 1.2 V


Transient 2.25 A – 3 A @ 2.5 A/μs

$V_{pp} = 31.2 \text{ mV}$

Fsw = 571 kHz


Lout = 1μH, Cout = 4 x 47 μF

Ripple

 

No Load
 $V_{PP} = 6.0 \text{ mV}$

$V_{out} = 1.2 \text{ V}$

 


3 A Load
 $V_{PP} = 4.8 \text{ mV}$

VTT

0.6 V / 1.5 A

- C210 VTT_Terminator
- $F_{sw} = 1 \text{ MHz}$
- $L = 1 \text{ } \mu\text{H}$, P/N Wurth 74438366010
- $C = 8 \times 47 \text{ } \mu\text{F}$

Transient

 

$V_{out} = 0.6 \text{ V}$


Transient $1.125\text{A} - 1.5\text{A} @ 2.5 \text{ A}/\mu\text{s}$

$V_{pp} = 22.0 \text{ mV}$


$F_{sw} = 1 \text{ MHz}$

$L_{out} = 1 \mu\text{H}$, $C_{out} = 8 \times 47 \mu\text{F}$

Ripple

 

No Load
 $V_{PP} = 2.8 \text{ mV}$

 

$V_{out} = 0.6 \text{ V}$

1.5A Load
 $V_{PP} = 2.0 \text{ mV}$



Thank You