

Description

Careful design considerations must be used when selecting and designing linear power components. While P_{Vin} (power fet drain) Voltage range is explicitly specified in the datasheets of these power components, the chip bias voltage V_{in} must respect specific conditions in order to obtain the desired operation.

Specifically:

- For C710/C715 LDO Power Component, V_{in} must be 2.3V higher than the desired output voltage.
- For C750/C755 Load Switch Power Component, V_{in} must be 2.0V higher than the desired output voltage.

If these conditions are not met, the application might still be possible with the addition of small external passive components. Please contact AnDAPT factory for application support and example schematics.

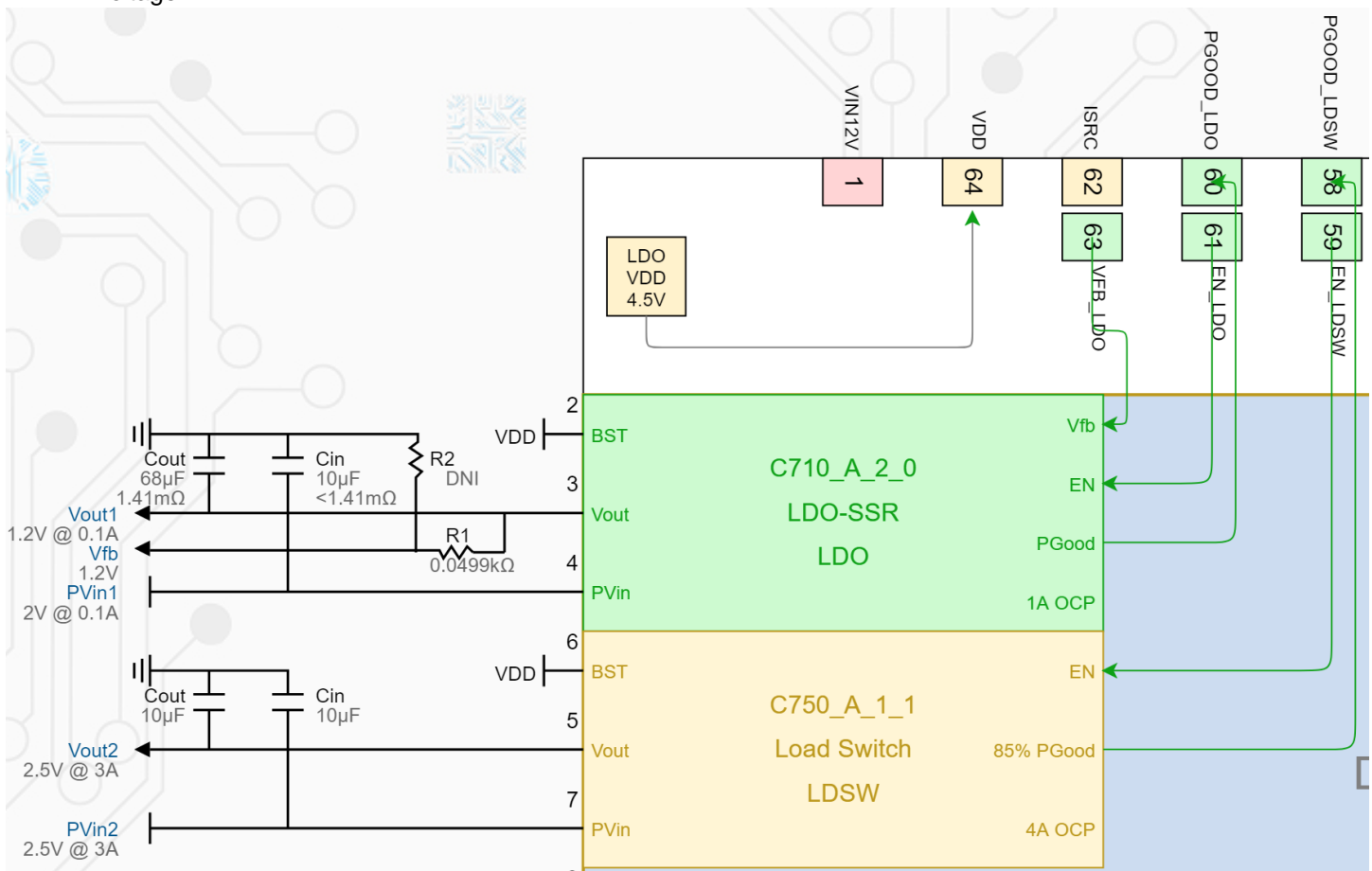


Figure 1. LDO and LDSW example WebAmP Design View showing V_{in} = 12V, PV_{in}1 = 2V and PV_{in}2 = 2.5V

Revision History

Date	Revision
01/30/2020	Initial release

AnDAPT

On-Demand Power Management

www.AnDAPT.com

Trademarks

© 2020 AnDAPT, Inc., the AnDAPT logo, AmP, WebAmP, AmPLink, AmPScope, WebAdapter and other designated brands included herein are trademarks of AnDAPT in the United States and other countries. All other trademarks are the property of their respective owners.