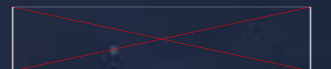



# C200/C220 Compensator Design: Voltage Mode Control

Sep 2<sup>nd</sup> 2022


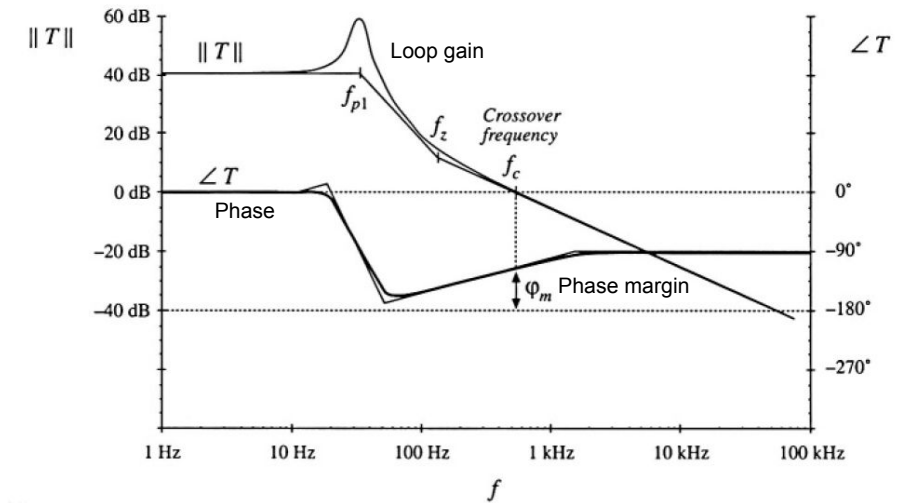
# Bode Plot Basics

- Why compensator?
  - In a Voltage regulator, the output filter ( $L_{out}$ ,  $C_{out}$ ) and the PWM modulator create the converter forward plant
  - Bode plots (loop gain and phase) are employed to analyze the frequency response of this linear system
  - In the loop, a Compensator is inserted to ensure stability and dynamic performance





# Compensator Design Example

- Power component: C200/C220
- $V_{in} = 12 \text{ V}$
- $V_{out} = 1.3 \text{ V}$
- $f_{SW} = 571 \text{ kHz}$
- $L_{out}, L = 1.1 \text{ uH}$
- $DCR = 3.15 \text{ m}\Omega$
- $C_{out}, C = 4 \times 47 \text{ uF}$
- Resonant frequency  $f_{LC} = 1/(2 * \pi * \sqrt{LC}) = 11 \text{ kHz}$
- Load: 0 – 5 A
- Voltage mode compensator parameters:  $f_{z1}, f_{z2}, \text{DC Gain}$





# Compensator Design 1

Gain = 650  
Z1 = 10.6 kHz  
Z2 = 40 kHz

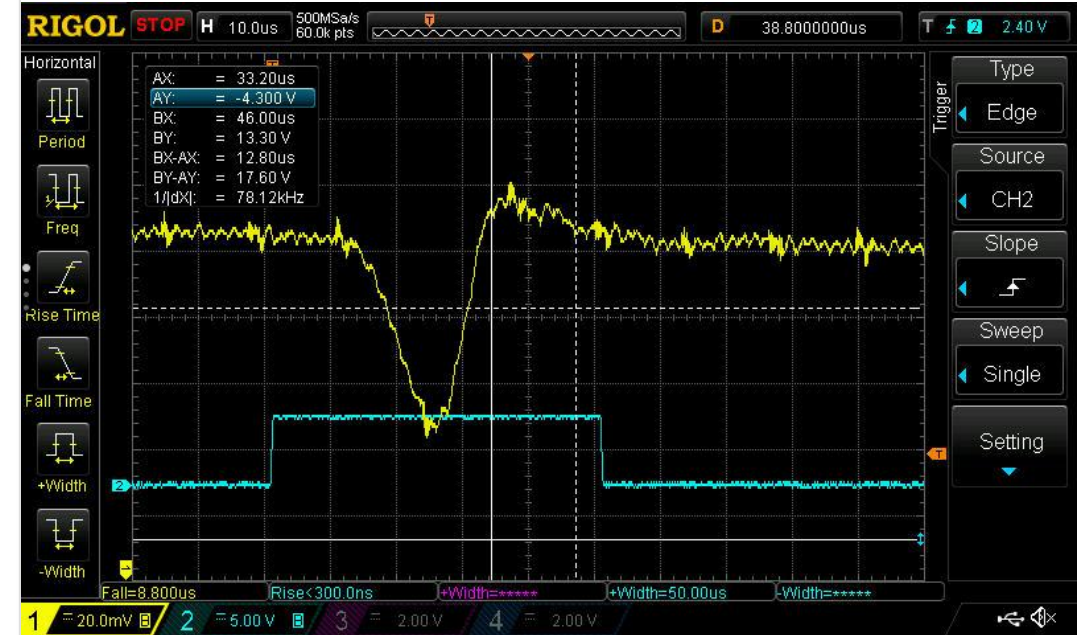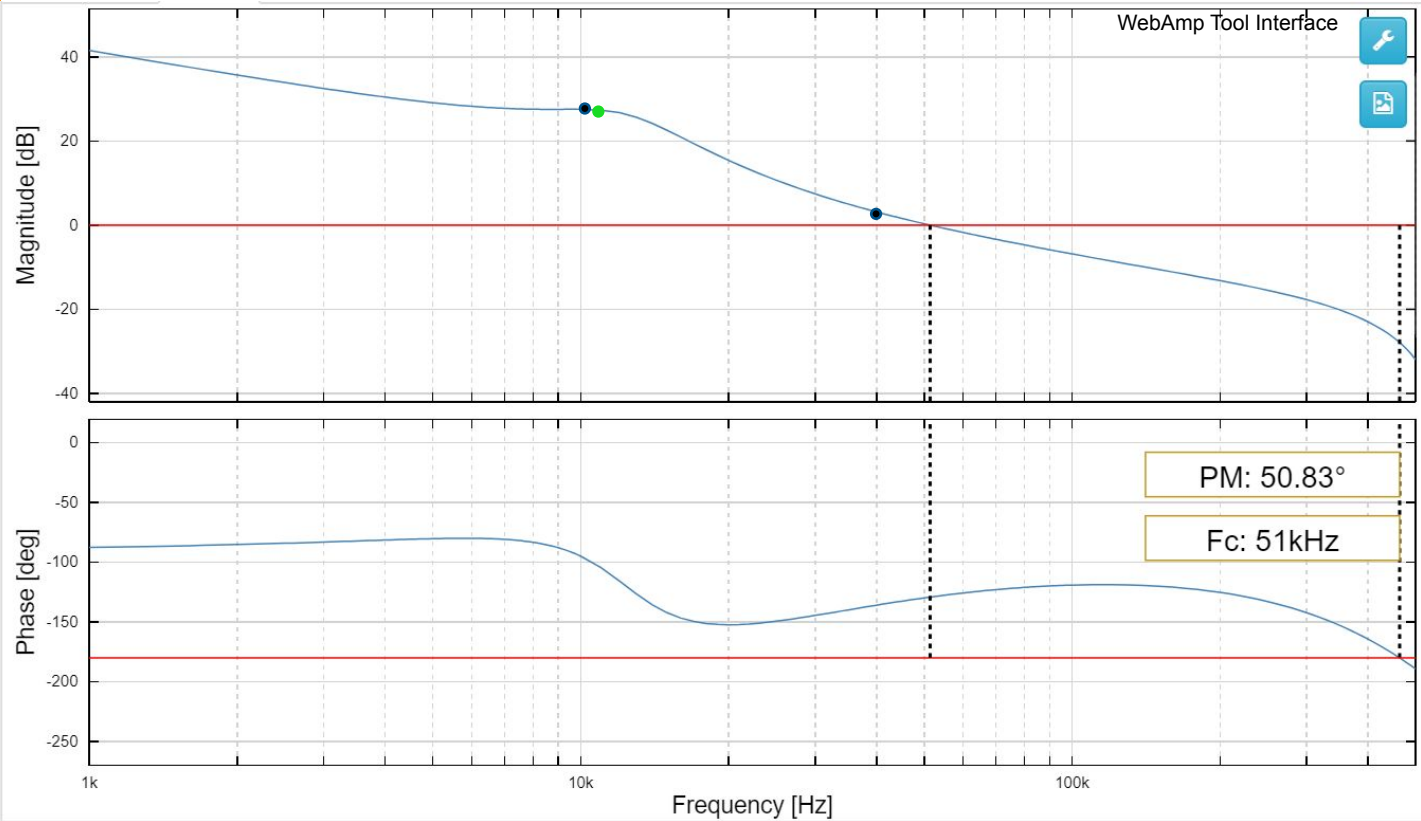


# Compensator Design 2 - Increasing $f_{z1}$

Gain = 650  
Z1 = 15 kHz  
Z2 = 40 kHz

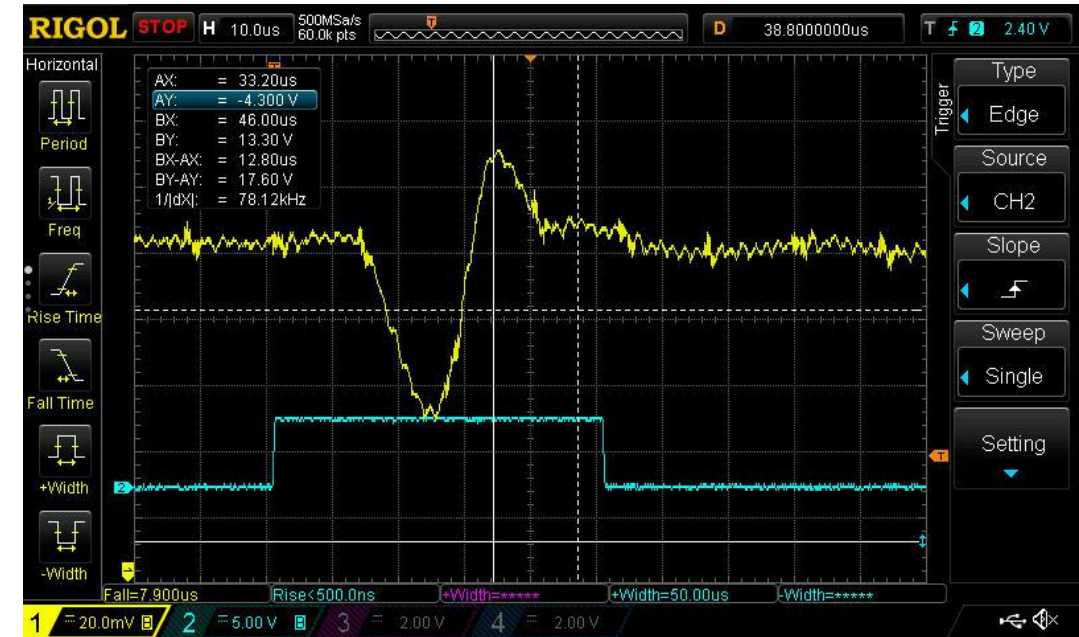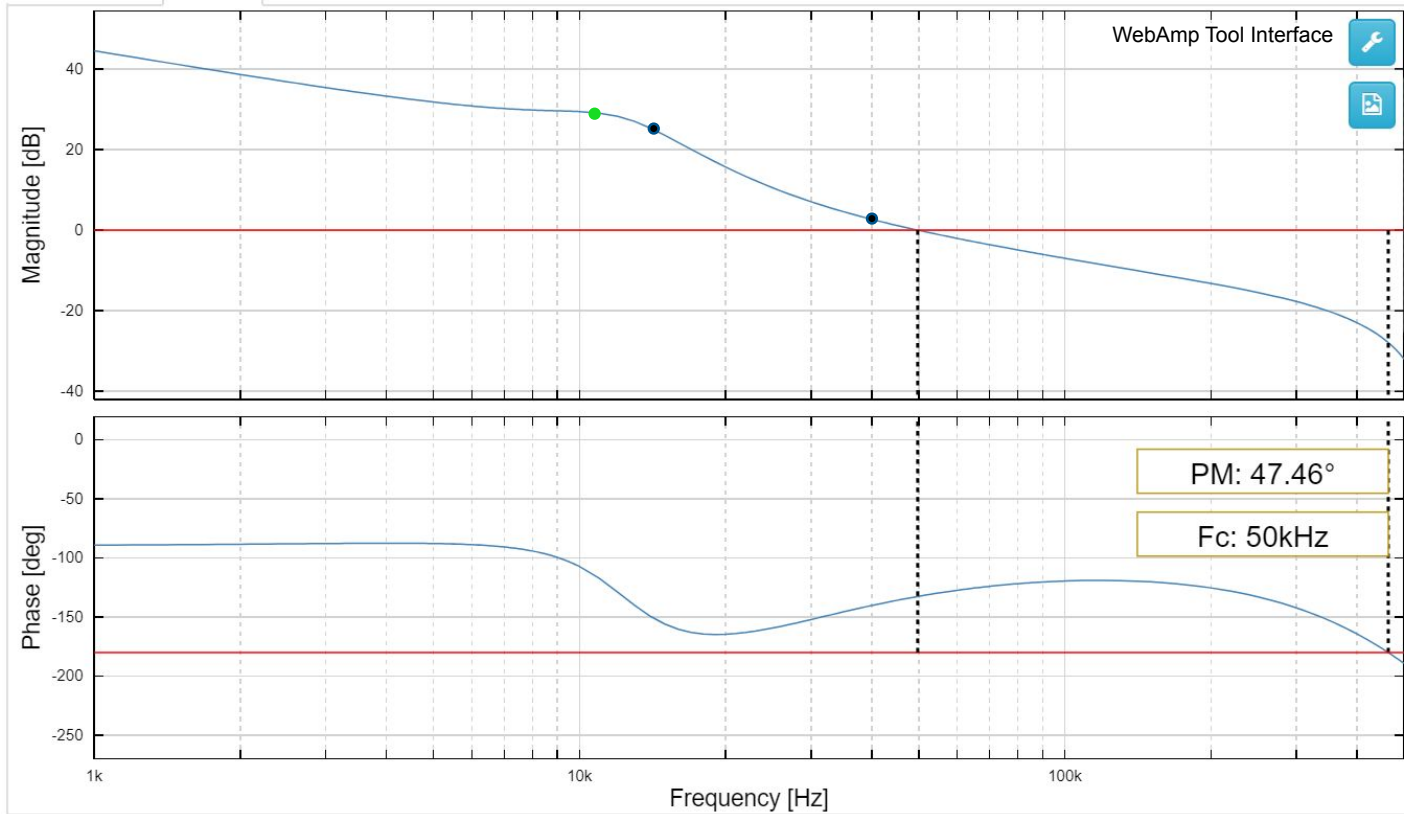


# Compensator Design 3 - Decreasing $f_{Z2}$

Gain = 650  
Z1 = 10.6 kHz  
Z2 = 20 kHz

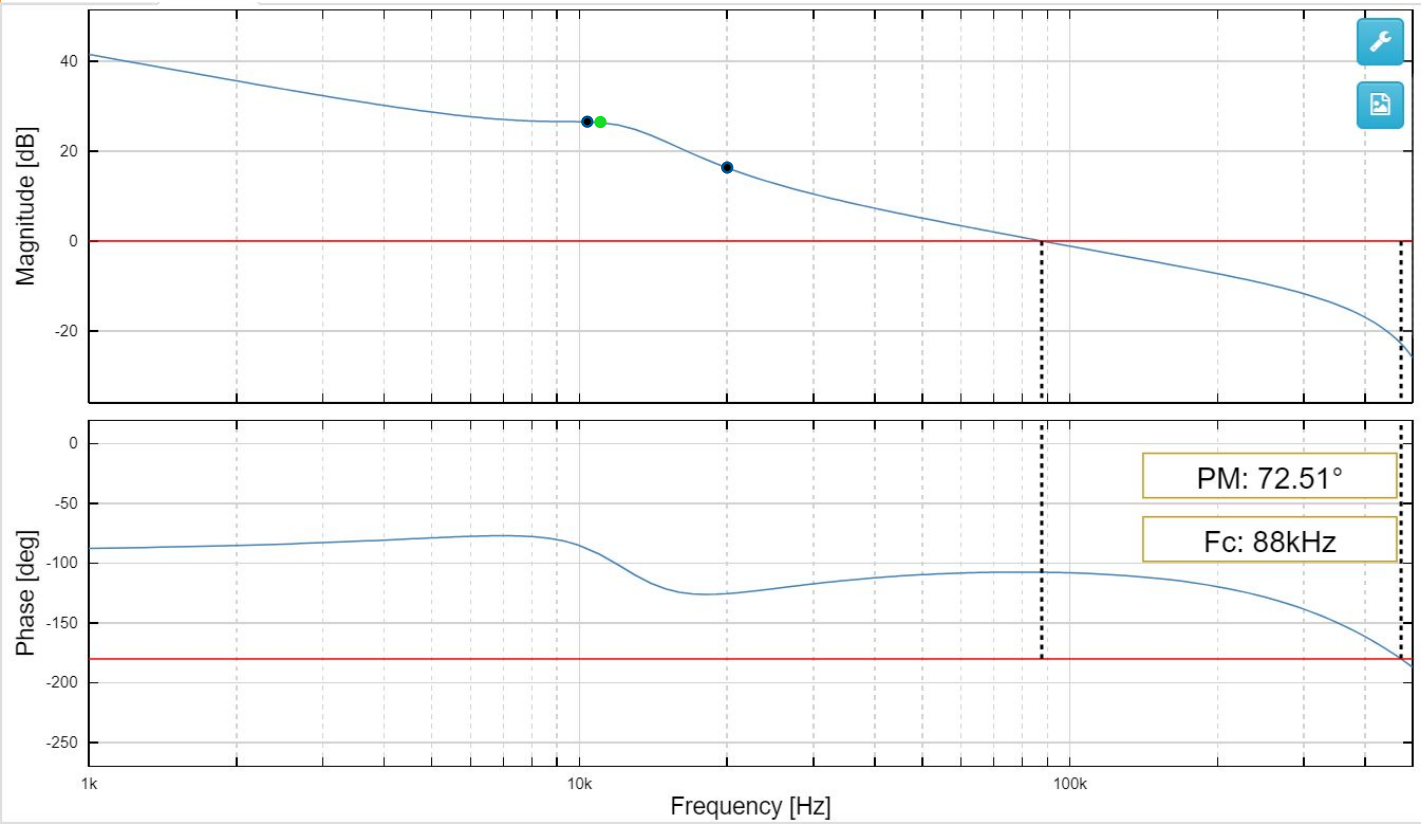

# Compensator Design 4 - Decreasing $f_{z1}$ and $f_{z2}$

Gain = 650  
 Z1 = 8 kHz  
 Z2 = 15 kHz

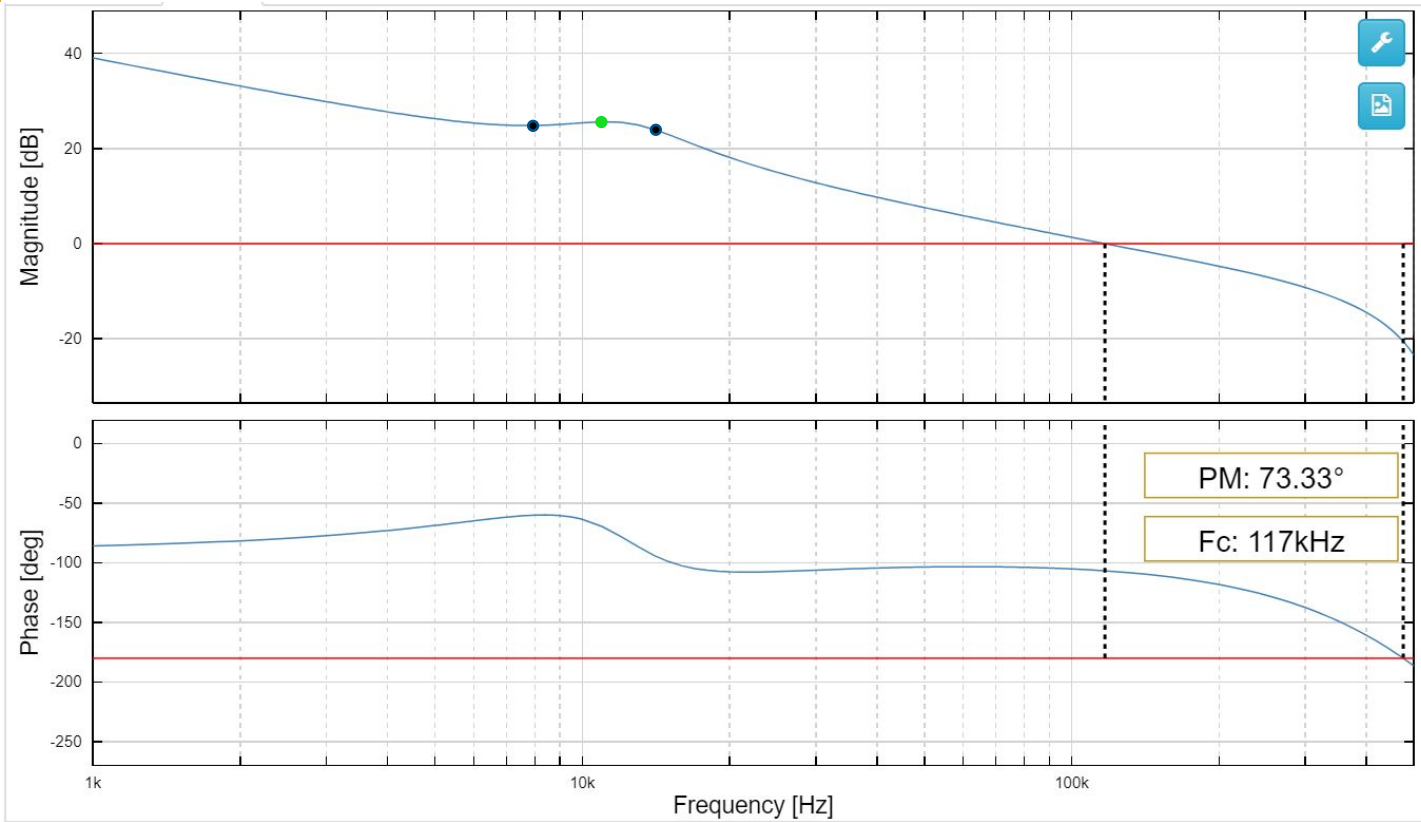

- Crossover frequency,  $f_c = 117$  kHz is too high for  $F_{sw} = 571$  kHz, resulting in ringing and possible instability
- Thumb-rule: choose  $f_c \leq F_{sw} / 10$
- Bode plot is based on linear modeling, PCB parasitics and other non-linearities affect Bode plot accuracy beyond frequencies =  $F_{sw} / 5$



# Effects of different Gain settings

Z1 = 10.6 kHz

Z2 = 40 kHz

Gain	PM (deg)	Fc (kHz)
650	51	51
800	54	60
950	57	70

- Increased DC Gain increases crossover frequency,  $f_c$





# Compensator Design Steps

1. Place first zero,  $f_{z1}$ , slightly below filter's resonant frequency,  $f_{LC} = 1/(2*\pi*\sqrt{LC})$
2. Place second zero,  $f_{z2}$  at around  $f_{SW}/12$
3. Modify DC gain to obtain desired crossover frequency

- Recommendations:

- Crossover frequency ( $F_c$ ):

- Optimal:  $0.05*f_{SW} < F_c < 0.1*f_{SW}$
- Acceptable:  $0.03*f_{SW} < F_c < 0.12*f_{SW}$

- Phase Margin (PM):

- Optimal:  $PM > 45^\circ$
- Acceptable:  $PM > 35^\circ$

